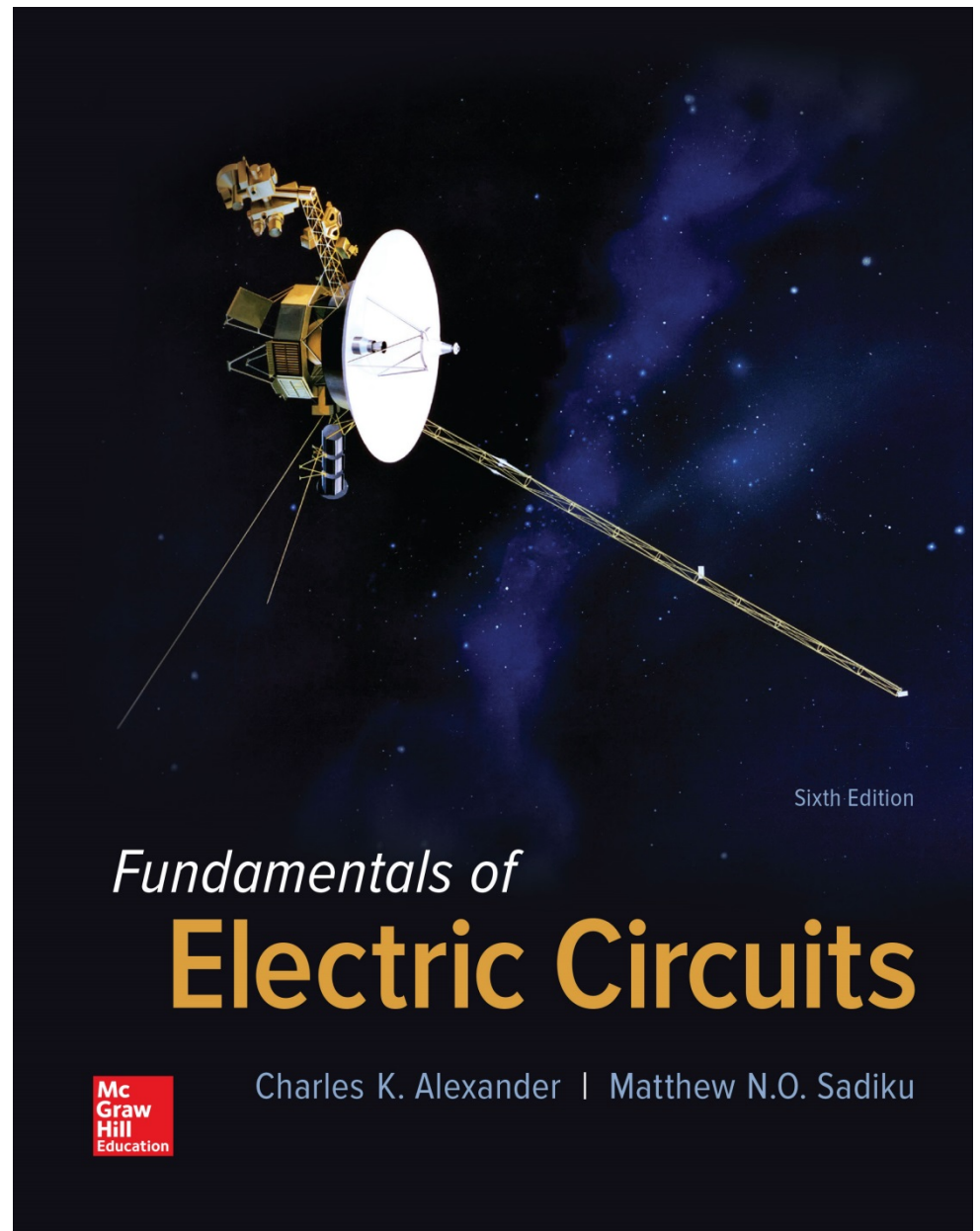


Fundamentals of Electric Circuits Chapter 1




Introduction

- **This chapter introduces the concept of voltage and current.**
- **The concept of a circuit will be introduced.**
- **Sources will be introduced.**
- **These can provide either a specified voltage or current.**
- **Dependent and independent sources will be discussed.**
- **Also a strategy for solving problems will be introduced.**

What is a circuit?

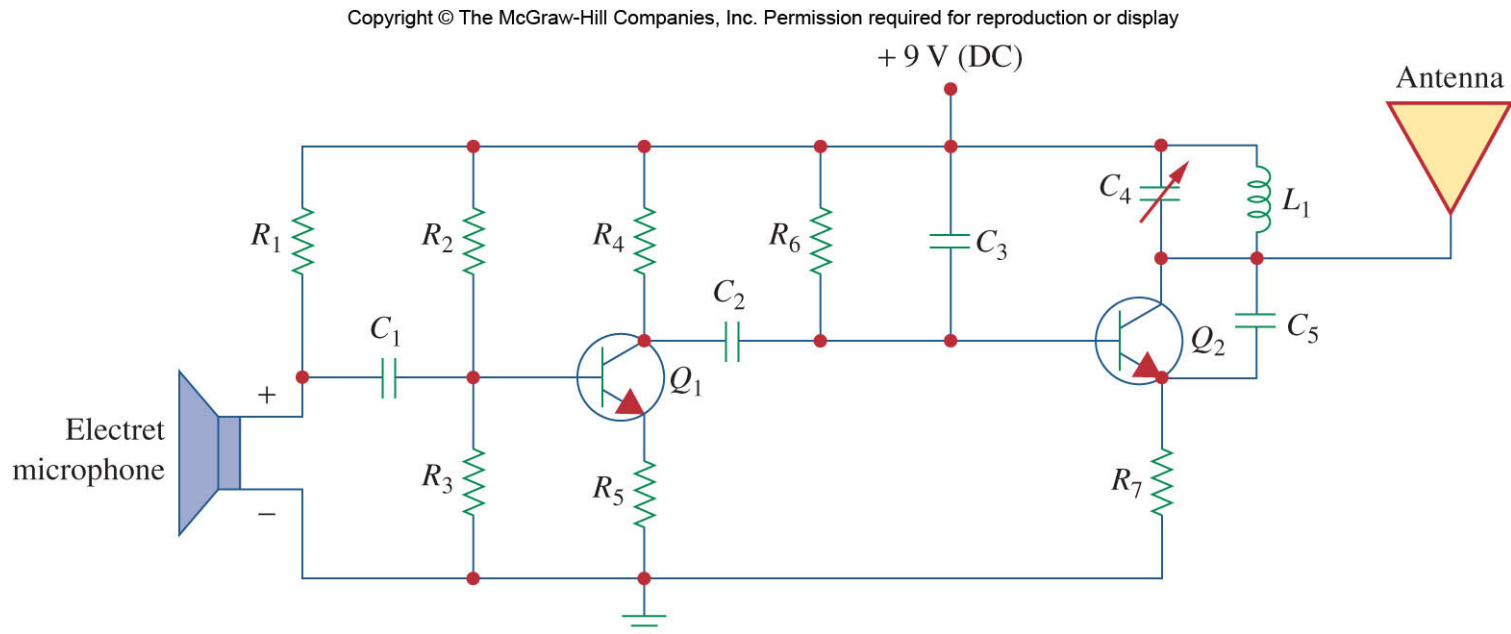- An electric circuit is an interconnection of electrical elements.
- It may consist of only two elements or many more:



Units

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

TABLE 1.2

The SI prefixes.

Multiplier	Prefix	Symbol
10^{18}	exa	E
10^{15}	peta	P
10^{12}	tera	T
10^9	giga	G
10^6	mega	M
10^3	kilo	k
10^2	hecto	h
10	deka	da
10^{-1}	deci	d
10^{-2}	centi	c
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f
10^{-18}	atto	a

- **When taking measurements, we must use units to quantify values**
- **We use the International Systems of Units (SI for short)**
- **Prefixes on SI units allow for easy relationships between large and small values**

Charge

- **Charge** is a basic SI unit, measured in **Coulombs (C)**
- Counts the number of electrons (or positive charges) present.
- **Charge** of single **electron** is **$1.602 \times 10^{-19} \text{ C}$**
- One Coulomb is quite large, 6.24×10^{18} electrons.


Charge II

- In the lab, one typically sees (pC, nC, or μC)
- Charge is always multiple of electron charge
- Charge cannot be created or destroyed, only transferred.

Current

- The movement of charge is called a current
- Historically the moving charges were thought to be positive
- Thus we always note the direction of the equivalent positive charges, even if the moving charges are negative.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display

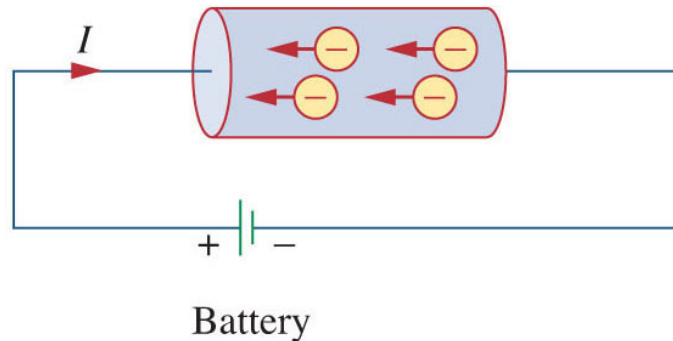

Current II

- **Current, i , is measured as charge moved per unit time through an element.**

$$i \equiv \frac{dq}{dt}$$


$$Q \triangleq \int_{t_0}^t i \, dt$$

- **Unit is Ampere (A), is one Coulomb/second**


DC vs. AC

- A current that remains constant with time is called Direct Current (DC)
- Such current is represented by the capital I , time varying current uses the lowercase, i .
- A common source of DC is a battery.
- A current that varies sinusoidally with time is called Alternating Current (AC)
- Mains power is an example of AC

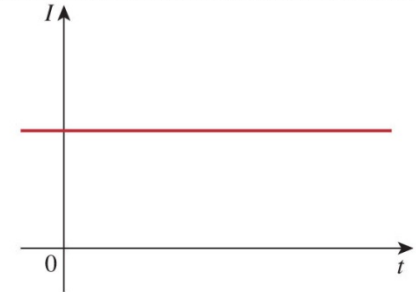Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



(a)

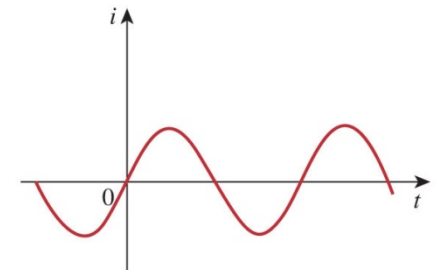

(b)


Direction of current

- **The sign of the current indicates the direction in which the charge is moving with reference to the direction of interest we define.**
- **We need not use the direction that the charge moves in as our reference, and often have no choice in the matter.**

Direction of Current II


- A positive current through a component is the same as a negative current flowing in the opposite direction.

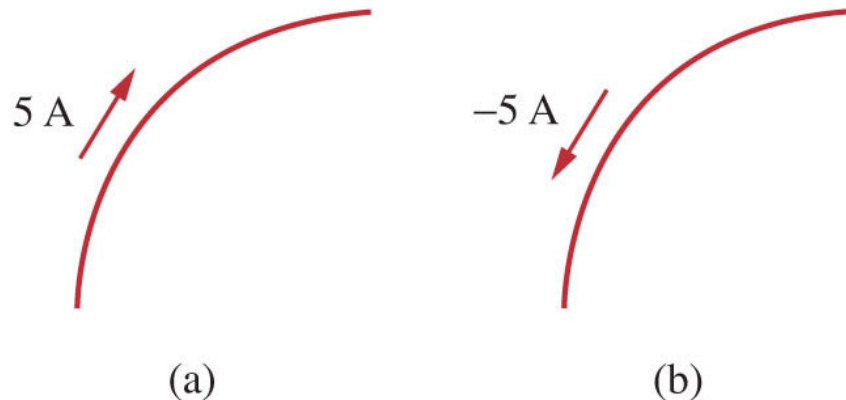Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




Voltage

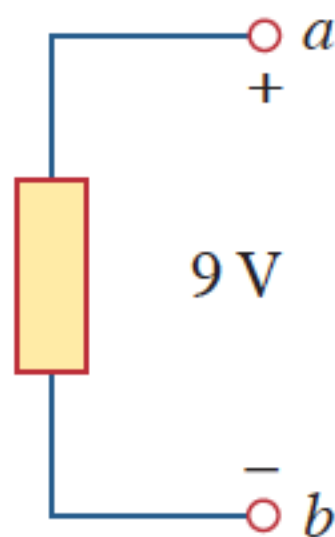- **Electrons move when there is a difference in charge between two locations.**
- **This difference is expressed at the potential difference, or voltage (V).**
- **It is always expressed with reference to two locations**



(a)

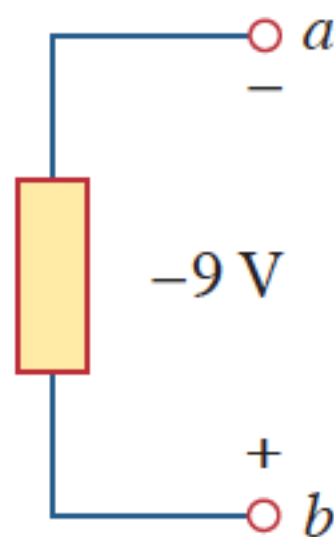

(b)

$$v_{ab} = -v_{ba}$$

Figure 1.7

Two equivalent representations of the same voltage v_{ab} : (a) point a is 9 V above point b , (b) point b is -9 V above point a .

Voltage II

- It is equal to the energy needed to move a unit charge between the locations.
- Positive charge moving from a higher potential to a lower yields energy.
- Moving from negative to positive requires energy.

Power and Energy

- Voltage alone does not equal power.
- It requires the movement of charge, *i.e.* a current.
- Power is the product of voltage and current

$$p = vi$$


$$p \triangleq \frac{dw}{dt}$$

- It is equal to the rate of energy provided or consumed per unit time.
- It is measured in Watts (W)

Passive Sign Convention

- By convention, we say that **an element being supplied power has positive power**.
- A **power source**, such as a battery has **negative power**.
- Passive sign convention is satisfied if the direction of current is selected such that current enters through the terminal that is more positively biased.

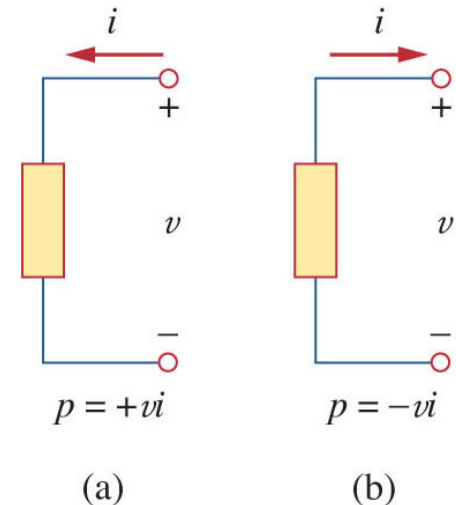Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Conservation of Energy

- In a circuit, energy cannot be created or destroyed.
- Thus power also must be conserved
- The sum of all power supplied must be absorbed by the other elements.
- Energy can be described as watts x time.
- Power companies usually measure energy in watt-hours

$$p \triangleq \frac{dw}{dt}$$


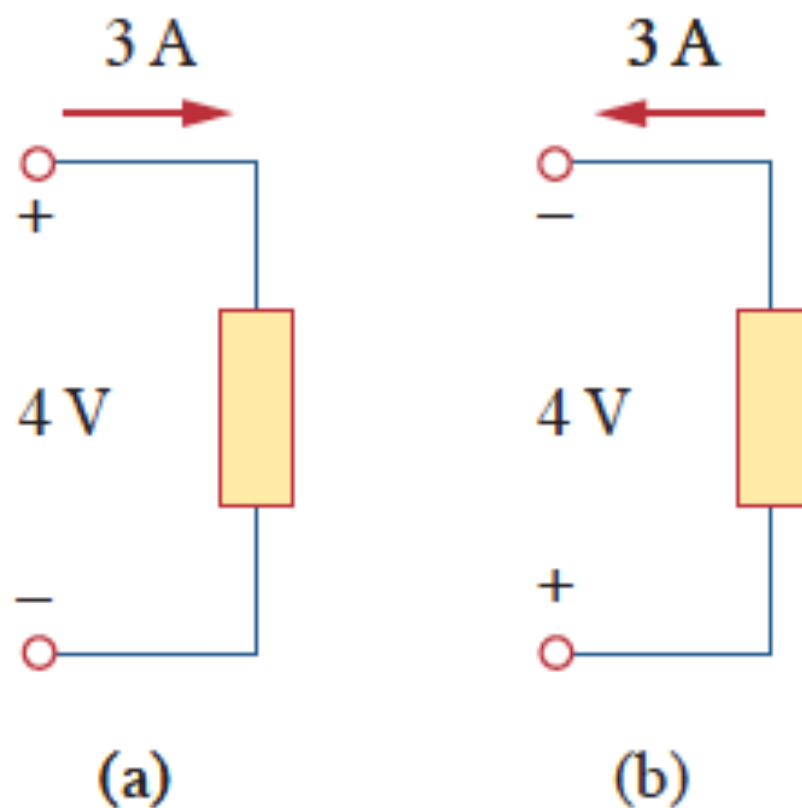


Figure 1.9


Two cases of an element with an absorbing power of 12 W: (a) $p = 4 \times 3 = 12$ W, (b) $p = 4 \times 3 = 12$ W.

Circuit Elements

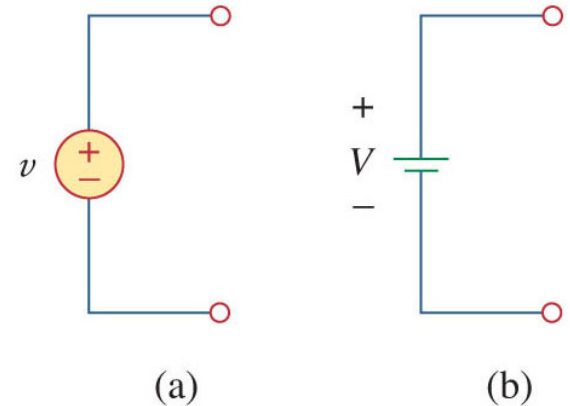
- Two types:
 - Active
 - Passive
- **Active elements can generate energy**
 - Generators
 - Batteries
 - Operational Amplifiers



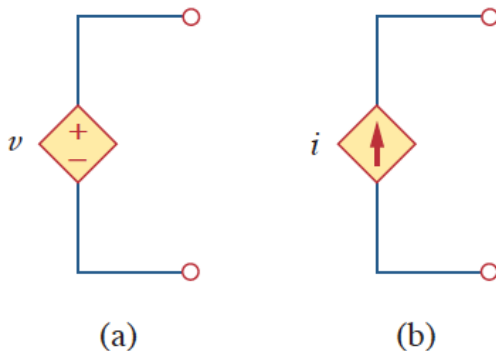Symbols for independent voltage sources:
(a) used for constant or time-varying voltage,
(b) used for constant voltage (dc).



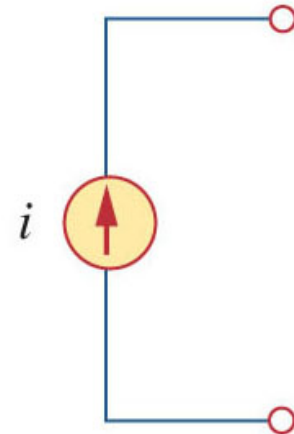Symbols for: (a) dependent voltage source, (b) dependent current source



Symbol for independent current source.

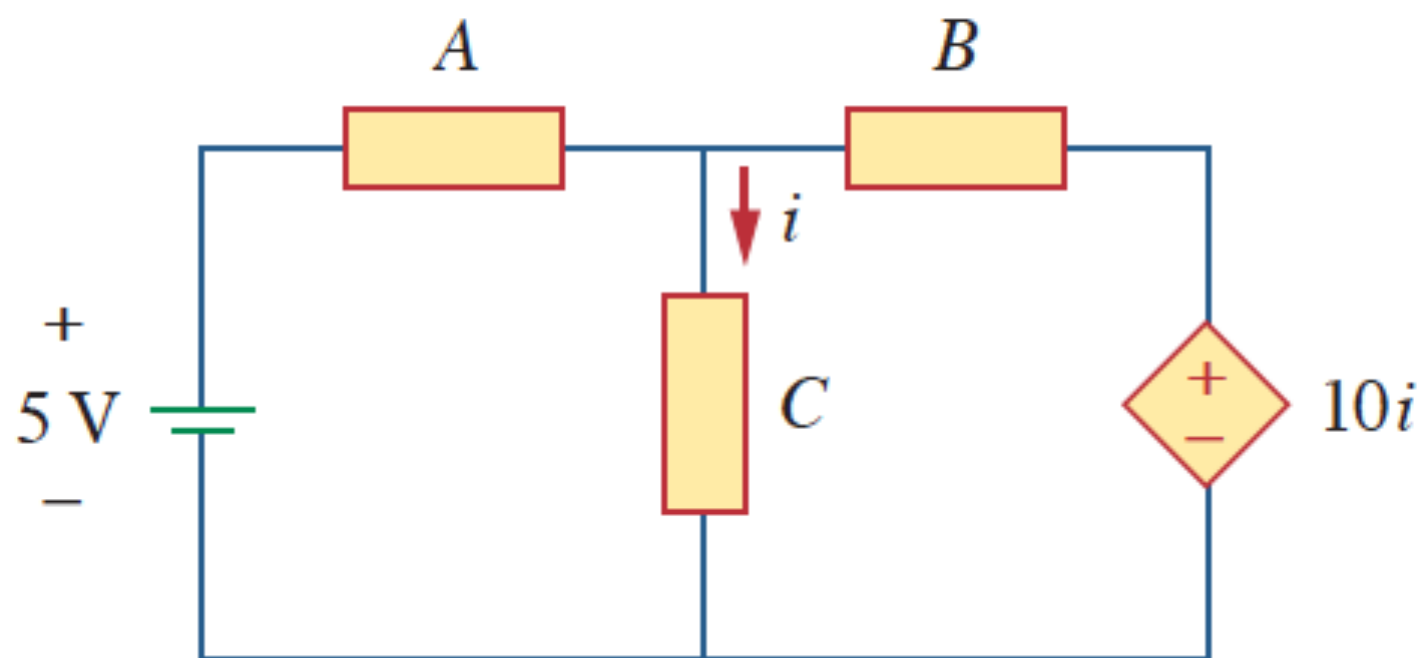


Figure 1.14

The source on the right-hand side is a current-controlled voltage source.

Circuit Elements II

- **Passives** absorb energy
 - Resistors
 - Capacitors
 - Inductors
- But it should be noted that only the resistor dissipates energy ideally.
- The inductor and capacitor do not.

Example 1.5

Find the power delivered to an element at $t = 3$ ms if the current entering its positive terminal is

$$i = 5 \cos 60\pi t \text{ A}$$

and the voltage is: (a) $v = 3i$, (b) $v = 3 di/dt$.

Solution:

(a) The voltage is $v = 3i = 15 \cos 60\pi t$; hence, the power is

$$p = vi = 75 \cos^2 60\pi t \text{ W}$$

At $t = 3$ ms,

$$p = 75 \cos^2 (60\pi \times 3 \times 10^{-3}) = 75 \cos^2 0.18\pi = 53.48 \text{ W}$$

(b) We find the voltage and the power as

$$v = 3 \frac{di}{dt} = 3(-60\pi)5 \sin 60\pi t = -900\pi \sin 60\pi t \text{ V}$$

$$p = vi = -4500\pi \sin 60\pi t \cos 60\pi t \text{ W}$$

At $t = 3$ ms,

$$\begin{aligned} p &= -4500\pi \sin 0.18\pi \cos 0.18\pi \text{ W} \\ &= -14137.167 \sin 32.4^\circ \cos 32.4^\circ = -6.396 \text{ kW} \end{aligned}$$

Example 1.7

Calculate the power supplied or absorbed by each element in Fig. 1.15.

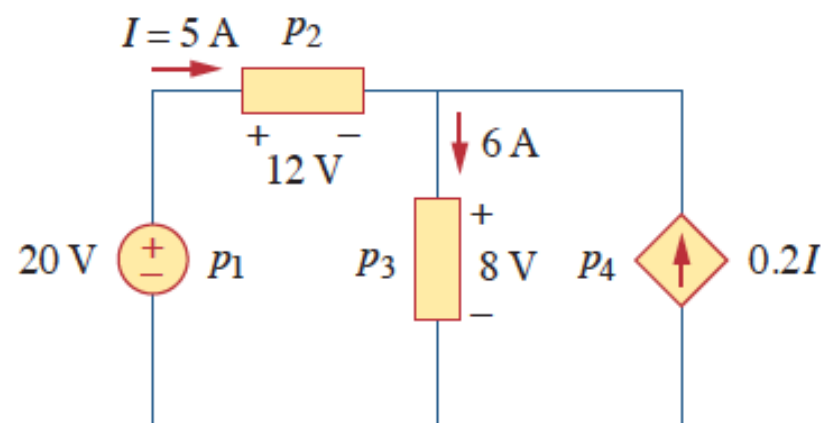


Figure 1.15

For Example 1.7. $p_1 = 20(-5) = -100\text{ W}$ Supplied power

$$p_2 = 12(5) = 60\text{ W} \quad \text{Absorbed power}$$

$$p_3 = 8(6) = 48\text{ W} \quad \text{Absorbed power}$$

$$p_4 = 8(-0.2I) = 8(-0.2 \times 5) = -8\text{ W} \quad \text{Supplied power}$$

$$p_1 + p_2 + p_3 + p_4 = -100 + 60 + 48 - 8 = 0$$

Ideal Voltage Source

- **An ideal voltage source has no internal resistance.**
- **It also is capable of producing any amount of current needed to establish the desired voltage at its terminals.**
- **Thus we can know the voltage at its terminals, but we don't know in advance the current.**

Ideal Current Source

- **An Ideal Current sources** are the opposite of the voltage source:
- They have **infinite resistance**
- They will generate any voltage to establish the desired current through them.
- We can know the current through them in advance, but not the voltage.


Ideal sources

- **Both the voltage and current source ideally can generate infinite power.**
- **They are also capable of absorbing power from the circuit.**
- **It is important to remember that these sources do have limits in reality:**
- **Voltage sources have an upper current limit.**
- **Current sources have an upper voltage limit.**

Dependent Sources

- A dependent source has its output controlled by an input value.
- Symbolically represented as a diamond
- Four types:
 - A voltage-controlled voltage source (VCVS).
 - A current-controlled voltage source (CCVS).
 - A voltage-controlled current source (VCCS).
 - A current-controlled current source (CCCS).

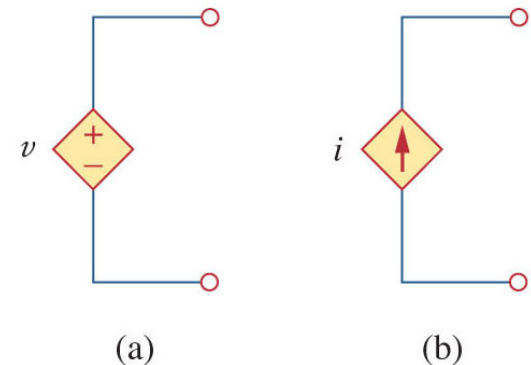
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



Dependent Source example

- The circuit shown below is an example of using a dependent source.
- The source on the right is controlled by the current passing through element C.

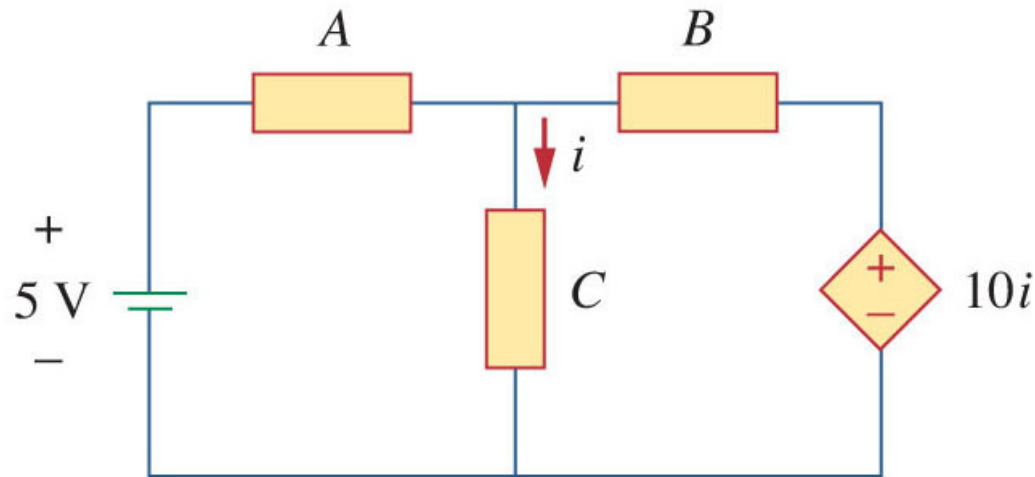Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display




Circuit Applications of Dependent Sources

- **Dependent sources are good models for some common circuit elements:**
 - **Transistors:** In certain modes of operation, transistors take either a voltage or current input to one terminal and cause a current that is somehow proportional to the input to appear at two other terminals.
 - **Operational Amplifiers:** Not covered yet, but the basic concept is they take an input voltage and generate an output voltage that is proportional to that.

TV Picture Tube

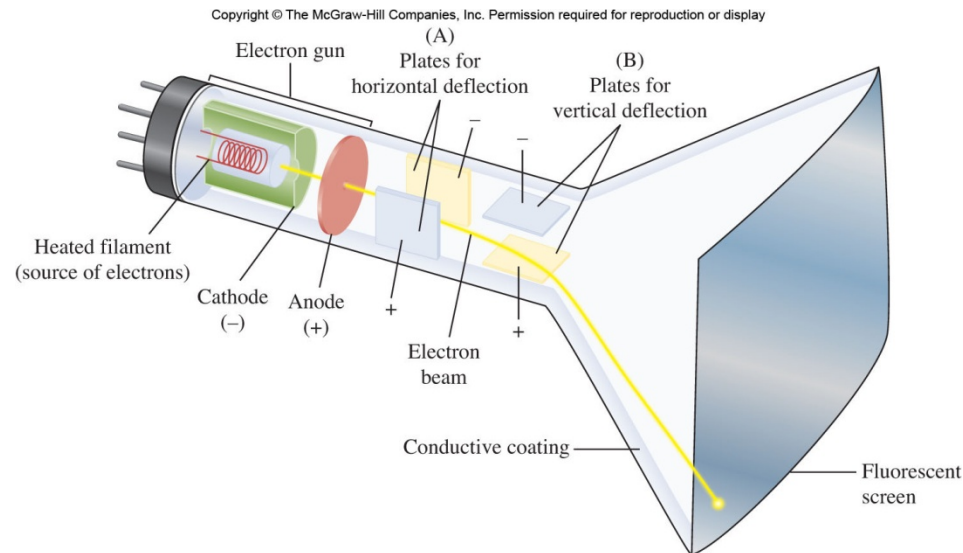- Old style cathode Ray Tubes (CRT) are a good example of the flow of electrons
- A hot filament is the source of electrons
- Charged plates accelerate and steer a thin stream (beam) of electrons
- The beam strikes a phosphor coated screen causing light emission.



Problem Solving I

- **Successfully solving an engineering problem requires a process.**
- **Shown here is an effective method for determining the solution any problem.**
 1. **Carefully **define** the problem.**
 2. **Present everything you know about the problem.**
 3. **Establish a set of **alternative solutions** and determine the one that promises the greatest likelihood of success.**

Problem Solving II

4. Attempt a **problem solution**.
5. Evaluate the solution and **check for accuracy**.
6. Has the problem been solved satisfactorily? If so, present the solution; if not, then return to step 3 and continue through the process again.

Problem Solving III

- **Carefully define the problem**
 - This is the most important step
 - What needs to be solved?
 - What questions need to be addressed before solving? Find the sources to answer them.
- **Present everything you know about the problem**
 - What do you know?
 - What don't you?

Problem Solving IV

- **Establish a set of alternative solutions and determine the one that promises the greatest likelihood of success.**
 - **Most problems have more than one way to be solved**
 - **But not all solutions are as simple**
 - **Are the required tools available?**

Problem Solving V

- **Attempt to solve the problem**
 - Documenting this process is very important
- **Evaluate the solution and check for accuracy**
 - Does it makes sense?
 - Is it consistent with any assumptions made?
- **Is the solution satisfactory? If not, try an alternate solution.**