

# Digital System Design Lab

## Lab 9 Verilog Exercises

Student ID: D1166506

Name: 周嘉禾

Date: 2023/11/22

## 1. Objectives

- To become familiar with Verilog

## 2. Theorem

None

## 3. Experimental Results

### (1) Step 1

#### a. Think

- Determine d0 and d1 separately by v
- According to v, set led to corresponding pins.
- Fill 7-segment led pins with corresponding graph.

#### b. Code

```
module step1(v, d0, d1);
    input [3:0] v;
    output reg[0:6] d0, d1;

    always @(v) begin
        case(v)
            4'b0000, 4'b1010: d0 = 7'b0000001; // 0
            4'b0001, 4'b1011: d0 = 7'b1001111; // 1
            4'b0010, 4'b1100: d0 = 7'b0010010; // 2
            4'b0011, 4'b1101: d0 = 7'b0000110; // 3
            4'b0100, 4'b1110: d0 = 7'b1001100; // 4
            4'b0101, 4'b1111: d0 = 7'b0100100; // 5
            4'b0110: d0 = 7'b0100000; // 6
            4'b0111: d0 = 7'b0001101; // 7
            4'b1000: d0 = 7'b0000000; // 8
            4'b1001: d0 = 7'b0000100; // 9
            default: d0 = 7'b1111111; // default


        endcase

        case(v)
            4'b0000, 4'b0001, 4'b0010,
            4'b0011, 4'b0100, 4'b0101,
            4'b0110, 4'b0111, 4'b1000,
            4'b1001: d1 = 7'b0000001; // 0

            4'b1010, 4'b1011, 4'b1100,
            4'b1101, 4'b1110, 4'b1111: d1 = 7'b1001111; // 1
            default: d1 = 7'b1111111; // default

        endcase
    end
endmodule
```

#### c. Simulation

 

## (2) Step 2

### a. Think


- i. Determine whether key[1] and key[0] is 0 or not.
- ii. According to SW, set led to corresponding pins.
- iii. Fill 7-segment led pins with corresponding graph.
- iv. Show the number A or B according to button.

### b. Code

```
module step2(SW, KEY, HEX3, HEX2);
    input [9:2] SW;
    input [1:0] KEY;
    output reg[0:6] HEX3, HEX2;

    always @(SW, KEY) begin
        if (KEY[1]==0)
            case(SW[9:6])
                4'b0000: HEX3 = 7'b0000001; // 0
                4'b0001: HEX3 = 7'b1001111; // 1
                4'b0010: HEX3 = 7'b0010010; // 2
                4'b0011: HEX3 = 7'b0000110; // 3
                4'b0100: HEX3 = 7'b1001100; // 4
                4'b0101: HEX3 = 7'b0100100; // 5
                4'b0110: HEX3 = 7'b0100000; // 6
                4'b0111: HEX3 = 7'b0001101; // 7
                4'b1000: HEX3 = 7'b0000000; // 8
                4'b1001: HEX3 = 7'b0000100; // 9
                4'b1010: HEX3 = 7'b0001000; // A
                4'b1011: HEX3 = 7'b1100000; // B
                4'b1100: HEX3 = 7'b0110001; // C
                4'b1101: HEX3 = 7'b1000010; // D
                4'b1110: HEX3 = 7'b0110000; // E
                4'b1111: HEX3 = 7'b0111000; // F
                default: HEX3 = 7'b1111111; // default
            endcase
        else
            HEX3 = 7'b1111111;
        if (KEY[0]==0)
            case(SW[5:2])
                4'b0000: HEX2 = 7'b0000001; // 0
                4'b0001: HEX2 = 7'b1001111; // 1
                4'b0010: HEX2 = 7'b0010010; // 2
                4'b0011: HEX2 = 7'b0000110; // 3
                4'b0100: HEX2 = 7'b1001100; // 4
                4'b0101: HEX2 = 7'b0100100; // 5
                4'b0110: HEX2 = 7'b0100000; // 6
                4'b0111: HEX2 = 7'b0001101; // 7
                4'b1000: HEX2 = 7'b0000000; // 8
                4'b1001: HEX2 = 7'b0000100; // 9
                4'b1010: HEX2 = 7'b0001000; // A
                4'b1011: HEX2 = 7'b1100000; // B
                4'b1100: HEX2 = 7'b0110001; // C
                4'b1101: HEX2 = 7'b1000010; // D
                4'b1110: HEX2 = 7'b0110000; // E
                4'b1111: HEX2 = 7'b0111000; // F
                default: HEX2 = 7'b1111111; // default
            endcase
        else
            HEX2 = 7'b1111111;
        end
    end
endmodule
```

### c. Simulation

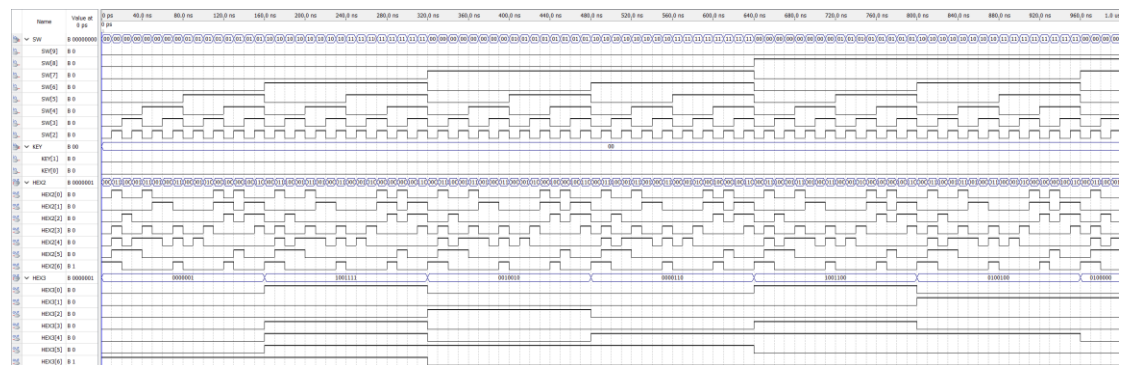

## 4. Comments

None

## 5. Problems & Solutions

None

## 6. Feedback

None