

Digital System Design Lab

Lab 11

Counters/Shift Registers

Student ID: D1166506

Name: 周嘉禾

Date: 2023/12/13

1. Objectives

- To become familiar with shift register in verilog
- To learn how to use counter in verilog

2. Theorem

(1) Counters:

Counters are essential digital circuits used in electronics to count clock pulses or specific events. They're versatile components found in various applications, including digital clocks, frequency dividers, and sequential circuit designs. These circuits can count up, down, or in more complex patterns, facilitating tasks like generating specific sequences or controlling the flow of operations within a system. Counters are integral to the functioning of many digital systems, providing the capability to manage and monitor events or timing within electronic devices.

(2) Shift Registers:

Shift registers are another crucial component in digital electronics used for storing and moving data in a serial manner. They allow the shifting of data bits, enabling serial-to-parallel or parallel-to-serial conversion. Shift registers come in different configurations, such as serial-in-serial-out (SISO), serial-in-parallel-out (SIPO), parallel-in-serial-out (PISO), and parallel-in-parallel-out (PIPO), offering flexibility in data manipulation and transfer. These registers find applications in data storage, data transfer between different parts of a system, and serial data communication.

3. Experimental Results

(1) Step 1

a. Think

- i. Initialize the led
- ii. If reset, reset led to initial status
- iii. If clk, let led shift right

b. Code

```


module step_1(clk, reset, led);
    input clk;
    input reset;
    output reg[7:0] led=8'b10000000;

    initial begin
        led = 8'b10000000;
    end

    always @(posedge clk, negedge reset) begin
        if (!reset) begin
            led <= 8'b10000000; // Reset the shift
        end
        else begin
            led <= {led[0], led[7:1]}; // Shift right
        end
    end
endmodule

```

c. Simulation

 

(2) Step 2

a. *Think*

- i. Initialize the led
- ii. If reset, reset led to initial status 0
- iii. If clk, let count +1/-1 according to dir
- iv. Set led value as count

b. Code

```

module step_2(dir, clk, reset, led);
    input dir;
    input clk;
    input reset;
    output reg[3:0] led=4'b0000;


    reg [3:0] count=0;

    initial begin
        led = 4'b0000;
    end

    always @(posedge clk, negedge reset) begin
        if (!reset) begin
            count = 0;
        end
        else begin
            case (dir)
                1'b0: count = count - 1;
                1'b1: count = count + 1;
            endcase
        end
        led <= count;
    end
endmodule

```

c. Simulation

 

(3) Step 3

a. Think

- i. If reset, reset led to initial status 0/1 according to EO
- ii. If clk, let count +2
- iii. If EO isn't same as last state, reset the count
- iv. Set led value as converted led according to count

b. Code

```
module step_3(EO, clk, reset, led);
    input EO, clk;
    input reset;
    output reg[0:6] led;

    reg [3:0] count;

    initial begin
        case (EO)
            1'b0: count = 0;    // initialize to 0
            1'b1: count = 1;    // initialize to 1
        endcase
    end

    always @(posedge clk or negedge reset) begin
        if (!reset) begin
            case (EO)
                1'b0: count = 0;    // reset to 0
                1'b1: count = 1;    // reset to 1
            endcase
        end
        else if (EO && !(count&1)) count <= 1;
        else if (!EO && count&1) count <= 0;
        else count <= (count + 2) % 10;
    end

    always @* begin
        led = converted_led(count);
    end

    function [0:6] converted_led;
        input [3:0] number;

        begin
            case (number)
                0: converted_led = 7'b0000001;
                1: converted_led = 7'b1001111;
                2: converted_led = 7'b0010010;
                3: converted_led = 7'b0000110;
                4: converted_led = 7'b1001100;
            endcase
        end
    end
```

```


// 5
// 6
// 7
// 8
// 9

5: converted_led = 7'b0100100;
6: converted_led = 7'b0100000;
7: converted_led = 7'b0001101;
8: converted_led = 7'b0000000;
9: converted_led = 7'b0000100;

default: converted_led =
7'b1111111; // default
endcase
end
endfunction
endmodule

```

c. Simulation

 

4. Comments

None

5. Problems & Solutions

None

6. Feedback

None