

A blue header bar at the top of the slide, featuring a solid blue upper portion and a lower portion with light blue wavy lines.


# Lab 34. Basic AC Circuit

# Next Experiment


APP – Magnetic field measurement

## Question 1

# GOS-622G

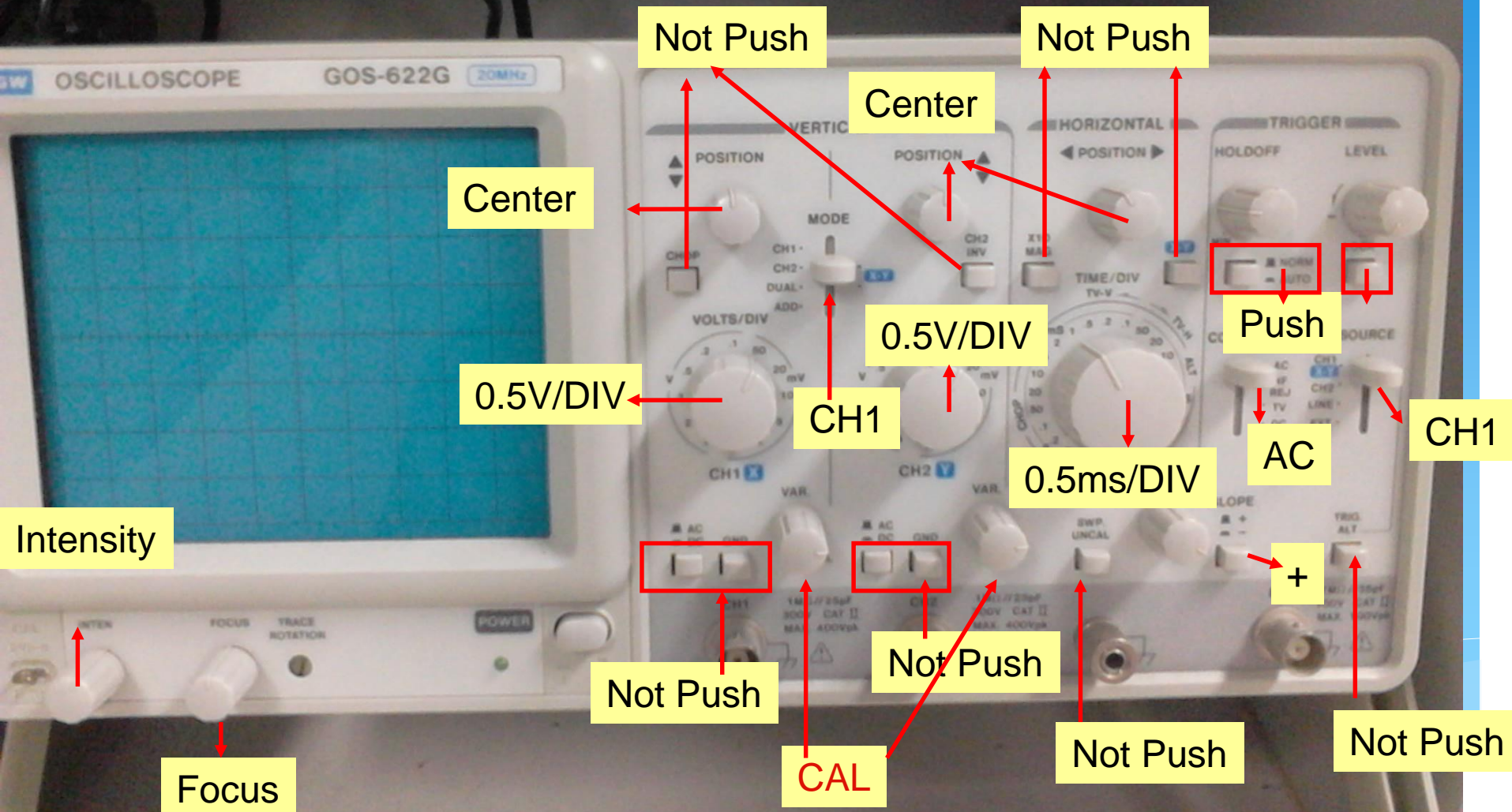

# Function Generator

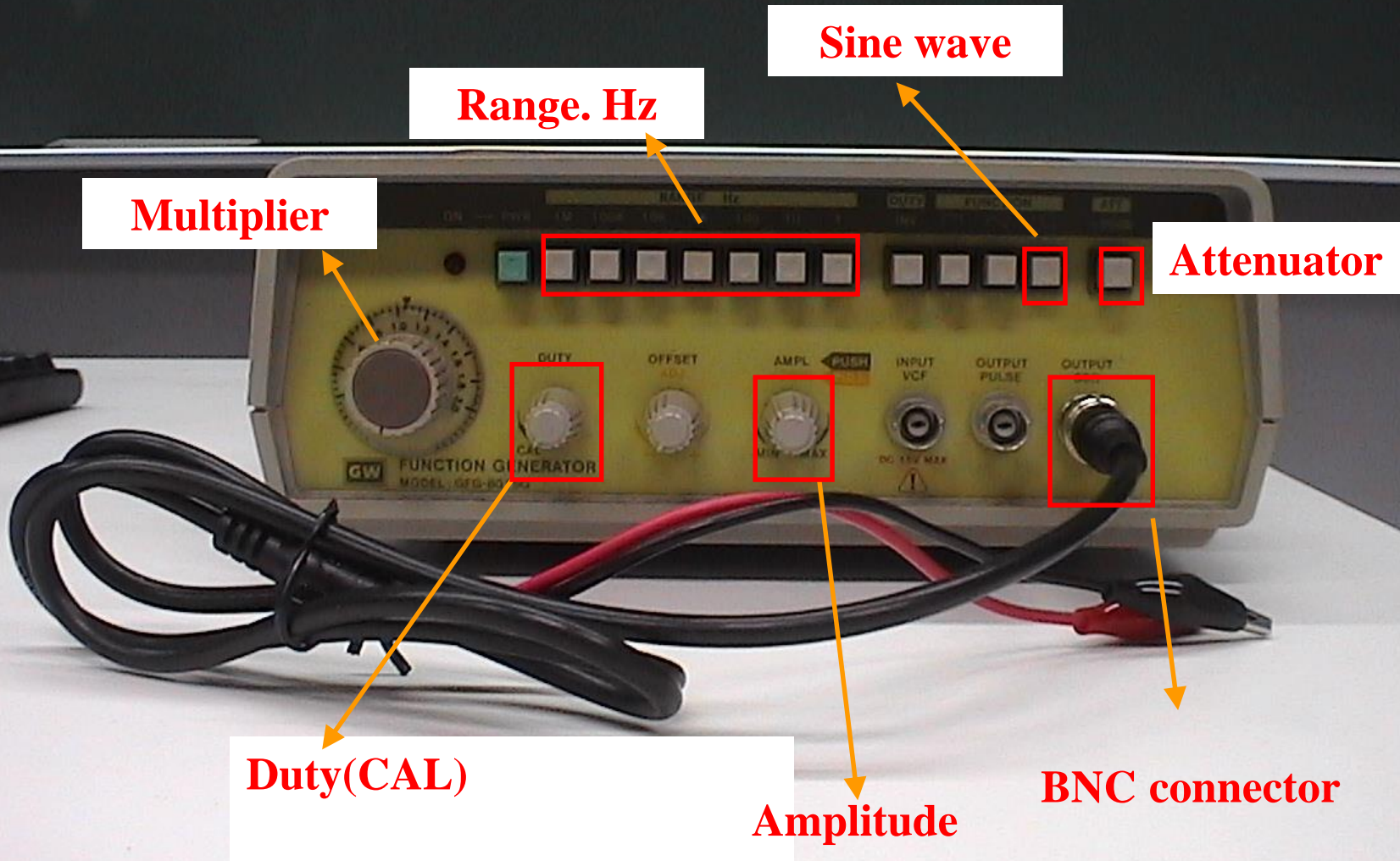

Use an **oscilloscope** to measure

$V_R$   $V_L$   $V_C$   $V_i$




# Procedure

(1) Set the amplitude to 5V




5V

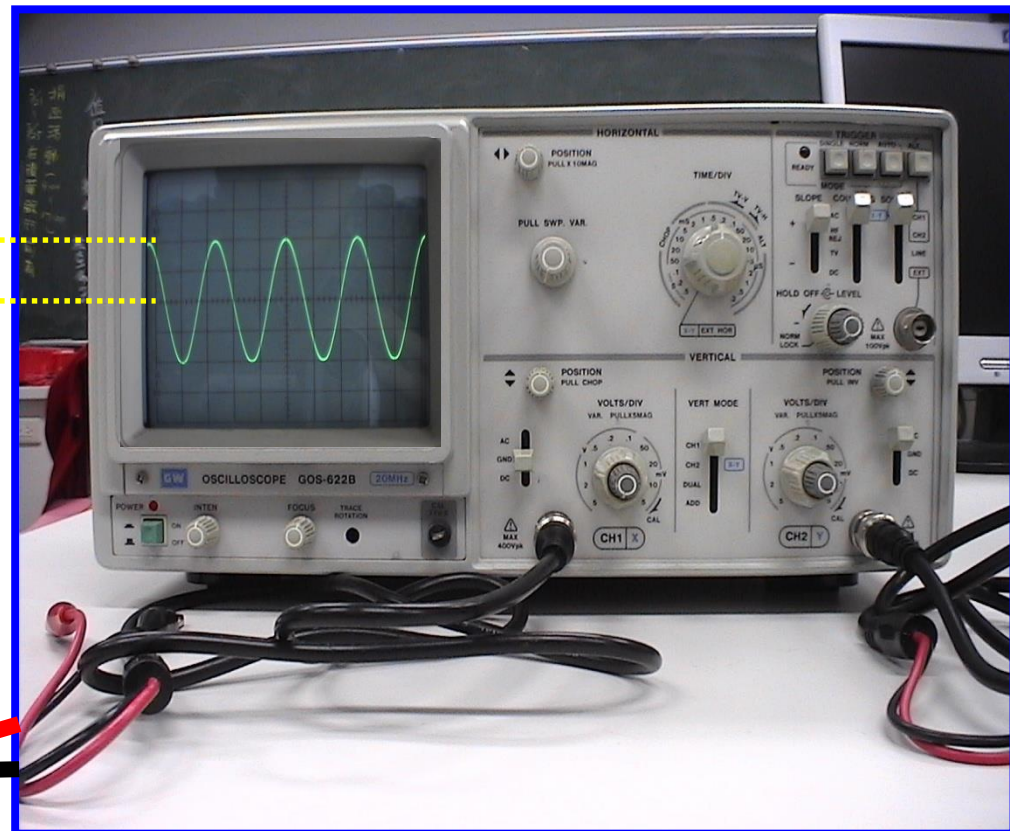

Amplitude = 1V


0.5 V/DIV

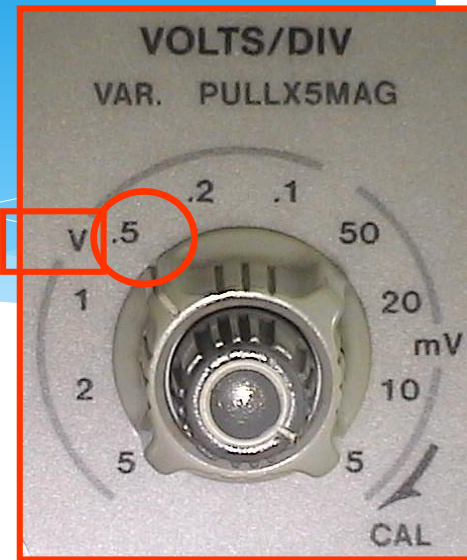

4 divisions


0.5 v/div

$$V_{pp} = 4 \times 0.5 = 2V$$

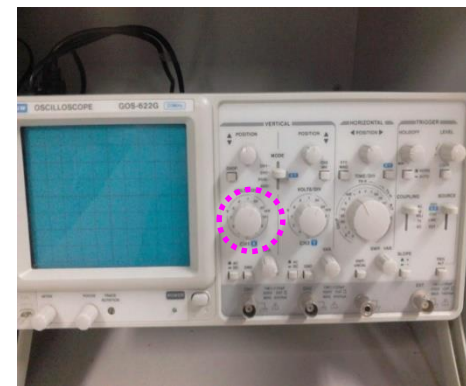

# Procedure

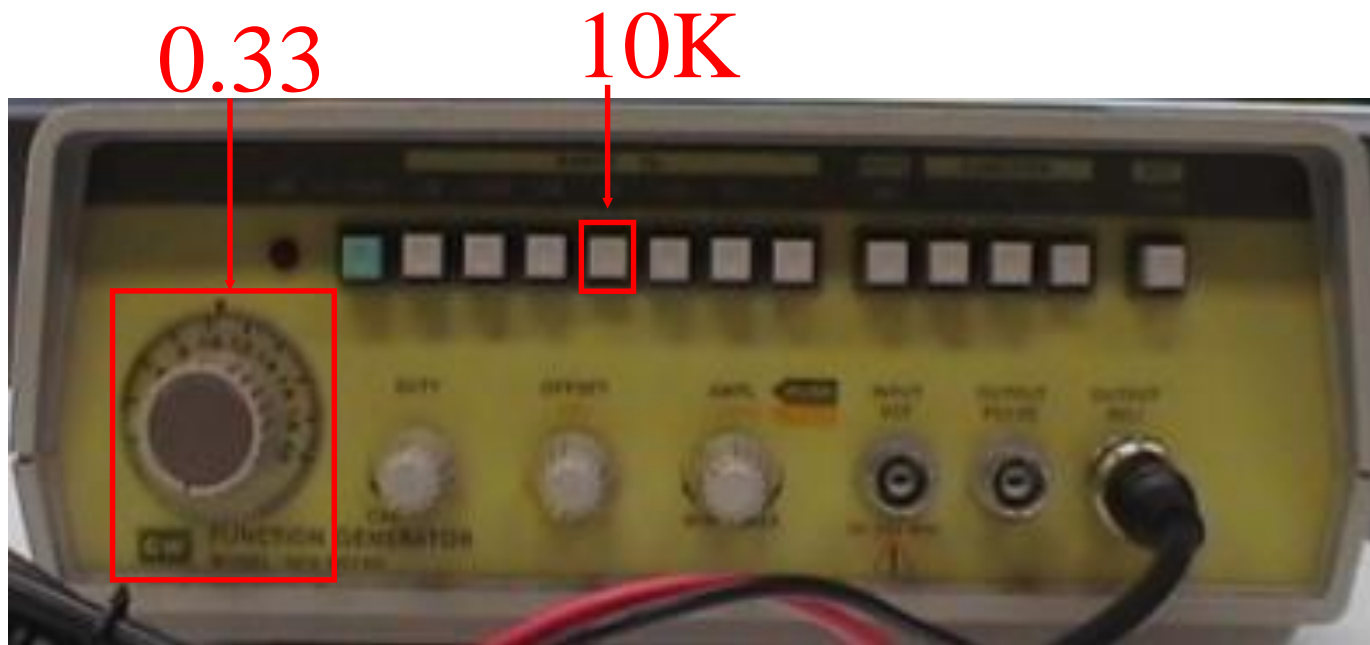(2) Set the frequency to 3.3K Hz. Use the multimeter to double-check its value.



$$3.3\text{K Hz} = 10\text{K} \times 0.33$$



20K Hz


Frequency  
3.3KHz

0.33




10K






Sine

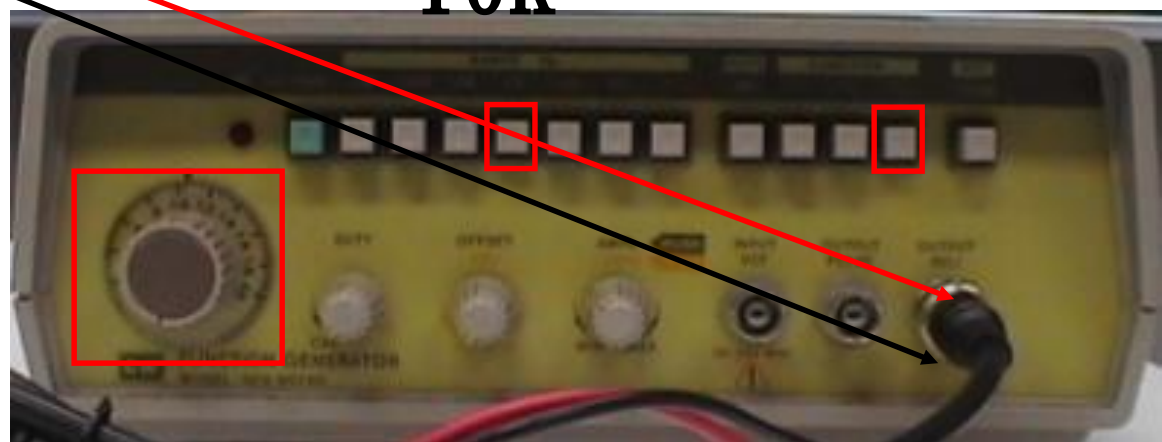

# Procedure

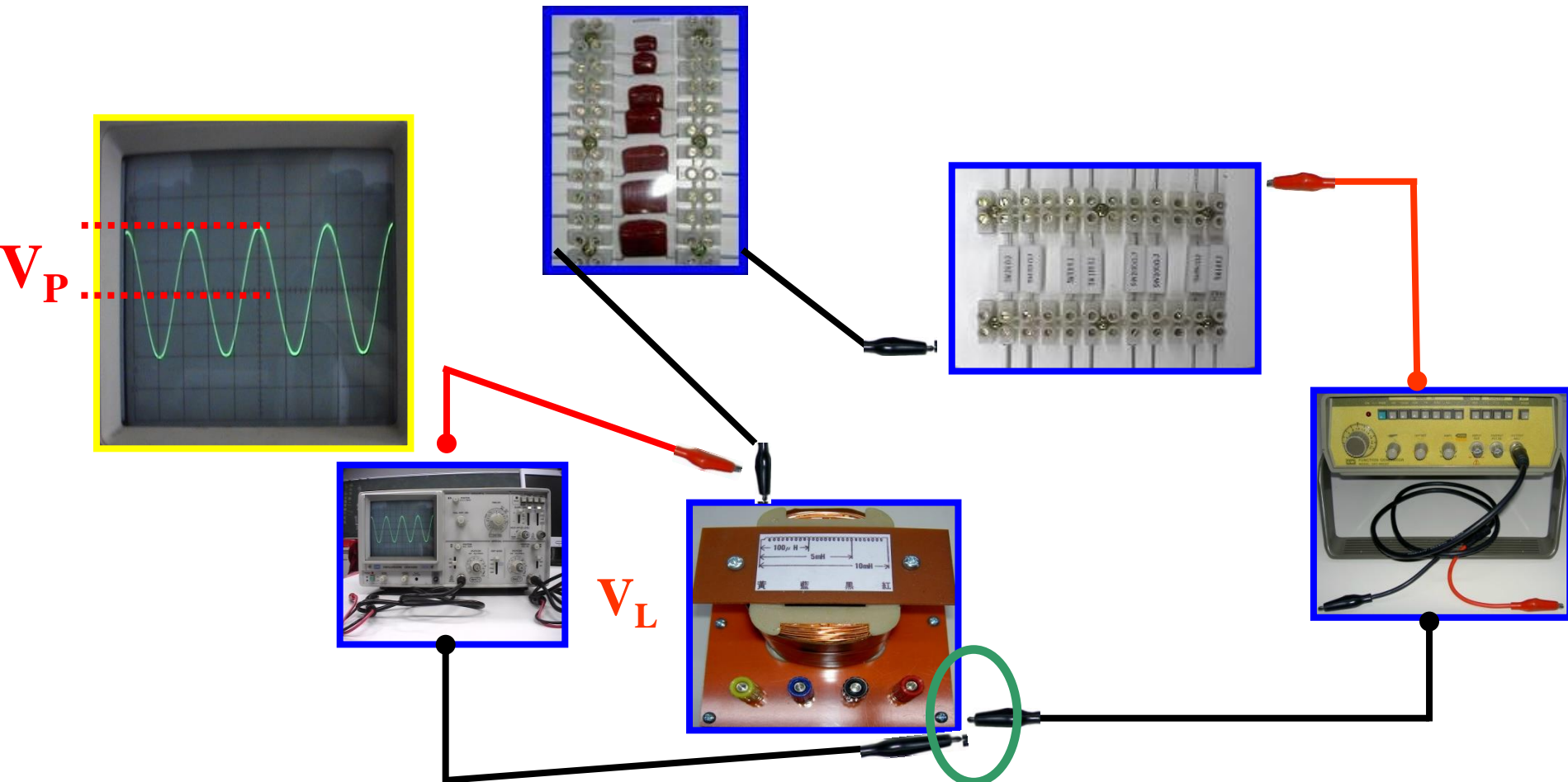(3) Connect **RLC** series circuit as below and use an oscilloscope to measure  $V_R$   $V_L$   $V_C$   $V_i$



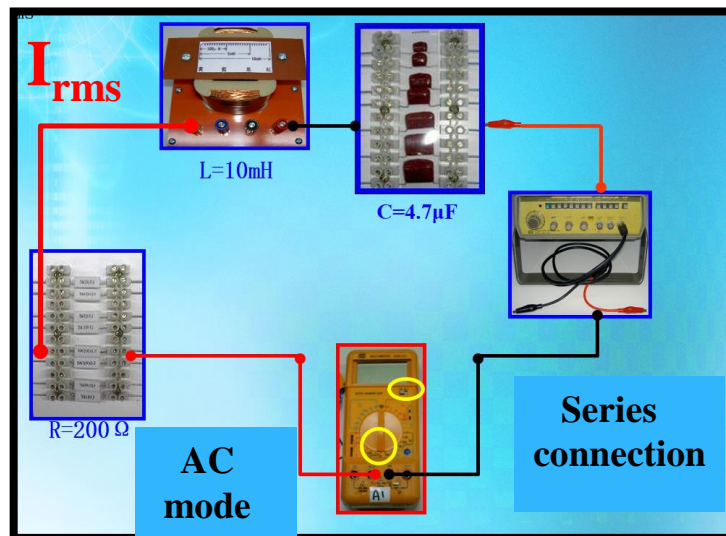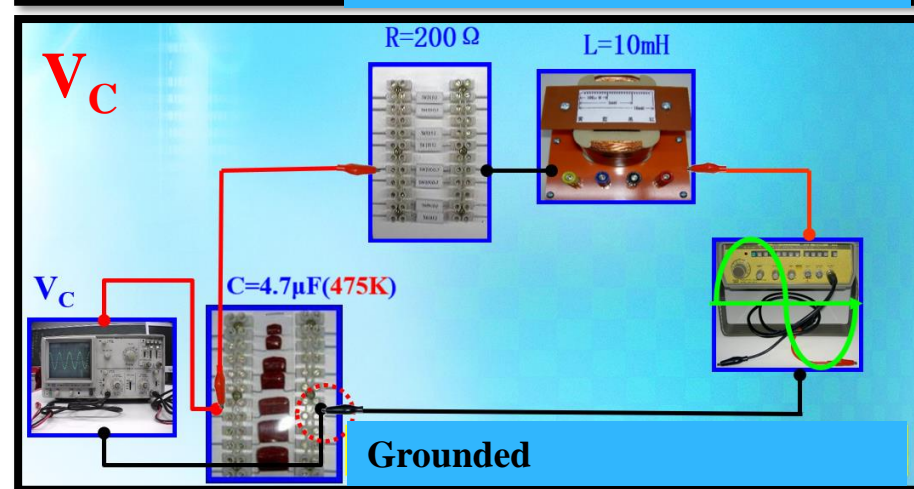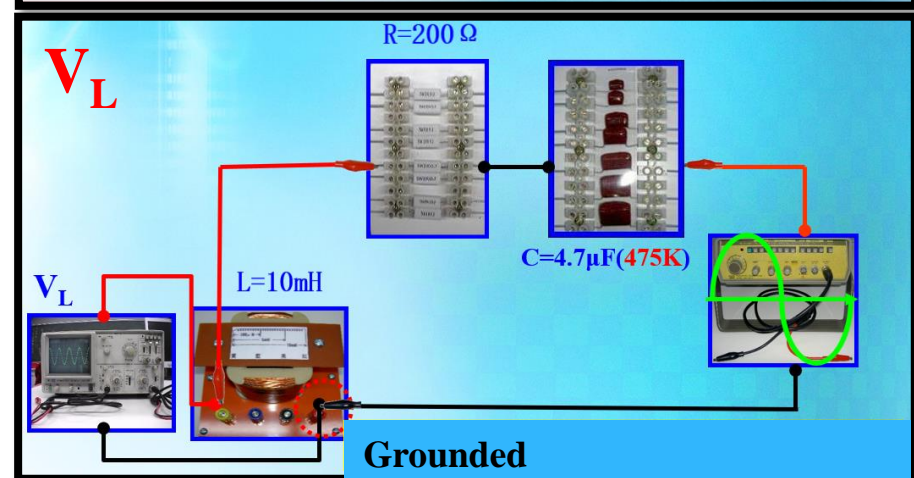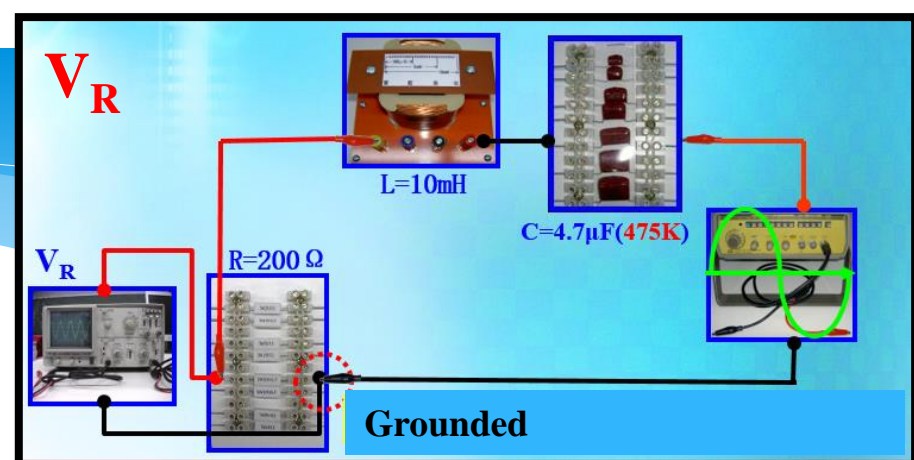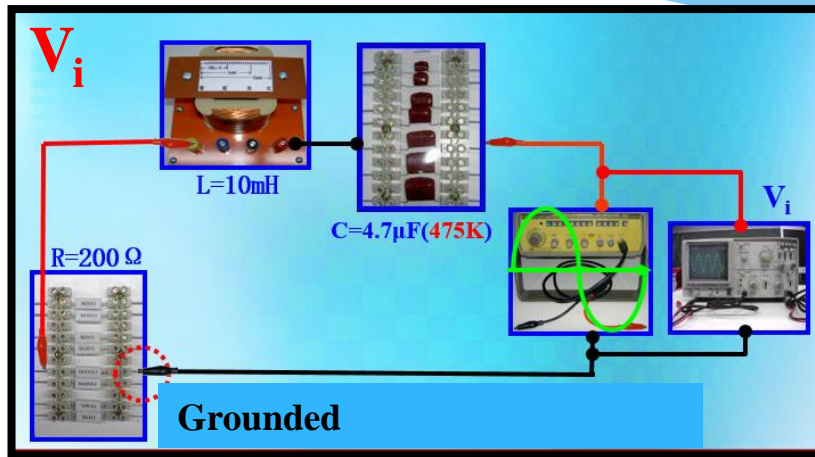

# Report Sheet P.34-5

(3)  $R = 200 \, \Omega$  ,  $L = 10 \, \text{mH}$  ,  $C = 4.7 \, \mu\text{F}$

$10^{-3}$   $10^{-6}$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$f$	$V_m$ (amplitude)						$\Omega$	$I_m$ mA		
(Hz)	$V_R$	$V_L$	$V_C$	$\sqrt{V_R^2 + (V_L - V_C)^2}$	$V_i$	error	$X_L$	$X_C$	$Z$	$V_m/Z$
3.3K	4.8	5	2.5		5					

$$X_L = \omega L$$


$$X_C = 1/\omega C$$

$$\omega = 2\pi f$$



Use the **multimeter** to measure

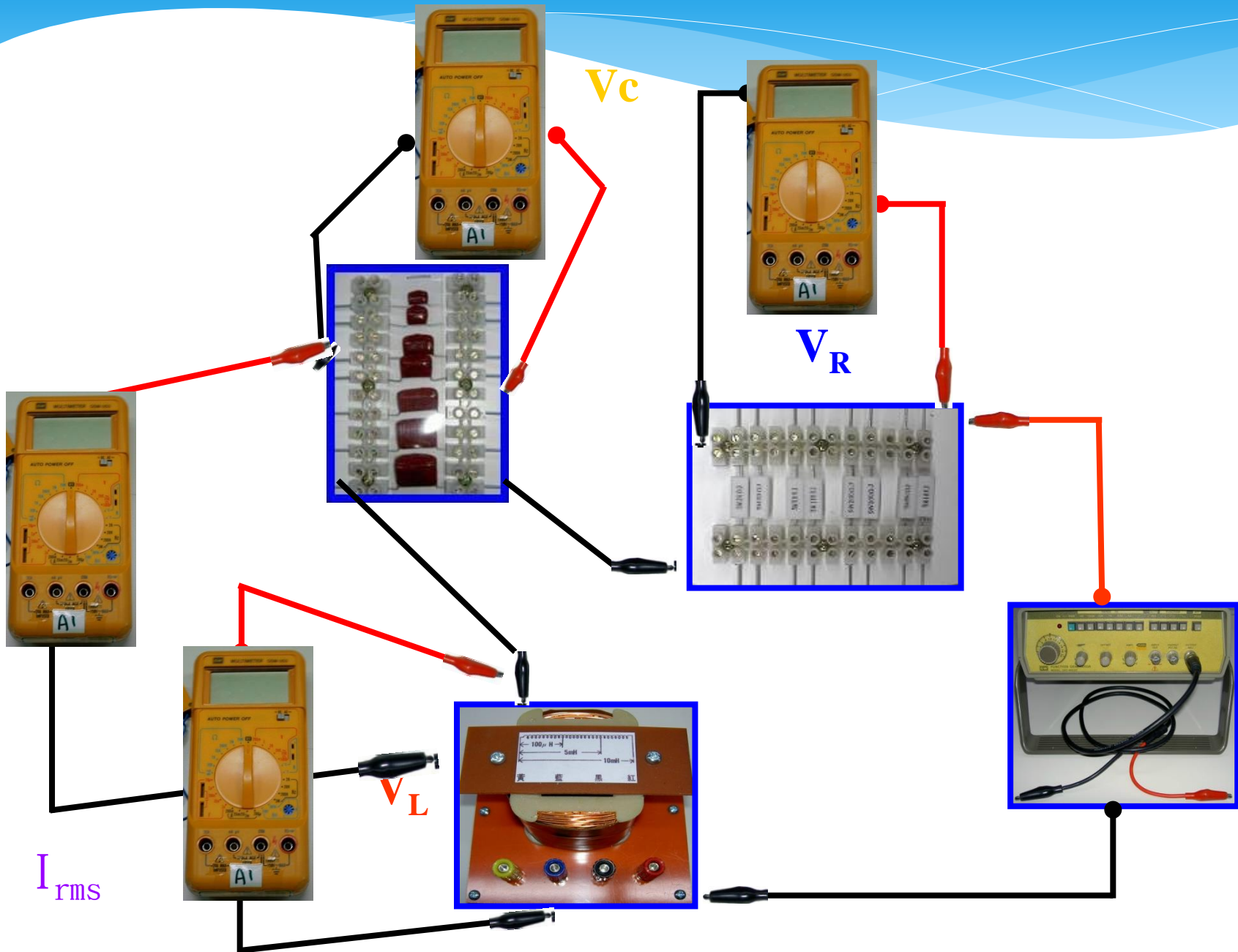$V_R$   $V_L$   $V_C$   $V_i$   $I_{rms}$





# Report Sheet P.34-5

from table 1

[illegible]





$L=10\text{mH}$




$C=4.7\mu\text{F}$



$R=200\ \Omega$



Ground

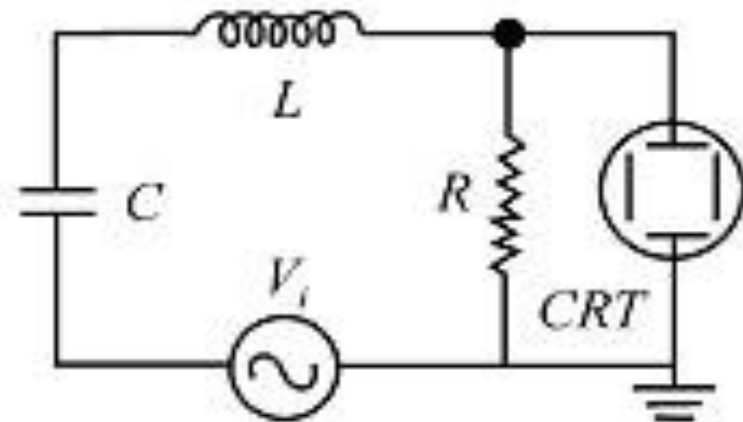


CH1

CH2



CH1

CH2

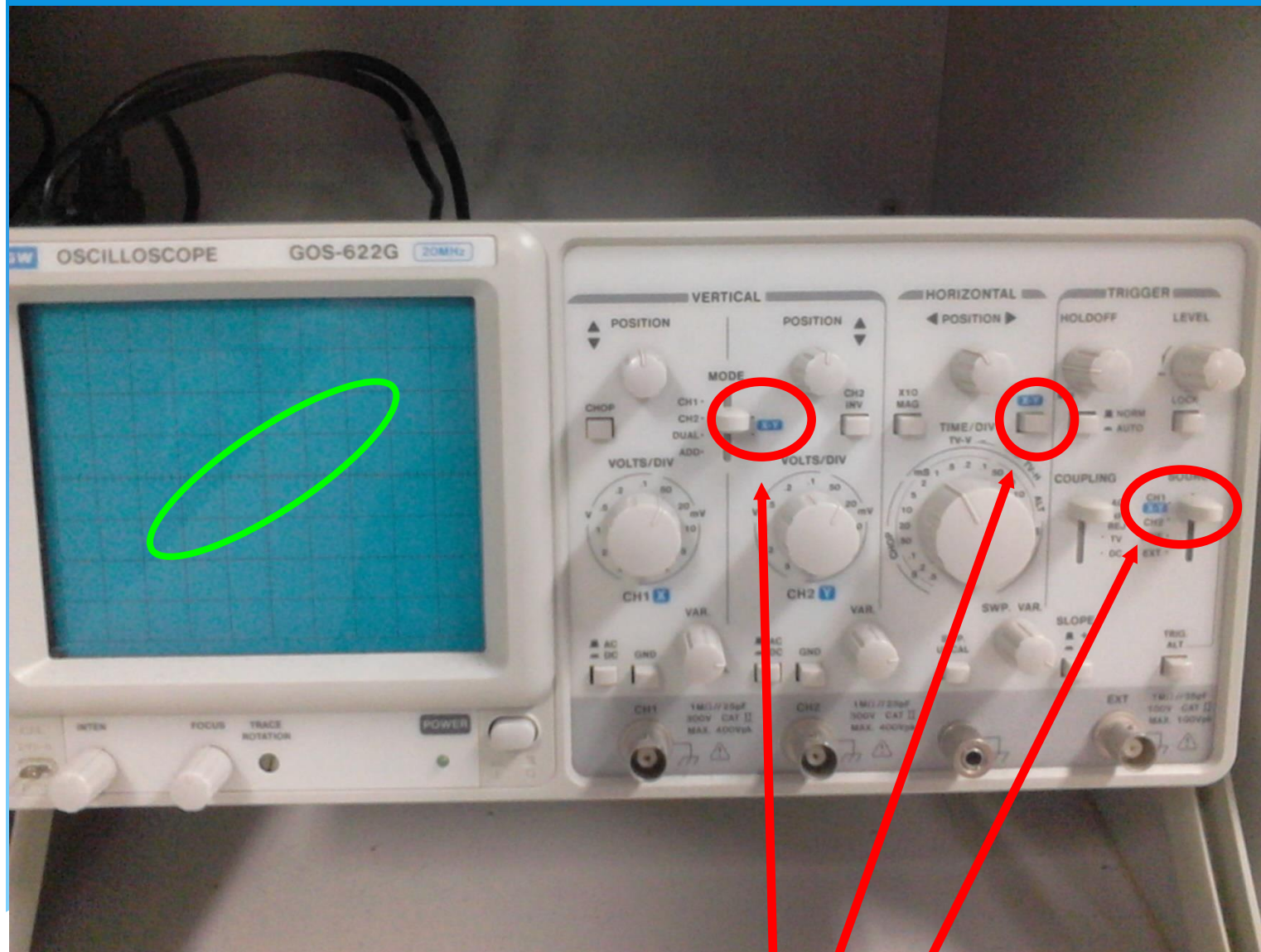

X-Y

# Report Sheet P.34-5

$f$ (Hz)	$X_L$	$X_C$	$\tan^{-1} \frac{X_L - X_C}{R}$	$Y_1$	$Y_2$	$\sin^{-1} \frac{Y_1}{Y_2}$	error
3.3K			Theoretical value	3.5	5	Experimental value	

$$X_L = \omega L$$

$$X_C = 1 / \omega C$$

$$\omega = 2\pi f$$

Use  
oscilloscope

# Measure phase difference

