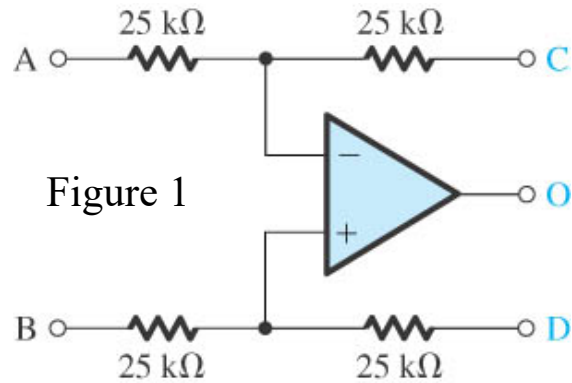


112-2

Electrical Engineering Fundamentals II


Test 2

Keys




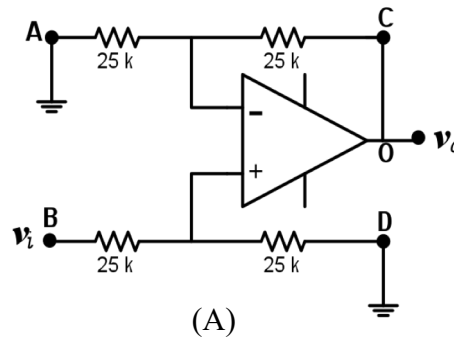1. 10% The circuit shown in Fig. 1 is a representation of a versatile, commercially available IC, the INA 105, manufactured by Burr-Brown and known as a differential amplifier module. It consists of an OP Amp and precision, laser-trimmed, metal-film resistors. The circuit can be configured for a variety of applications by the appropriate connection of terminals, A, B, C, D, and O.


Derive the implemented gain $\frac{v_o}{v_i}$ for (A)~(D).




1

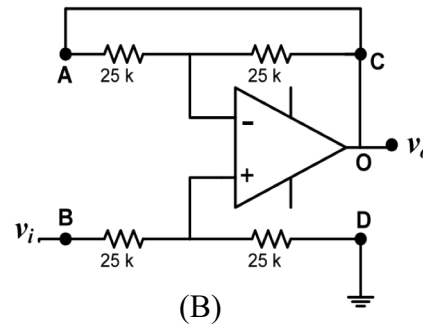

1/2

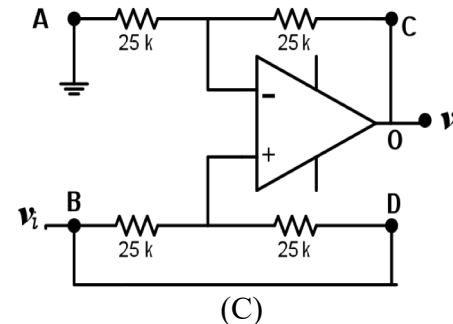

2

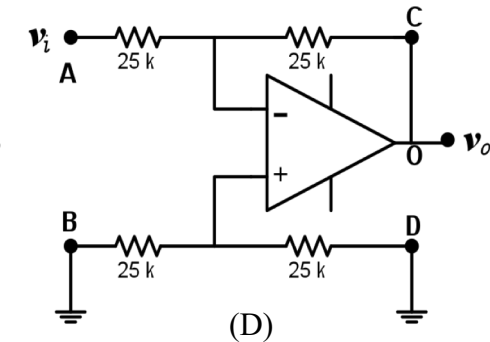

-1

2. (10%) Derive V_O in terms of $V_1 \sim V_4$ for the mathematical operation in the circuit of Figure 2.

$$v_+ = V_1 \times \frac{10 \parallel 20}{20 + 10 \parallel 20} + V_2 \times \frac{20 \parallel 20}{10 + 20 \parallel 20}$$

$$= \frac{1}{4} \cdot V_1 + \frac{1}{2} \cdot V_2$$

$$V_O = v_+ \times \left(1 + \frac{40}{10 \parallel 10}\right) - V_3 \times \frac{40}{10} - V_4 \times \frac{40}{10}$$

$$= \left(\frac{1}{4} \cdot V_1 + \frac{1}{2} \cdot V_2\right) \times 9 - 4 \cdot V_3 - 4 \cdot V_4$$

$$= \frac{9}{4} \cdot V_1 + \frac{9}{2} \cdot V_2 - 4 \cdot V_3 - 4 \cdot V_4$$

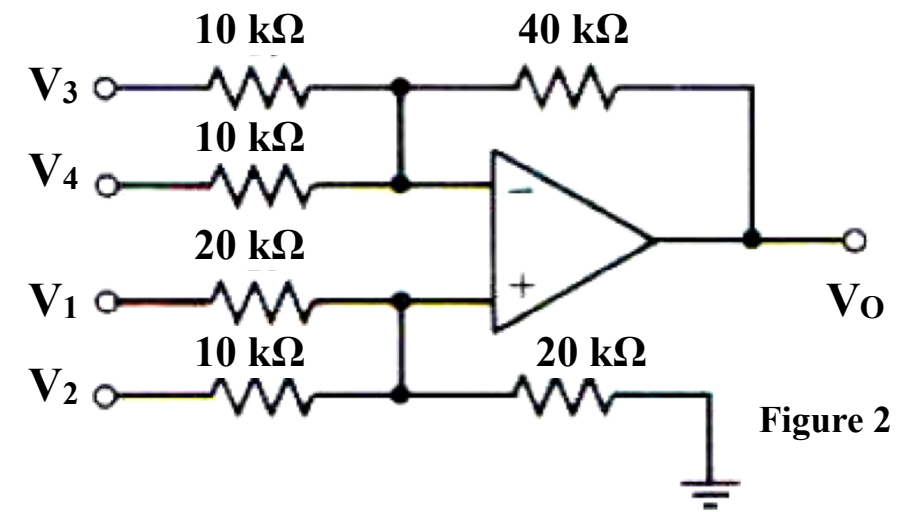


Figure 2

3. (20%) Use only one op amp to implement the function $V_O = \frac{1}{2} \cdot V_1 - \frac{1}{4} \cdot V_2 + \frac{3}{4} \cdot V_3$, with all R's of larger than 10 k Ω but as small as possible. Draw the circuit diagram with your design.

$$V_O = \frac{1}{2} V_1 - \frac{1}{4} V_2 + \frac{3}{4} V_3$$

$$-\frac{R_F}{R_2} = -\frac{1}{4} \Rightarrow R_2 = 4 \cdot R_F \Rightarrow \begin{cases} R_F = 10 \text{ k}\Omega \\ R_2 = 40 \text{ k}\Omega \end{cases}$$


$$V^+ \cdot \left(1 + \frac{R_F}{R_2}\right) = \frac{5}{4} V^+ = \frac{1}{2} V_1 + \frac{3}{4} V_3$$

$$\frac{5}{4} \left(\frac{R_3}{R_1 + R_3} \cdot V_1 + \frac{R_1}{R_1 + R_3} \cdot V_3 \right) = \frac{1}{2} V_1 + \frac{3}{4} V_3$$


$$\Rightarrow \begin{cases} \frac{R_3}{R_1 + R_3} = \frac{4}{10} \\ \frac{R_1}{R_1 + R_3} = \frac{3}{5} = \frac{6}{10} \end{cases}$$

$$\Rightarrow \frac{R_1}{R_3} = \frac{6}{4} \Rightarrow 4R_1 = 6R_3 \Rightarrow R_1 = 1.5 \cdot R_3$$
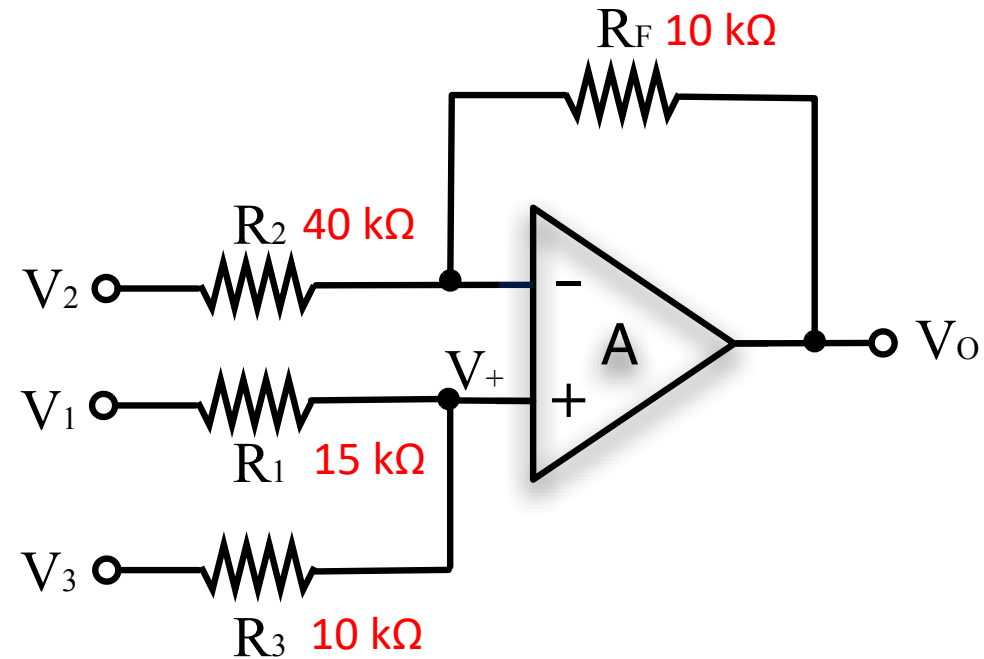
$$\Rightarrow \begin{cases} R_3 = 10 \text{ k}\Omega \\ R_1 = 15 \text{ k}\Omega \end{cases}$$



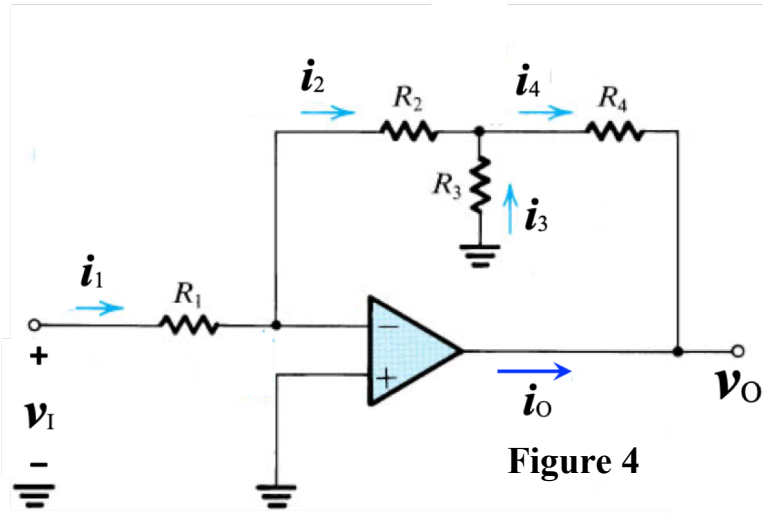4. (15%) The inverting circuit with the T network in the feedback is shown in Fig. 4. Derive the the voltage gain $\frac{v_O}{v_I}$ (10%) and the current gain $\frac{i_O}{i_1}$ (5%).



5. (20%) Design the circuit ($R_1, R_2, R_3 = ?$) to have an input resistance of $100 \text{ k}\Omega$ and a voltage gain that can be varied from $-1 \sim -100$ using the $100\text{-k}\Omega$ potentiometer R_4 . What voltage gain results when the potentiometer is set exactly at its middle value?

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

To obtain an input resistance of $100 \text{ k}\Omega$, we select $R_1 = 100 \text{ k}\Omega$. From Example 2.2 we have

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} \left[1 + \frac{(1-x)R_4}{R_2} + \frac{(1-x)R_4}{R_3 + xR_4} \right]$$

The minimum gain magnitude is obtained when $x = 1$,

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} = -1$$

Thus, $R_2 = 100 \text{ k}\Omega$.

The maximum gain magnitude is obtained when $x = 0$,

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1} \left[1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right] = -100$$

$$\Rightarrow 1 + \frac{100}{100} + \frac{100}{R_3} = 100$$

$$\Rightarrow R_3 = \frac{100}{98} = 1.02 \text{ k}\Omega$$

When the potentiometer is set exactly in the middle, $x = 0.5$ and

$$\begin{aligned} \frac{v_O}{v_I} &= -\frac{R_2}{R_1} \left[1 + \frac{0.5R_4}{R_2} + \frac{0.5R_4}{R_3 + 0.5R_4} \right] \\ &= -\frac{100}{100} \left[1 + \frac{0.5 \times 100}{100} + \frac{0.5 \times 100}{1.02 + 0.5 \times 100} \right] \\ &= -2.48 \text{ V/V} \end{aligned}$$



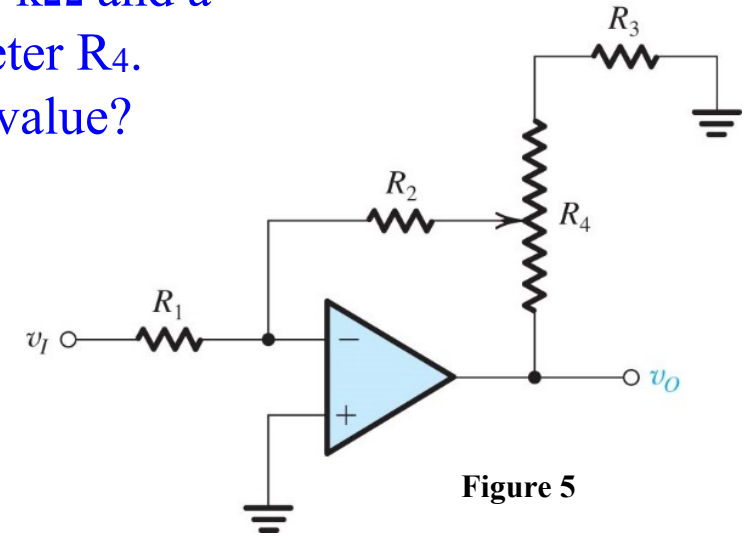


Figure 5

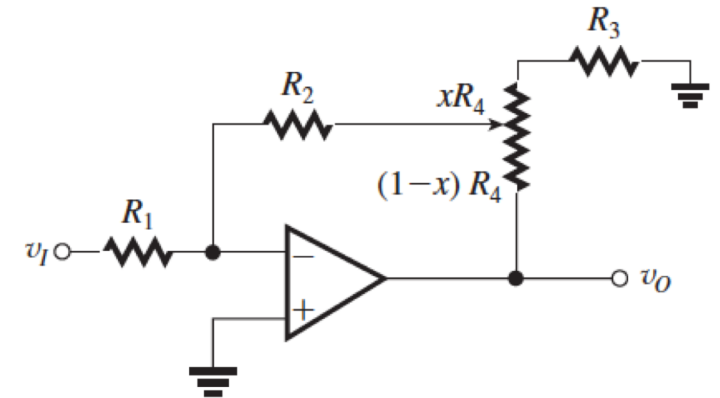

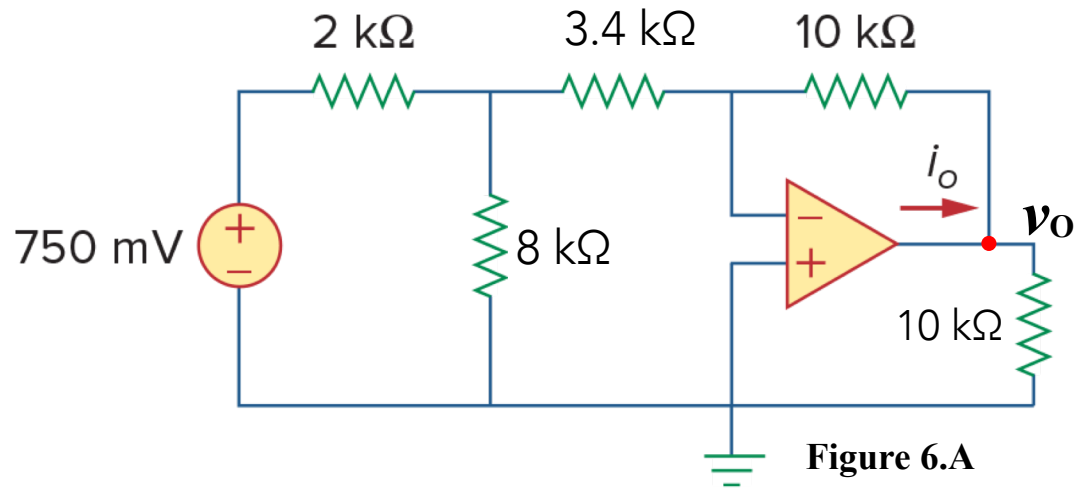6. (20%) Derive v_o and i_o in the circuit of Figure 6.A and 6.B.




$$V_{Th} = 750 \times \frac{8}{2 + 8} = 600(mV)$$

$$R_{Th} = 2k \parallel 8k = 1.6(k\Omega)$$

$$\begin{aligned} V_o &= -\frac{10}{R_{Th} + 3.4} \times V_{Th} \\ &= -\frac{10}{1.6 + 3.4} \times 600 \\ &= -1200(mV) = -1.2(V) \end{aligned}$$
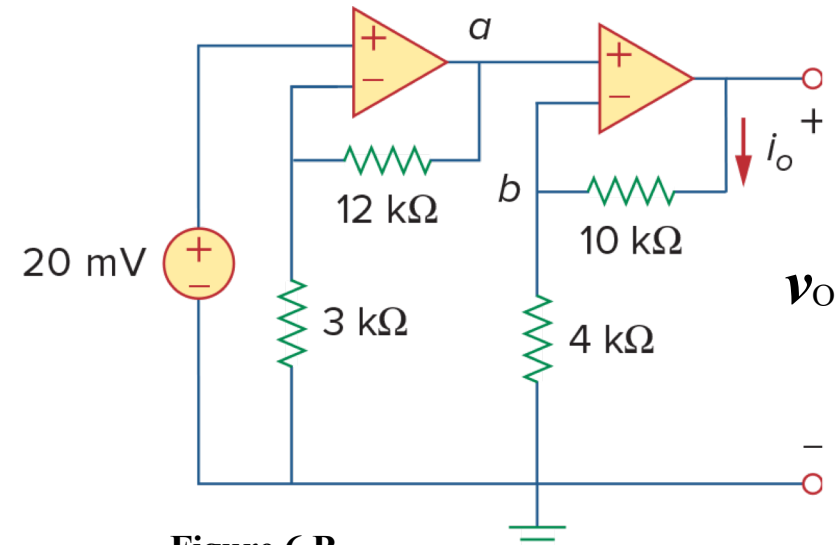
$$i_o = \frac{V_o}{10k} + \frac{V_o}{10k} = -0.24(mA) = -240(\mu A)$$



$$v_a = \left(1 + \frac{12}{3}\right) (20) = 100 \text{ mV}$$

$$v_o = \left(1 + \frac{10}{4}\right) v_a = (1 + 2.5)100 = 350 \text{ mV}$$

$$i_o = \frac{v_o - v_b}{10} \text{ mA}$$

$$v_b = v_a = 100 \text{ mV}$$

$$i_o = \frac{(350 - 100) \times 10^{-3}}{10 \times 10^3} = 25 \mu A$$

7. (20%) Derive v_o in Fig. 7.A and voltage gain $\frac{v_o}{v_i}$ in Fig 7.B for the OP Amp circuits

$$\begin{aligned} V_2 &= 15.5 \times \frac{60 \parallel (20 + 80)}{40 + 60 \parallel (20 + 80)} \\ &= 15.5 \times \frac{37.5}{40 + 37.5} \\ &= 7.5 \text{ (mV)} \end{aligned}$$

$$V_{80k} = V_2 \times \frac{80}{20 + 80} = 7.5 \times 0.8 = 6 \text{ (mV)}$$

$$\begin{aligned} \frac{15.5 - V_1}{10k} &= \frac{V_1}{30k} + \frac{V_1 - V_{80k}}{20k} \\ 93 - 6V_1 &= 2V_1 + 3V_1 - 18 \\ 11V_1 &= 111 \\ \Rightarrow V_1 &= 10.0909 \text{ (mV)} \end{aligned}$$

$$\begin{aligned} V_o &= (V_2 - V_1) \times \frac{80k}{20k} \\ &= (7.5 - 10.0909) \times 4 \\ &= -10.3636 \text{ (mV)} \end{aligned}$$

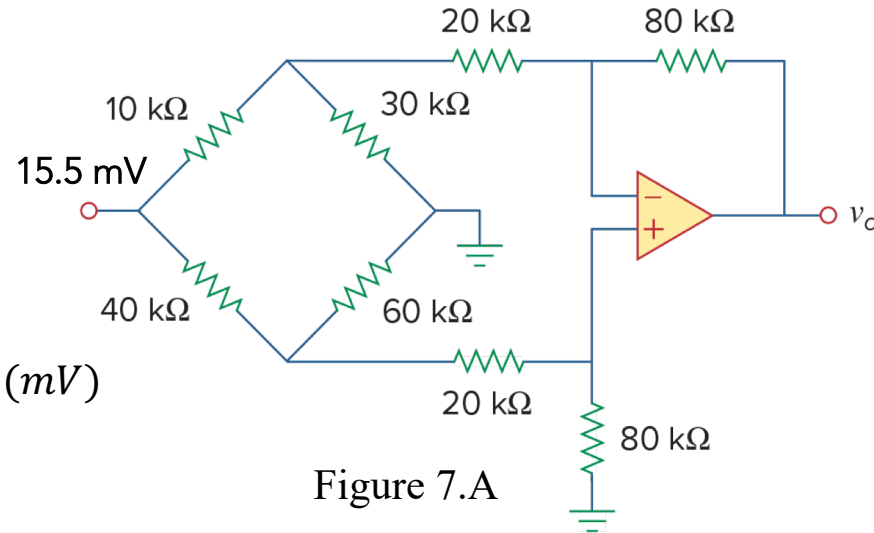


Figure 7.A

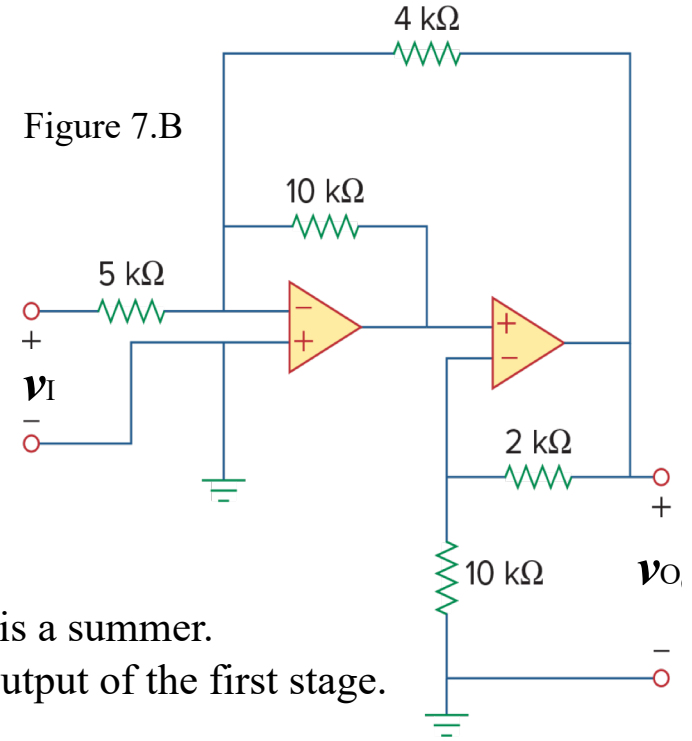
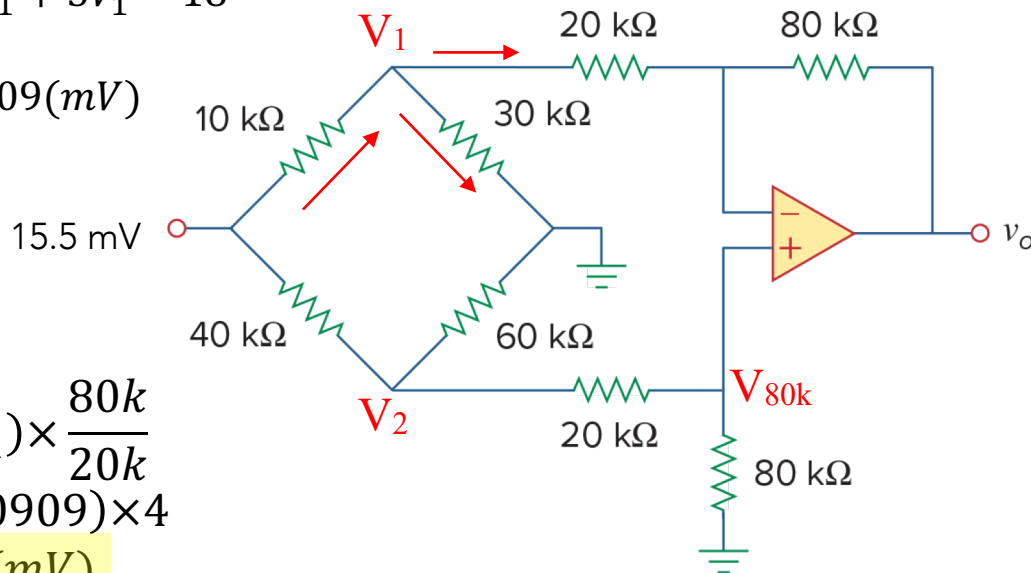


Figure 7.B

The first stage is a summer.
Let V_1 be the output of the first stage.

$$v_1 = -\frac{10}{5}v_i - \frac{10}{4}v_o \longrightarrow v_1 = -2v_i - 2.5v_o \quad (1)$$

By voltage division,

$$v_1 = \frac{10}{10+2}v_o = \frac{5}{6}v_o \quad (2)$$

Combining (1) and (2),

$$\frac{5}{6}v_o = -2v_i - 2.5v_o \longrightarrow \frac{10}{3}v_o = -2v_i$$

$$\frac{v_o}{v_i} = -6/10 = \underline{-0.6}$$

8. (25%) Figure 8 shows a circuit that is known as a first-order, low-pass active filter.

a. (10%) Derive the transfer function $\frac{V_o}{V_i}$ (in s and $j\omega$), and show its dc gain and 3-dB frequency ω_b .

b. (10%) Design the circuit (R_1 , R_2 and C) to obtain an input resistance of 10 k Ω , a dc gain of 40 dB, and a 3-dB frequency (f_b) of 1 kHz. What is its unity frequency ($f_t = ?$)?

c. (5%) Construct the Bode plot (frequency response of $|V_o/V_i|$ (dB)) with the design.

$$\text{Let } Z_2 = R_2 \parallel \frac{1}{sC} \text{ and } Z_1 = R_1$$

$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{Y_1}{Y_2} = -\frac{1/R_1}{\frac{1}{R_2} + sC}$$

$$= -\frac{(R_2/R_1)}{1 + sCR_2} \quad 5\%$$

This function is of the STC low-pass type, having

a dc gain of $-\frac{R_2}{R_1}$ and a 3-dB frequency

5%

$$\omega_0 = \frac{1}{CR_2} \quad 5\%$$

$$R_{in} = R_1 = 10 \text{ k}\Omega \quad 5\%$$

$$\text{dc gain} = 40 \text{ dB} = 100$$

$$\therefore 100 = \frac{R_2}{R_1} \Rightarrow R_2 = 100R_1 = 1 \text{ M}\Omega$$

5%

3-dB frequency at 1 kHz

$$\therefore \omega_0 = 2\pi \times 1 \times 10^3 = \frac{1}{CR_2}$$

$$C = \frac{1}{2\pi \times 1 \times 10^3 \times 10^6} = 0.16 \text{ nF}$$

5%


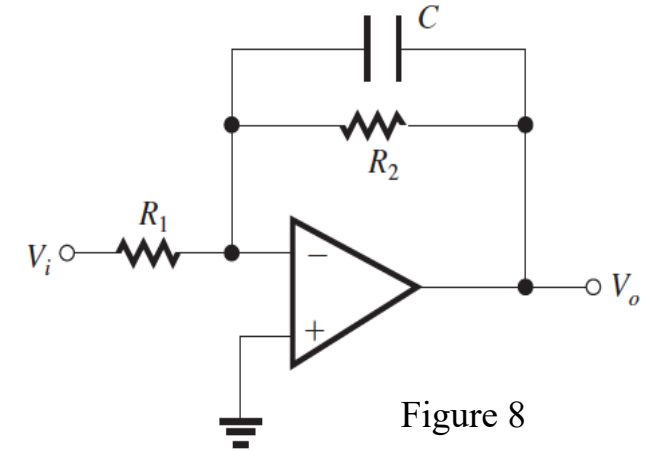


Figure 8

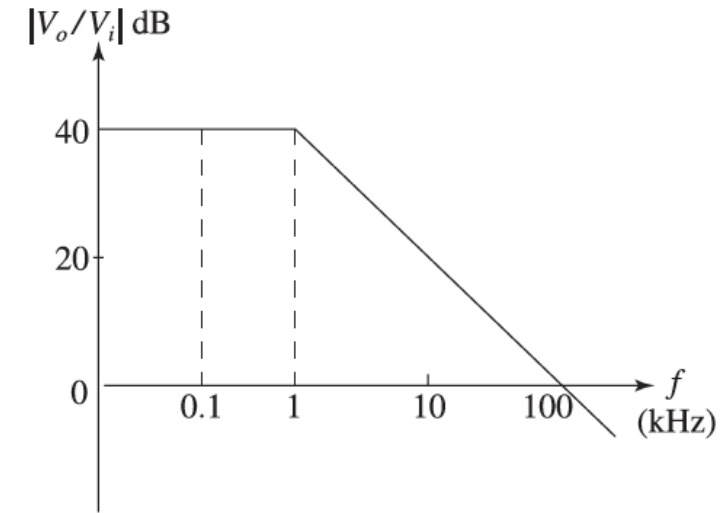

From the Bode plot shown in previous column, the unity-gain frequency is 100 kHz.