

1. (15%) Find the charge q flowing through a device if the current i is:

a. $i(t) = 5 \text{ (A)}, q(0) = 0$

$$q(t) = \int i(t)dt + q(0) = 5t \text{ (C)}$$

b. $i(t) = (2t + 1) \text{ (}\mu\text{A)}, q(0) = 1 \text{ (mC)}$

$$q(t) = t^2 + t + 1000 \text{ (}\mu\text{C)}$$

c. $i(t) = 10 \cdot \cos(10t + \pi/6) \text{ (}\mu\text{A)}, q(0) = 1 \text{ (}\mu\text{C)}$

$$q(t) = \sin(10t + \pi/6) + 0.5 \text{ (}\mu\text{C)}$$

2. (15%) Find the current i flowing through a device if the charge q is:

a. $q(t) = (3t + 8) \text{ (mC)}$

b. $q(t) = (e^{-3t} - 5e^{-5t}) \text{ (nC)}$

c. $q(t) = 8 \cdot \sin(60\pi t) \text{ (pC)}$



$$\text{a. } i = \frac{dq}{dt} = \frac{d(3t+8)}{dt} = 3 \text{ (mA)}$$

$$\text{b. } i = \frac{dq}{dt} = \frac{d(e^{-3t} - 5e^{-5t})}{dt} = -3e^{-3t} + 25e^{-5t} \text{ (nA)}$$

$$\text{b. } i = \frac{dq}{dt} = \frac{d(8 \cdot \sin(60\pi t))}{dt} = 480\pi \cdot \cos(60\pi t) \text{ (pA)}$$

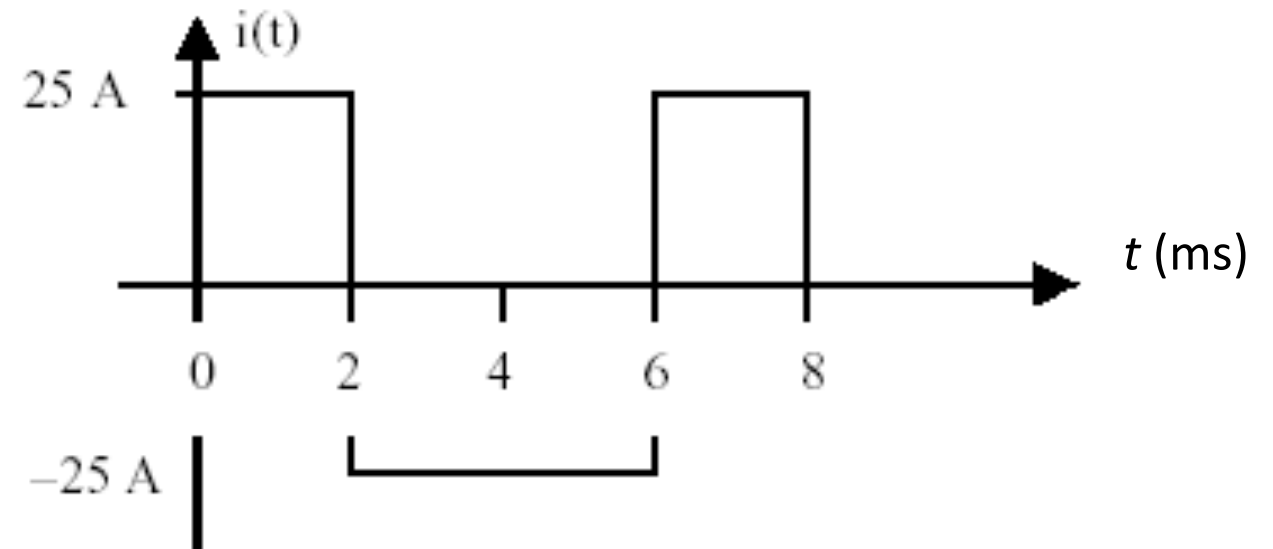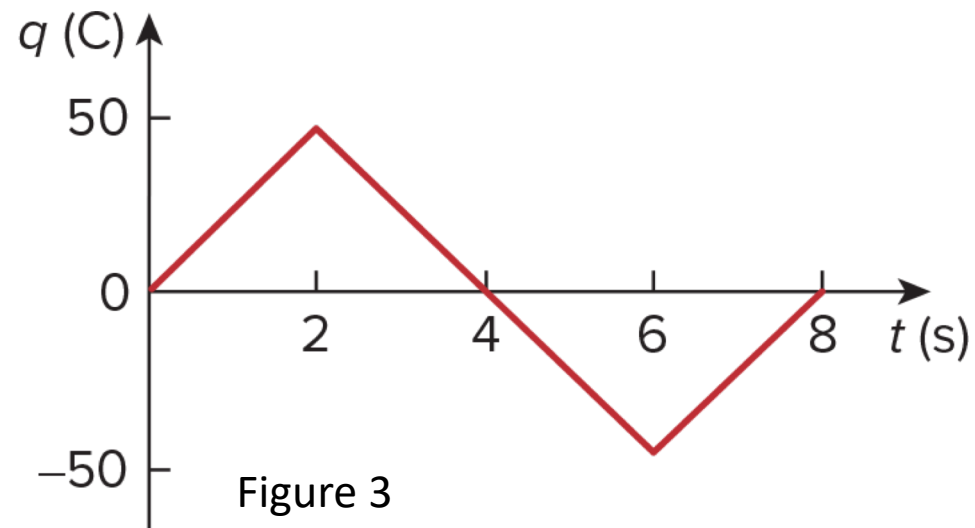3. (10%) The charge q flowing in a wire is plotted in Fig 2. **Sketch** the corresponding current.




$$i = \frac{dq}{dt} = \begin{cases} 25\text{A}, & 0 < t < 2 \\ -25\text{A}, & 2 < t < 6 \\ 25\text{A}, & 6 < t < 8 \end{cases}$$



4. (25%) Figure 3 shows the current through and the voltage across an element.

(a) (15%) Derive the current $i(t)$, voltage $v(t)$, and power delivered to the element $p(t)$ as a function of time (t) in the interval of $0 < t < 4$ (s)

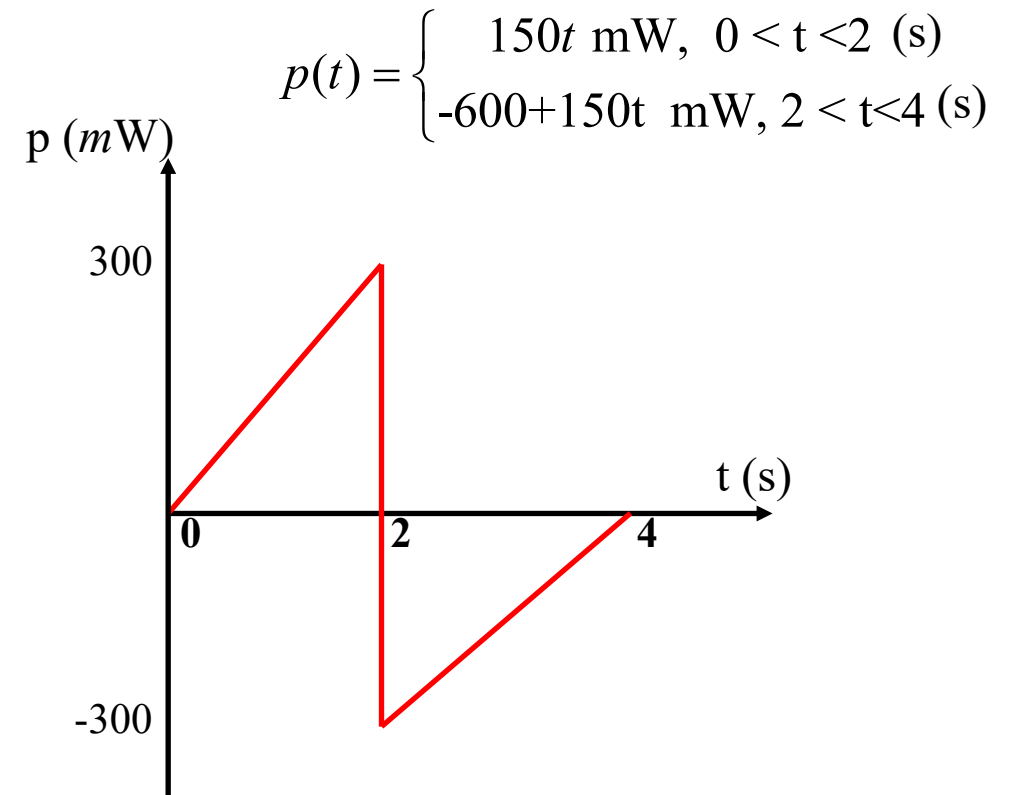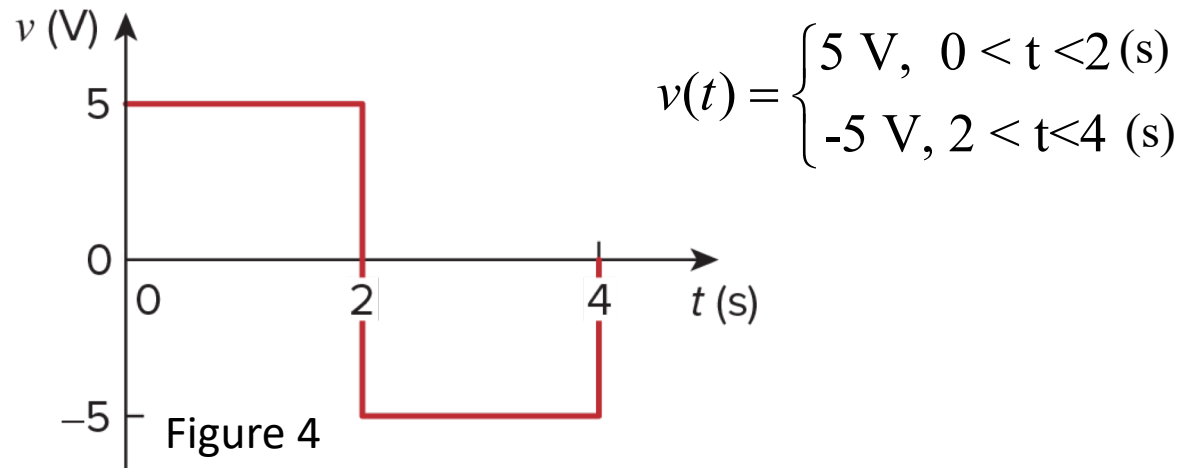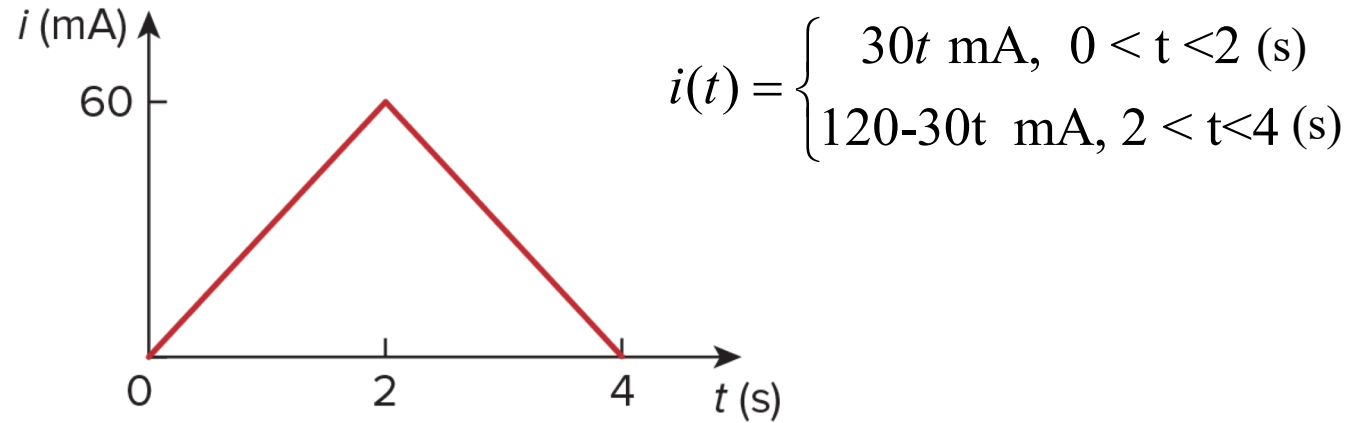(b) (10%) Sketch the power $p(t)$ delivered to the element for $t > 0$.



5. The current through an element is shown in Fig. 5. Determine the total charge that passed through the element at: (a) $t = 1$ s ; (b) $t = 3$ s ; (c) $t = 5$ s

(a) $t = 1$ s


$$q = \int i dt = \int_0^1 10 dt = \underline{10 \text{ C}}$$

(b) $t = 3$ s

$$\begin{aligned} q &= \int_0^3 i dt = 10 \times 1 + \left(10 - \frac{5 \times 1}{2} \right) + 5 \times 1 \\ &= 15 + 7.5 + 5 = \underline{22.5 \text{ C}} \end{aligned}$$

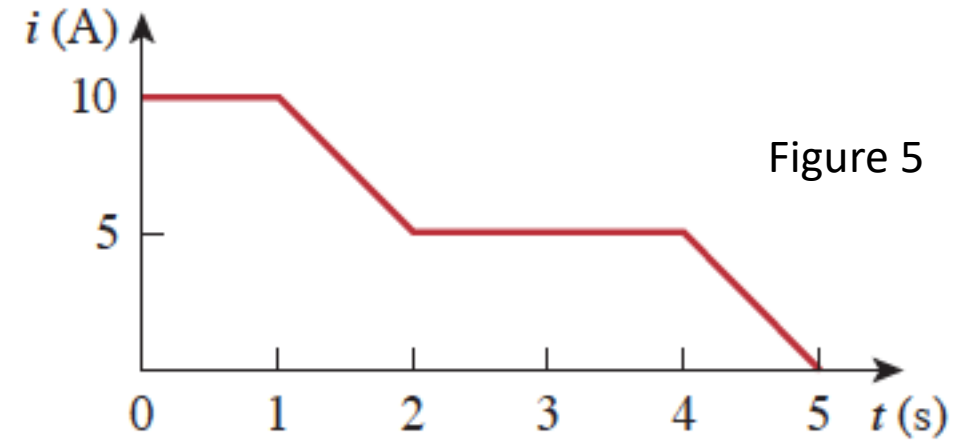(c) $t = 5$ s

$$q = \int_0^5 i dt = 10 + 10 + 10 = \underline{30 \text{ C}}$$



6. (25%) Find the power absorbed by each of the elements in Fig. 6.


$$p_1 = 30 \times (-10) = \mathbf{-300 \text{ (W)}}$$

$$p_2 = 10 \times (10) = \mathbf{100 \text{ (W)}}$$

$$p_3 = 20 \times (14) = \mathbf{280 \text{ (W)}}$$

$$p_4 = 8 \times (-4) = \mathbf{-32 \text{ (W)}}$$
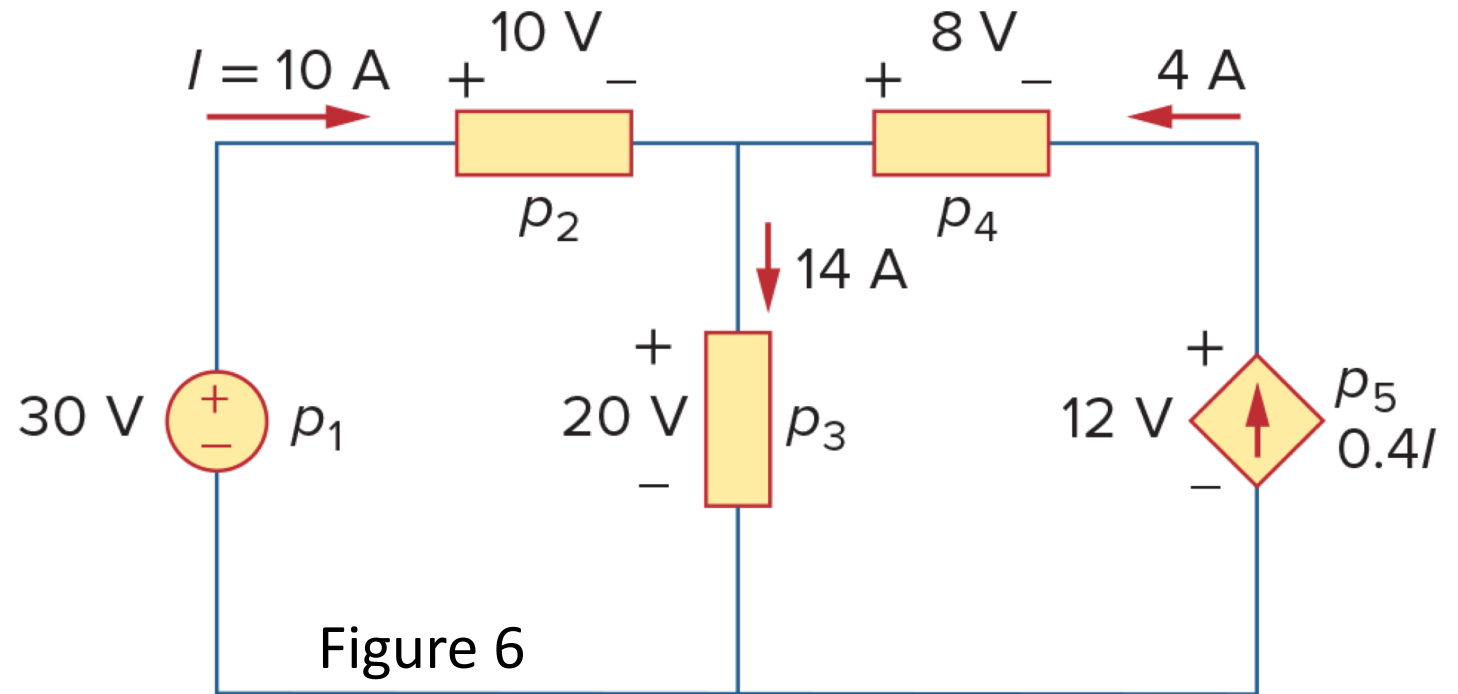
$$p_5 = 12 \times (-4) = \mathbf{-48 \text{ (W)}}$$



7. Find V_o and the power absorbed by each element in the circuit of Fig. 7.


$$p_{30 \text{ volt source}} = 30 \times (-6) = -180 \text{ W}$$

$$p_{12 \text{ volt element}} = 12 \times 6 = 72 \text{ W}$$

$$p_{28 \text{ volt element with 2 amps flowing through it}} = 28 \times 2 = 56 \text{ W}$$

$$p_{28 \text{ volt element with 1 amp flowing through it}} = 28 \times 1 = 28 \text{ W}$$
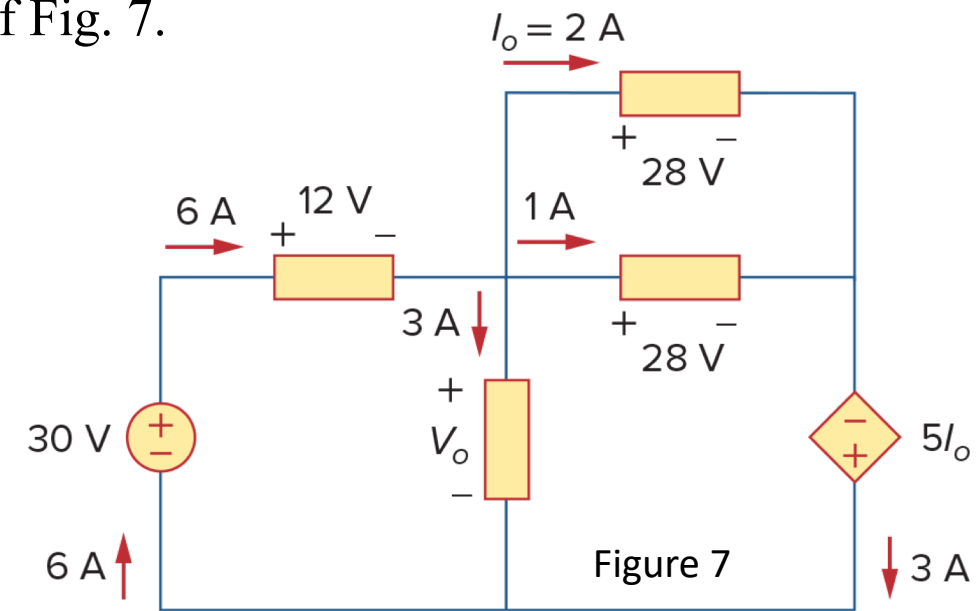
$$p_{\text{the } 5I_o \text{ dependent source}} = 5 \times 2 \times (-3) = -30 \text{ W}$$



Since the total power absorbed by all the elements in the circuit must equal zero,
or $0 = -180 + 72 + 56 + 28 - 30 + p_{\text{into the element with } V_o}$ or

$$p_{\text{into the element with } V_o} = 180 - 72 - 56 - 28 + 30 = 54 \text{ W}$$

Since $p_{\text{into the element with } V_o} = V_o \times 3 = 54 \text{ W}$ or $V_o = 18 \text{ V}$.