



ELECTRICAL ENGINEERING

FUNDAMENTALS I LAB

Laboratory 6

Input/Output Resistance and Δ -Y Conversion

Instructor

林賢龍 Prof. Shyan-Lung Lin

Equipment

- DC Power Supply
- Digital Multimeter
- Components

- $1.1\text{ k}\Omega \times 2$, $2.2\text{ k}\Omega \times 2$, $3.3\text{ k}\Omega \times 2$,
Variable Resistor R_T $\times 1$
- $1\text{ k}\Omega \times 2$, $3\text{ k}\Omega \times 4$, $6\text{ k}\Omega \times 1$





Learning Objectives

- To learn to use the “proportional measurement method” for input and output resistance measurement
- To learn the experimental measurement for Wheatstone bridge and the analysis and application of Δ -Y Conversion

Background

Input/Output Resistance Measurement By Definition

■ Input Resistance Measurement




- Measure the current I_i flow into the circuit, and the voltage V_i across the circuit.

- $R_{in} = V_i / I_i$

■ Output Resistance Measurement

- Turn off the voltage source ($V_s=0$), and leave R_L open
- Measure output current I_X & output voltage V_X .

- $R_{out} = V_X / I_X$

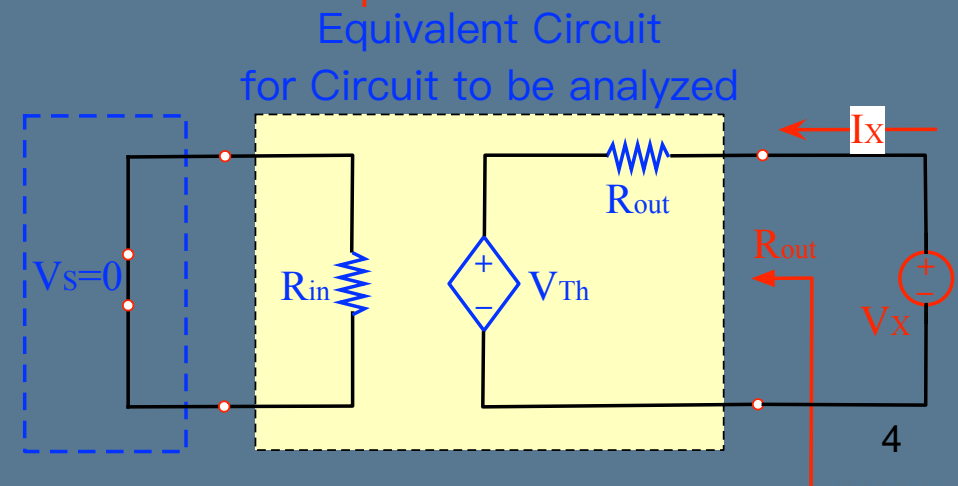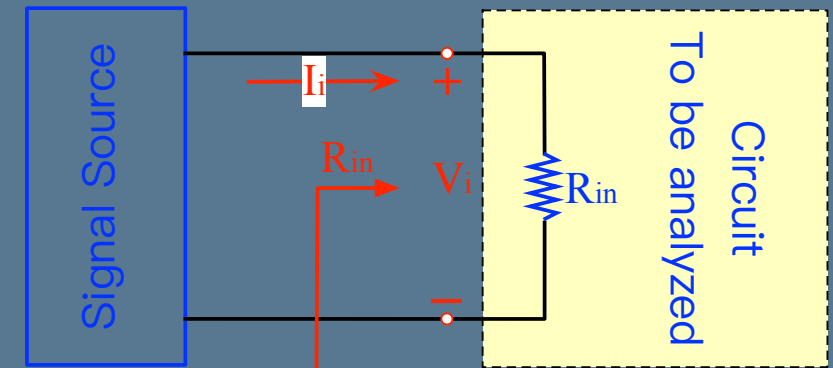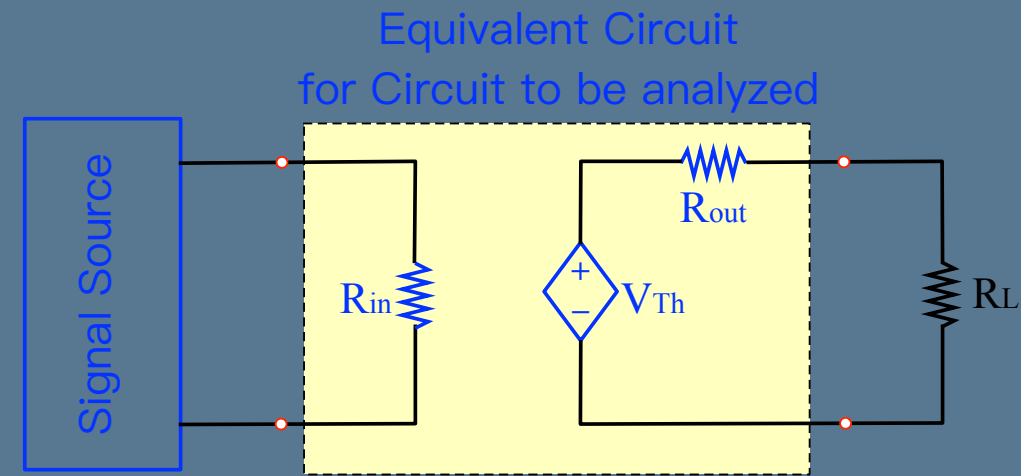



Background

Input/Output Resistance Measurement

Proportional Method

■ Input Resistance Measurement

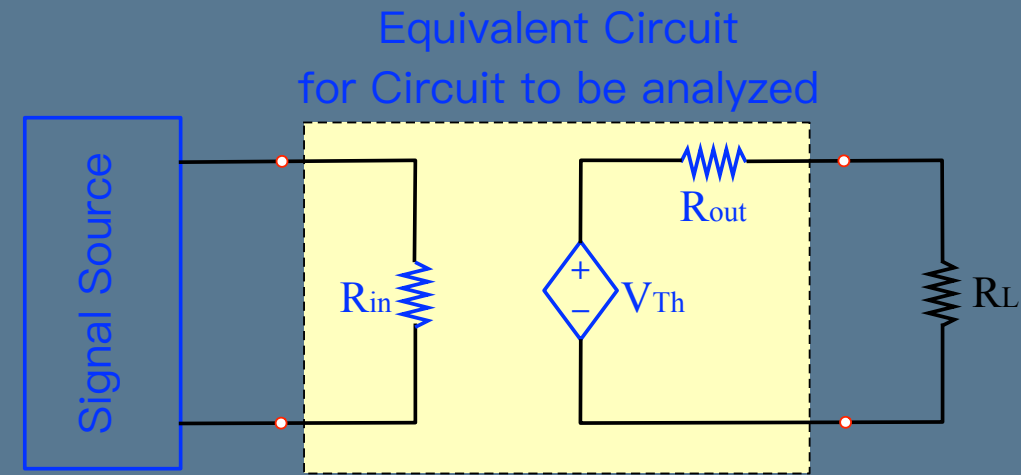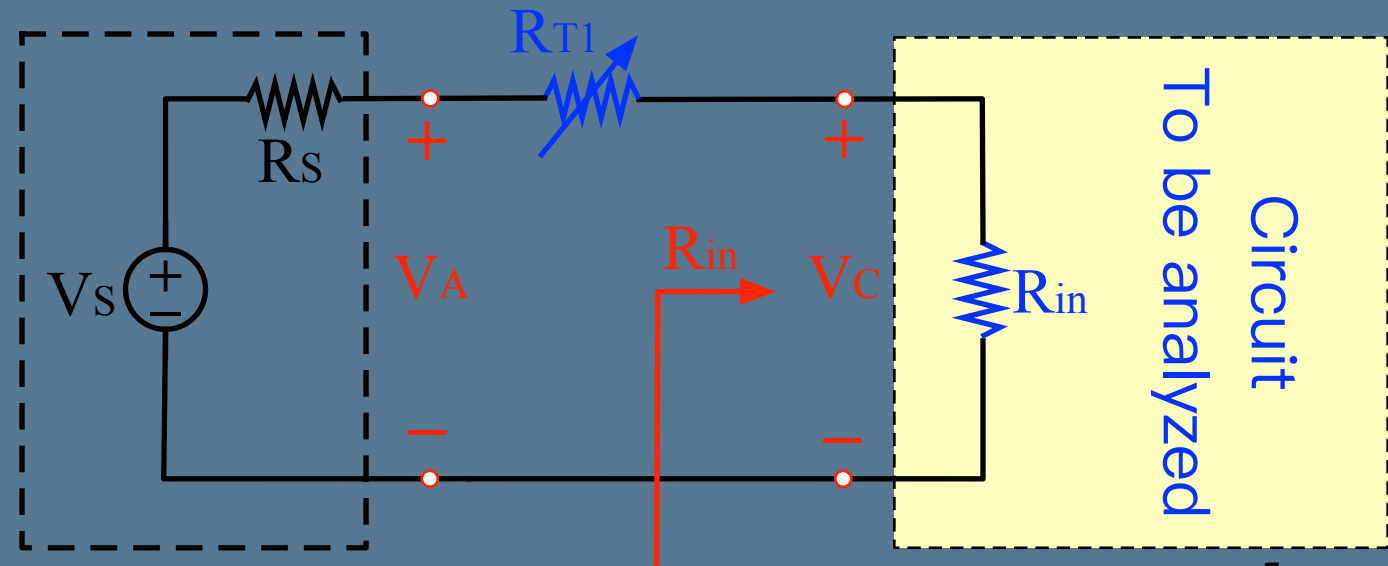- Connect a variable resistor (R_{T1}) in series
- Adjust R_{T1} until $V_C = \frac{1}{2} V_A$
- Measure $R_{T1} \Rightarrow R_{in} = R_{T1}$






Background

Input/Output Resistance Measurement

Proportional Method

■ Output Resistance Measurement

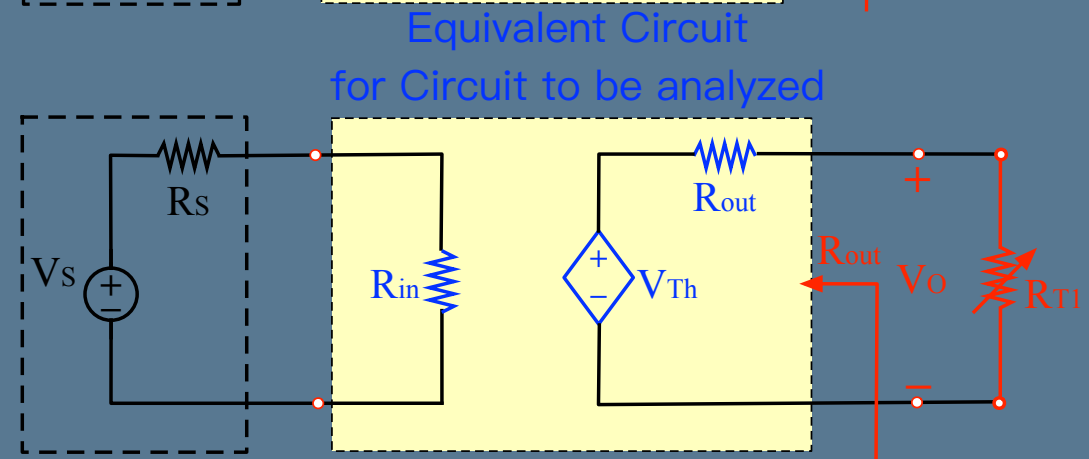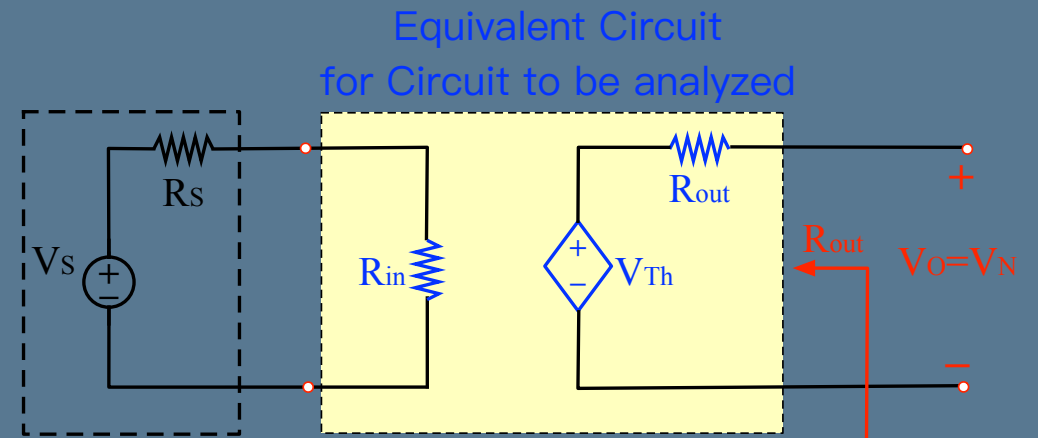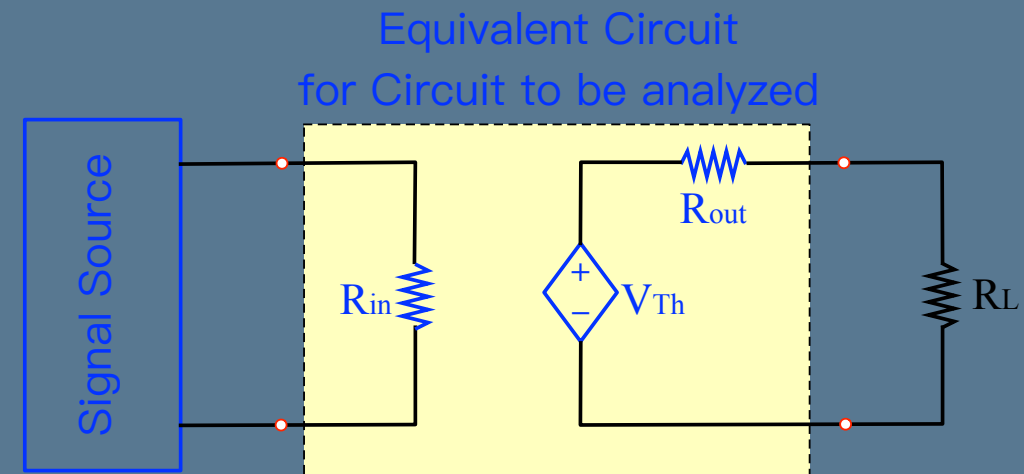
- With V_S applied, set $R_L = \infty$ (open circuit)
- measure output voltage V_O and set it to be V_N
- Connect R_{T1} in series as output load
- Adjust R_{T1} until $V_O = \frac{1}{2} V_N$
- Measure $R_{T1} \Rightarrow R_{out} = R_{T1}$



Background

Wheatstone bridge

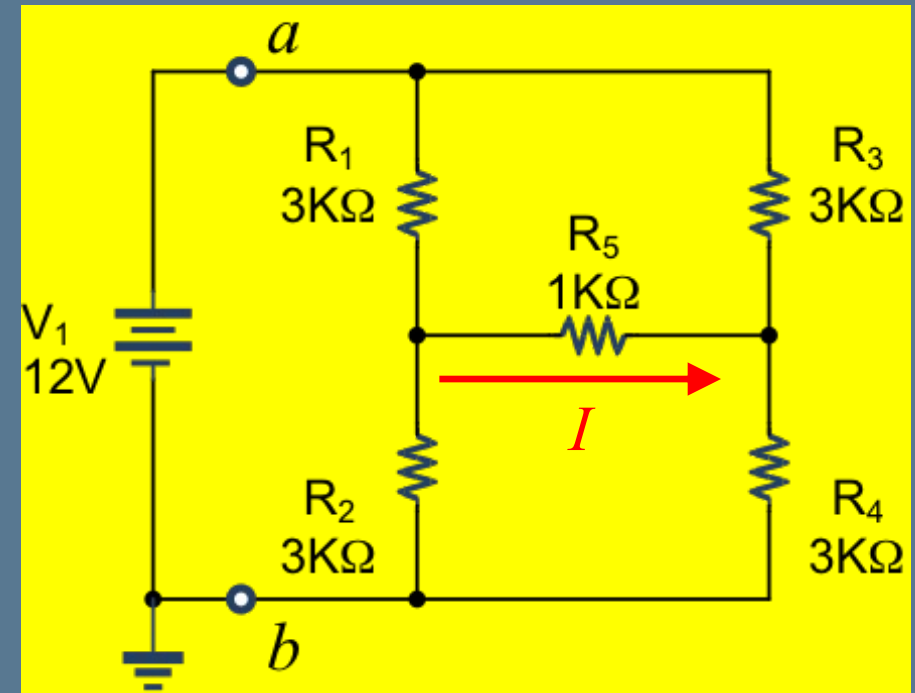
- The Wheatstone bridge circuit is often used in a sensor circuit application.
- Once the **unbalance** is occurred within the bridge, the **current**, whose amount depends on **the amplitude of the unbalance**, will flow through the branch that connecting the bridge.



Background

Δ -Y Conversion
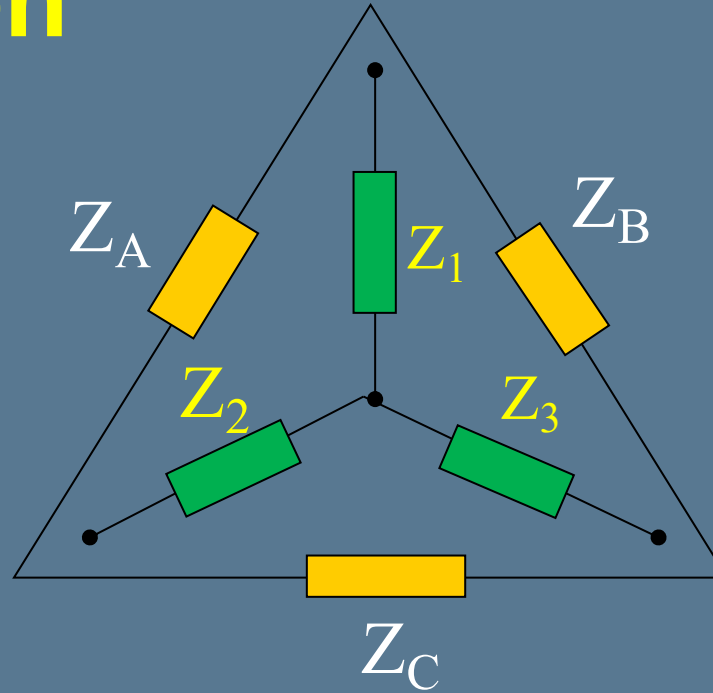
$$\left\{ \begin{array}{l} Z_1 = \frac{Z_A \cdot Z_B}{Z_A + Z_B + Z_C} \\ Z_2 = \frac{Z_A \cdot Z_C}{Z_A + Z_B + Z_C} \\ Z_3 = \frac{Z_B \cdot Z_C}{Z_A + Z_B + Z_C} \end{array} \right.$$



$$\left\{ \begin{array}{l} Z_A = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_3} \\ Z_B = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_2} \\ Z_C = \frac{Z_1 \cdot Z_2 + Z_2 \cdot Z_3 + Z_3 \cdot Z_1}{Z_1} \end{array} \right.$$



Experiments

Experiment 6

Input/Output Resistance Measurement & Δ -Y Conversion

- **Experiment 6.a**
Input/Output Resistance Measurement
- **Experiment 6.b**
 Δ -Y Conversion


Experiment 6.a

Input/Output Resistance Measurement

6.a.1 Input Resistance

- Determine the input resistance R_{in} of the circuit with **Proportional Method**
- Determine the input resistance R_{in} with **direct measurement**
- Calculate the input resistance R_{in} of by **theorem**
- Compare the results with % error

$$\begin{cases} R_1 = 3.3 \text{ k}\Omega \\ R_2 = 3.3 \text{ k}\Omega \\ R_3 = 2.2 \text{ k}\Omega \\ R_4 = 2.2 \text{ k}\Omega \\ R_5 = 1.1 \text{ k}\Omega \\ R_6 = 1.1 \text{ k}\Omega \end{cases}$$

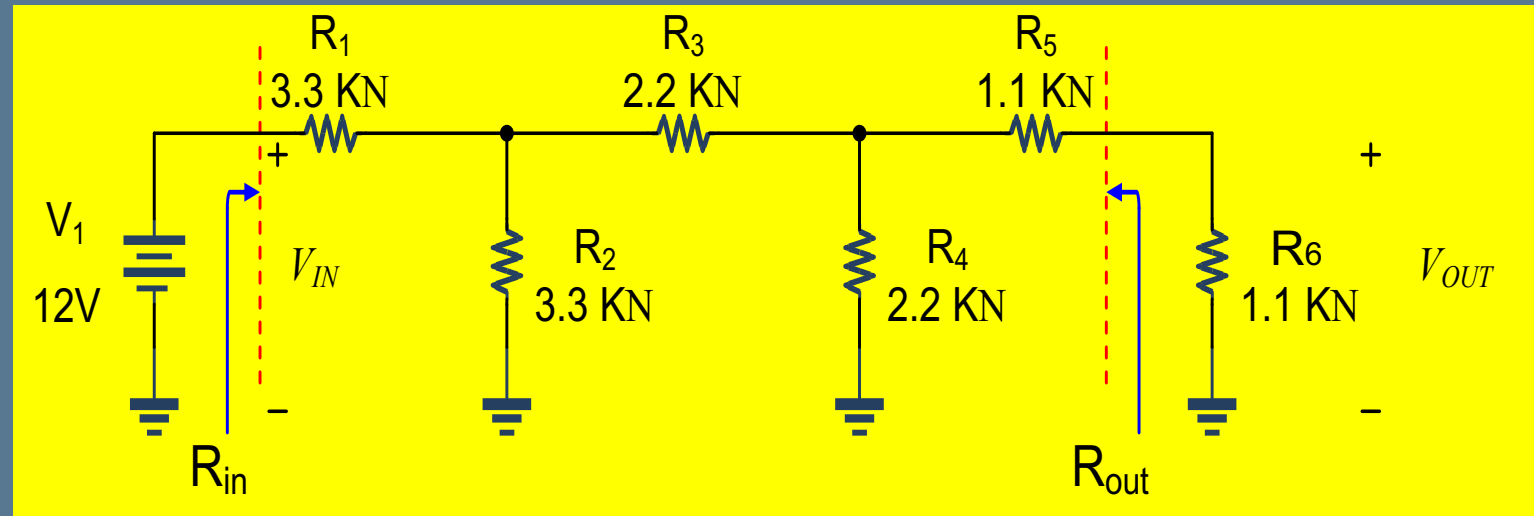


Experiment 6.a

Input/Output Resistance Measurement


6.a.2 Output Resistance

- Determine the output resistance R_{out} of the circuit with **Proportional Method**
- Determine the input resistance R_{in} with **direct measurement**
- Calculate the input resistance R_{in} of by **theorem**
- Compare the results with % error

$$\begin{cases} R_1 = 3.3 \text{ k}\Omega \\ R_2 = 3.3 \text{ k}\Omega \\ R_3 = 2.2 \text{ k}\Omega \\ R_4 = 2.2 \text{ k}\Omega \\ R_5 = 1.1 \text{ k}\Omega \\ R_6 = 1.1 \text{ k}\Omega \end{cases}$$

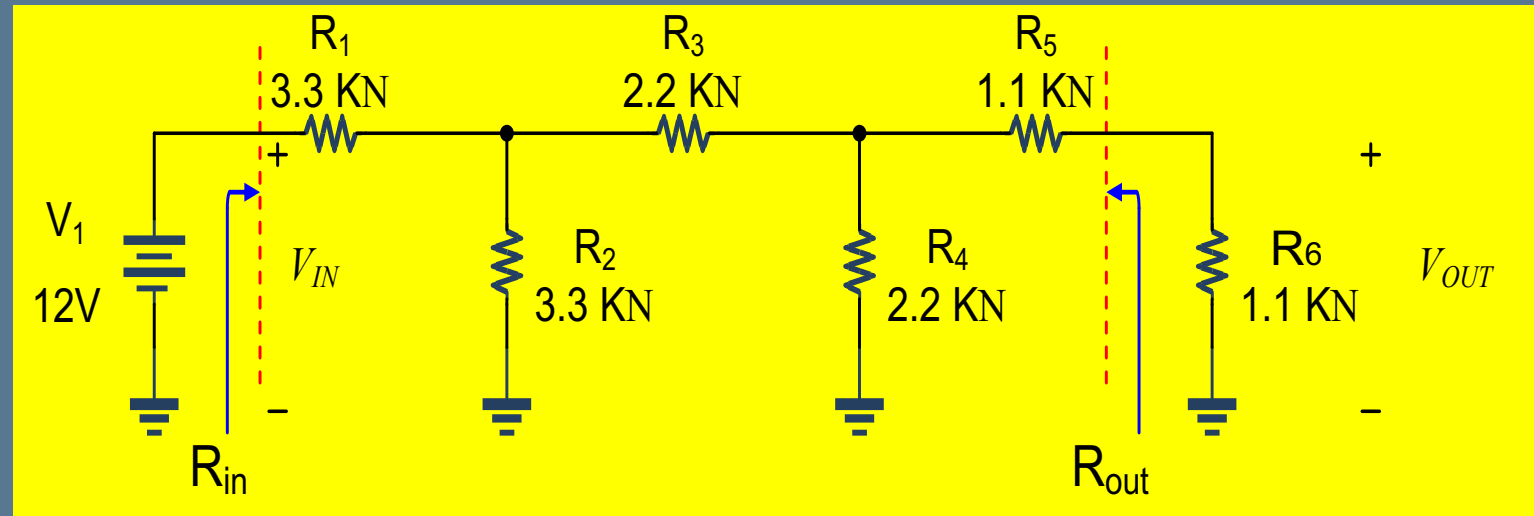


Experiment 6.b Δ -Y Conversion

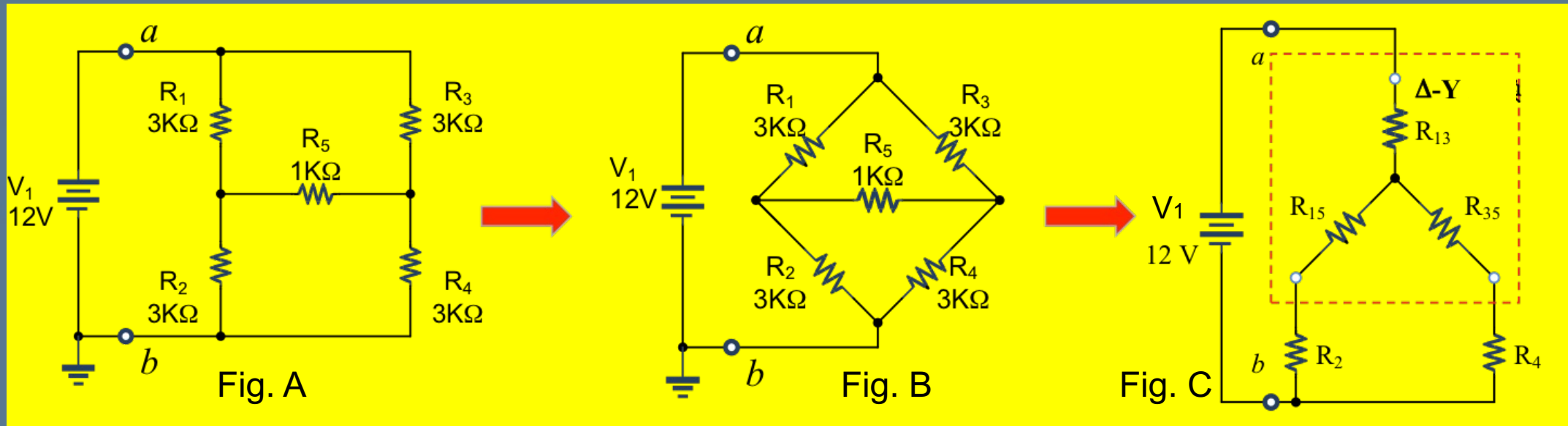

I. Based on Direct Measurement

1. Use the specified resistors to set up the circuit of Fig. A. $V_1=12$ V, $R_1 = R_2 = R_3 = R_4 = 3\text{k}\Omega$, $R_5 = 1\text{k}\Omega$
2. Measure the practical resistance of the resistors:
 $R_1 = \underline{\hspace{1cm}}$ $R_2 = \underline{\hspace{1cm}}$ $R_3 = \underline{\hspace{1cm}}$ $R_4 = \underline{\hspace{1cm}}$ $R_5 = \underline{\hspace{1cm}}$.
3. Measure the equivalent resistance of R_{ab} with DMM

Experiment 6.b Δ -Y Conversion

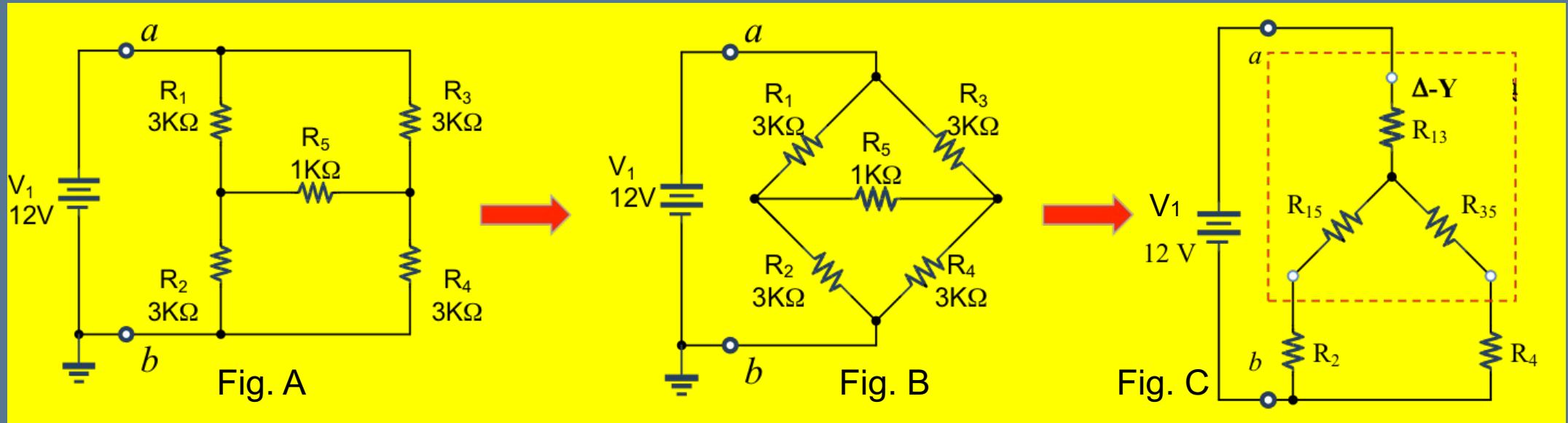

II. Based on Theoretical Calculation

1. Apply Δ -Y Conversion, convert Fig. A & B, into Fig. C.
2. Calculate the resistances of the equivalent circuit in Fig. C:

$$R_{13} = \underline{\hspace{2cm}} \quad R_{15} = \underline{\hspace{2cm}} \quad R_{35} = \underline{\hspace{2cm}}.$$


3. Calculate the equivalent resistance of R_{ab} with different R_4

a. $R_4 = 1 \text{ k}\Omega$, $R_{ab} = \underline{\hspace{2cm}};$

b. $R_4 = 3 \text{ k}\Omega$, $R_{ab} = \underline{\hspace{2cm}};$

c. $R_4 = 6 \text{ k}\Omega$, $R_{ab} = \underline{\hspace{2cm}}.$


Experiment 6.b Δ -Y Conversion

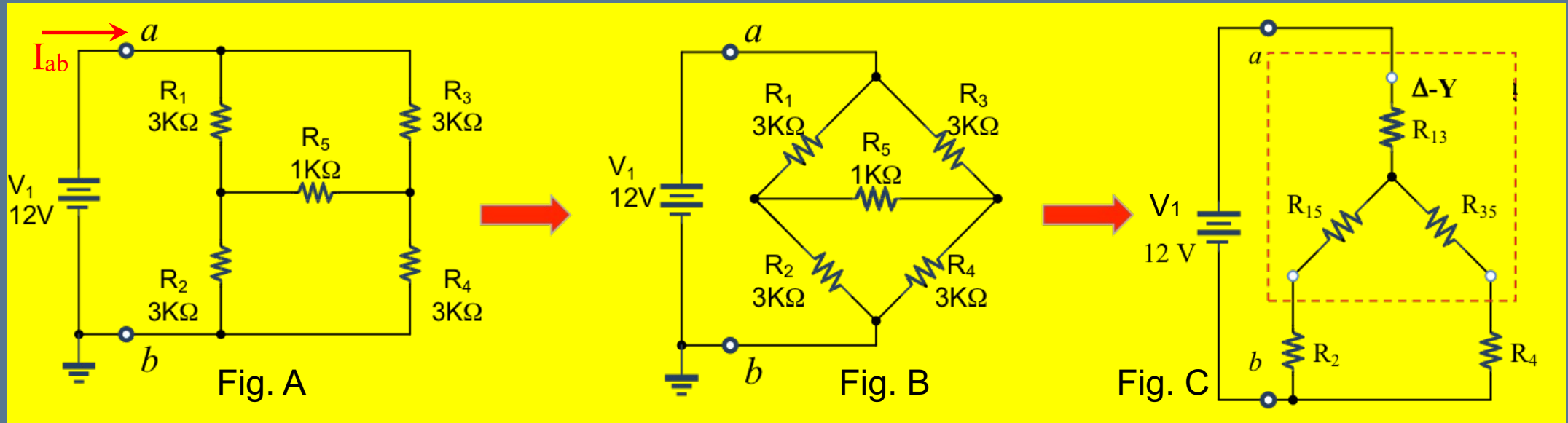

III. Based on Current-Voltage Measurement

1. Connect an Ammeter in series with node-**a** of Fig. A to measure the current I_{ab} based on different R_4 .
2. Based on the definition of $R_{ab} = V_1/I_{ab}$, calculate the resulted R_{ab}
 - a. $R_4 = 1 \text{ k}\Omega$, $I_{ab} =$ _____ ; $R_{ab} = V_1/I_{ab} =$ _____ ;
 - b. $R_4 = 3 \text{ k}\Omega$, $I_{ab} =$ _____ ; $R_{ab} = V_1/I_{ab} =$ _____ ;
 - c. $R_4 = 6 \text{ k}\Omega$, $I_{ab} =$ _____ ; $R_{ab} = V_1/I_{ab} =$ _____ .

Experiment 6.b Δ -Y Conversion

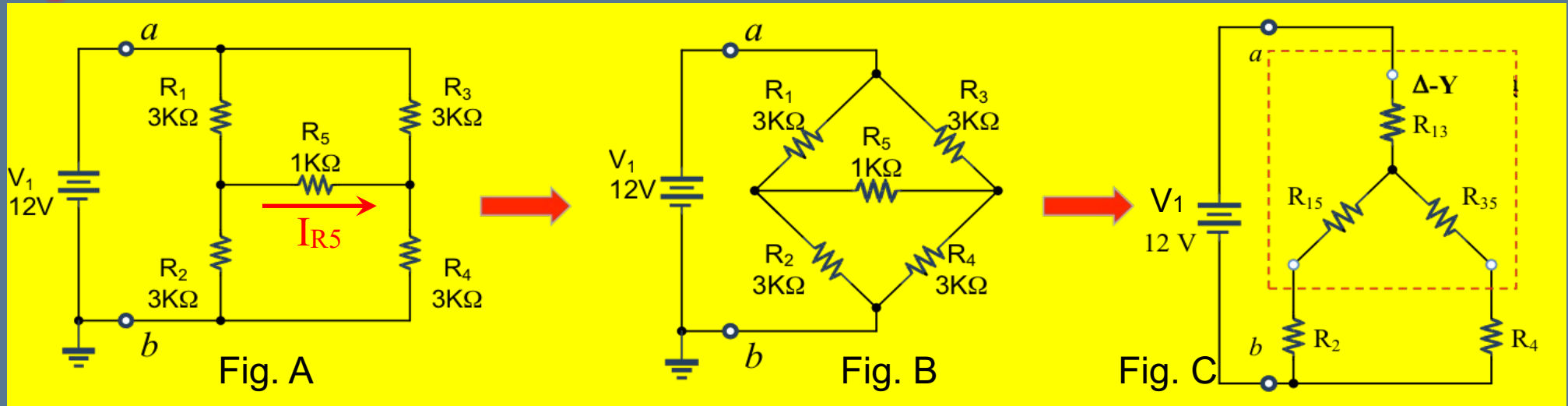

IV. Bridge Current Measurement

1. Connect an Ammeter in series with R_5 of Fig. A to measure the bridge current I_{R5} based on different R_4 .
 - a. $R_4 = 1\text{k}\Omega$, $I_{R5} =$ _____ ;
 - b. $R_4 = 3\text{k}\Omega$, $I_{R5} =$ _____ ;
 - c. $R_4 = 6\text{k}\Omega$, $I_{R5} =$ _____ .
2. Apply Thevenin's beyond R_5 and use the equivalent circuit to calculate for I_{R5} with different R_4 , and compare the results with Step 1 for % error.
3. Discuss your results of I~IV with tabulated data.