

Feng Chia University  
Electrical Engineering Fundamentals I Lab

Laboratory 11  
Diodes Circuit Applications Clipper and Clamper

Instructor: Prof. Shyan-Lung Lin

Student Name: 周嘉禾

Student ID: D1166506

Experiment Date: 22/02/2023


## I. Introduction

- Understand the circuit structure and function of the clipper circuits and clamper circuits.
- Understand the meaning of the voltage transfer characteristics (VTC).

## II. Materials

- DC Power Supply
- Waveform Generator
- Digital Oscilloscope
- Devices
  - Resistors:  $R = 20\text{ k}\Omega \times 1$   
Capacitors:  $C = 1\text{ }\mu\text{F} \times 1$   
Diode:  $D = 1\text{N4007} \times 1$

## III. Circuit diagram

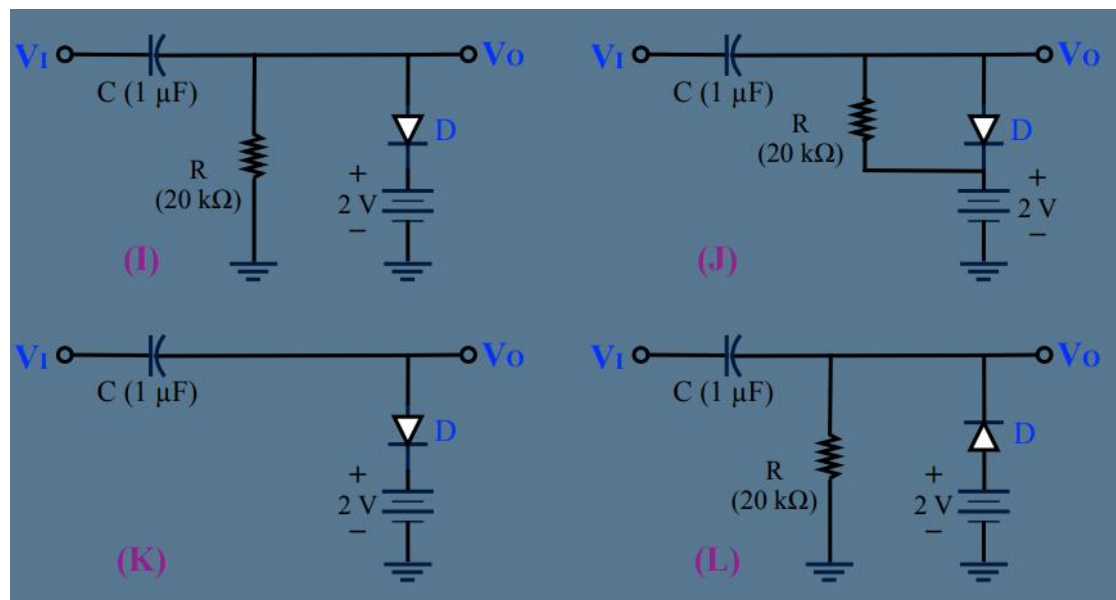

▲ Figure 1. Circuit of Experiment 11.c Clamper Circuits


## IV. Methods

Using Digital Oscilloscope to observe the wave through diode.


## V. Experiments data

None


VI. Results

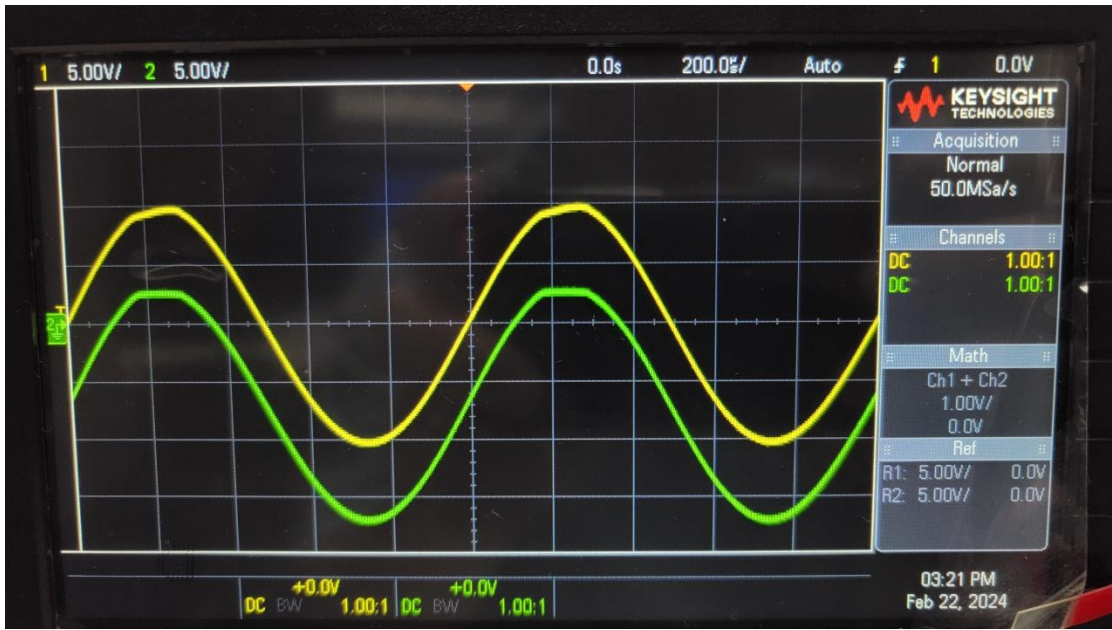

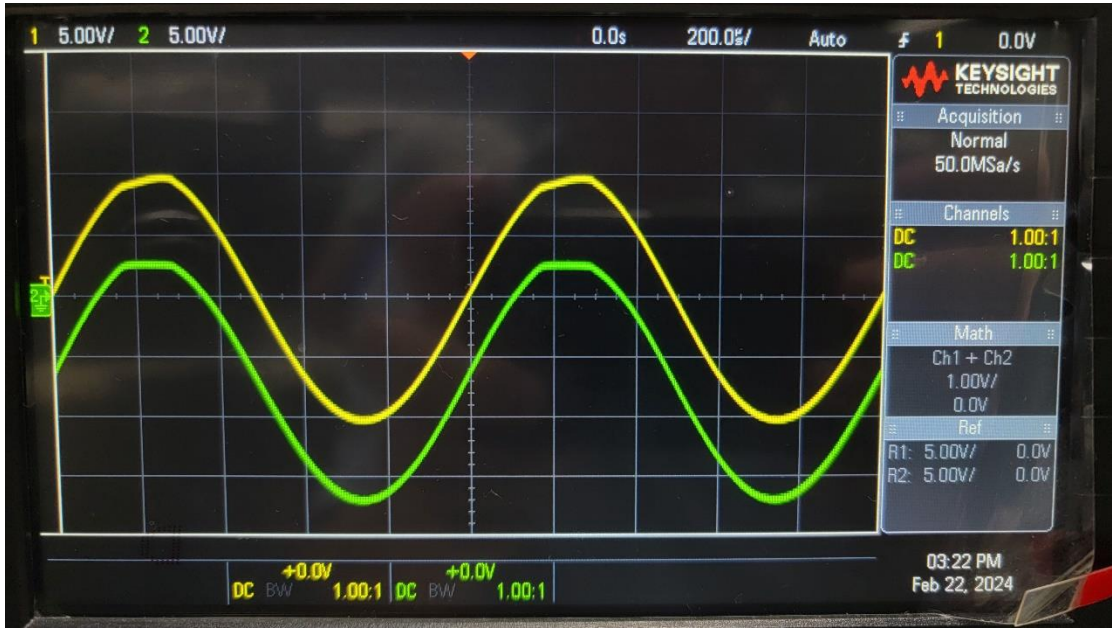
▲ Figure 2. Waveform comparisons of Experiment 11.c(I) with 1N4007



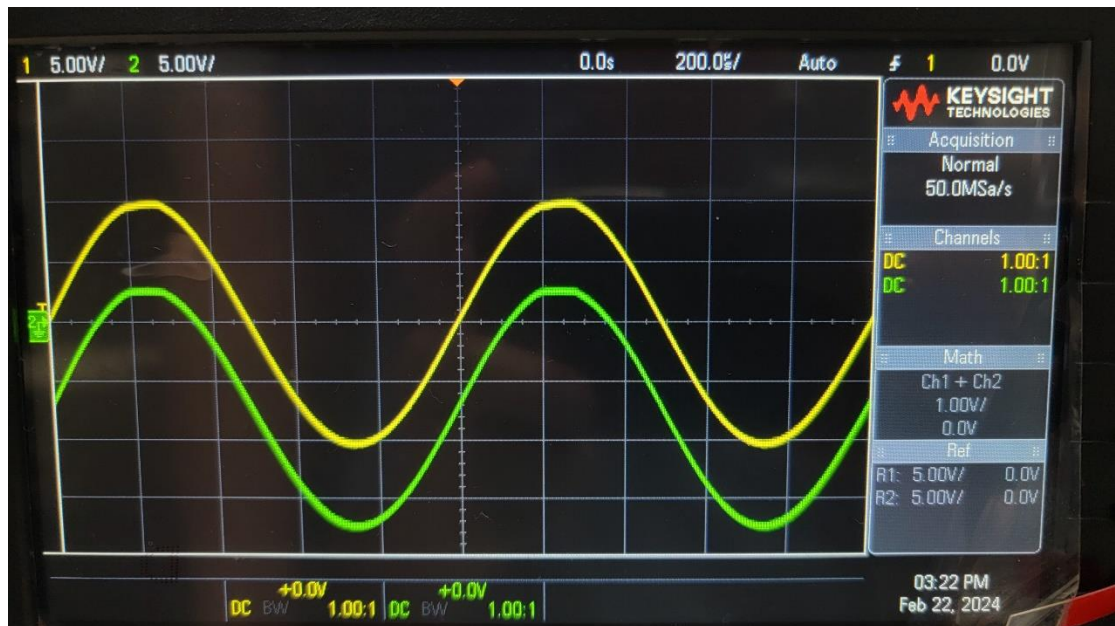▲ Figure 3. Waveform comparisons of Experiment 11.c(J) with 1N4007



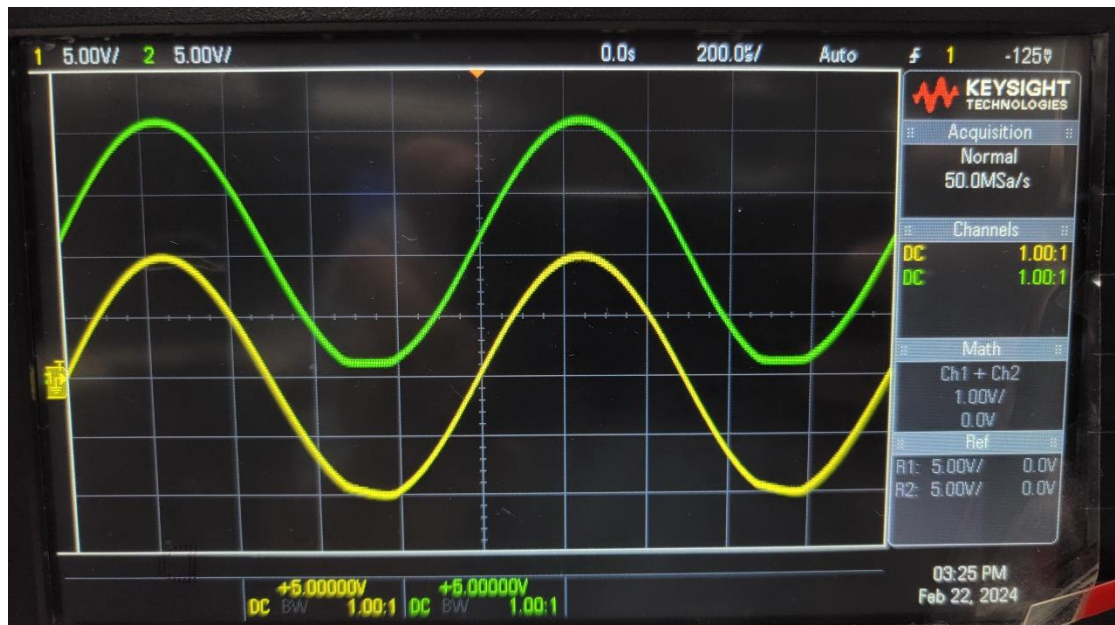▲ Figure 4. Waveform comparisons of Experiment 11.c(K) with 1N4007



▲ Figure 5. Waveform comparisons of Experiment 11.c(L) with 1N4007

## VII. Discussion

None

## VIII. Conclusion

Diode clipper and clamper circuits are wave-shaping circuits that modify the input signal waveform by using diodes, resistors, capacitors, and biasing voltages.