

1. (20%) Find i and V_o in the circuit of Fig. 1.

$$R_{eq1} = 30 // (50 + 10) = 20,$$

$$20 + R_{eq1} = 40,$$

$$60 // 20 = 15,$$

$$R_{eq2} = 80 + (25 + 60 // 20) // (20 + R_{eq1})$$

$$= 80 + (25 + 15) // 40$$

$$= 100 \, \Omega$$


$$i = 20/100 = 0.2 \, (A)$$

$$i_1 = i \times \frac{(25 + 60 // 20)}{(25 + 60 // 20) + (20 + R_{eq1})}$$


$$= 0.2 \times \frac{(25 + 15)}{(25 + 15) + (20 + 20)} = 0.1 \, (A)$$

$$i_o = i_1 \times \frac{30}{30 + (50 + 10)} = 0.1 \times \frac{30}{90} = \frac{0.1}{3} = 0.0333 \, (A)$$

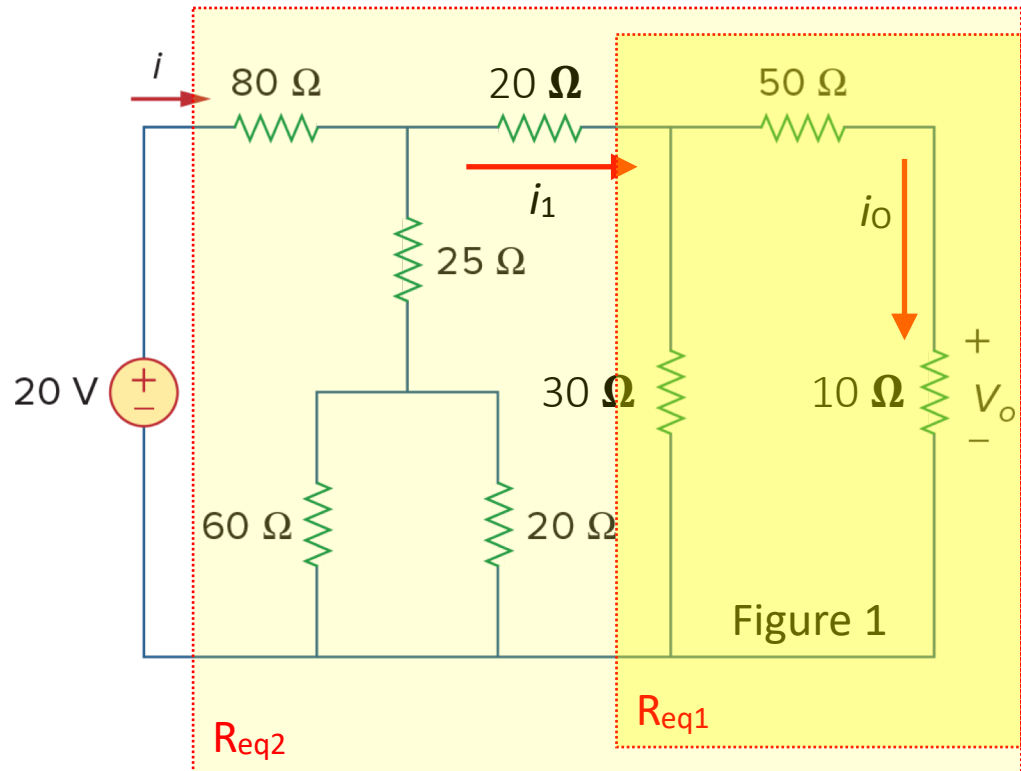
$$V_o = 10 \times i_o = \frac{1}{3} = 0.3333 \, (V)$$



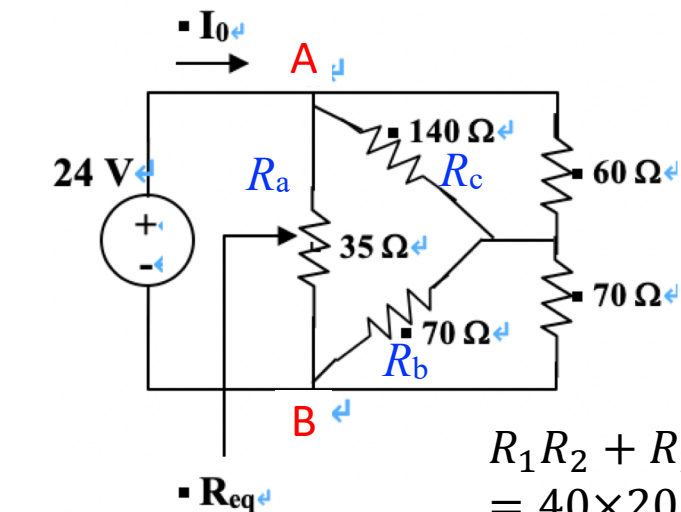2. (20%) Calculate I_o and V_1 in the circuit of Fig. 2.


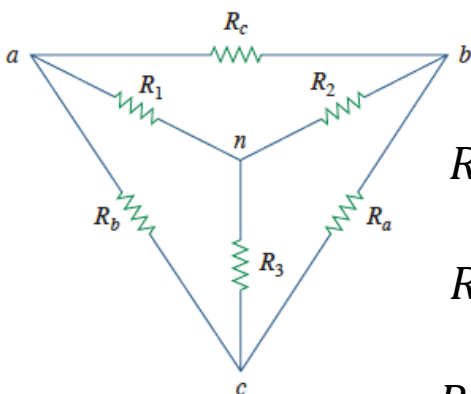
$$\begin{aligned}
 R_1 R_2 + R_2 R_3 + R_3 R_1 &= 40 \times 20 + 20 \times 10 + 10 \times 40 \\
 &= 1400(\Omega)
 \end{aligned}$$



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$


$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_a = \frac{1400}{R_1} = \frac{1400}{40} = 35(\Omega)$$

$$R_b = \frac{1400}{R_2} = \frac{1400}{20} = 70(\Omega)$$

$$R_c = \frac{1400}{R_3} = \frac{1400}{10} = 140(\Omega)$$
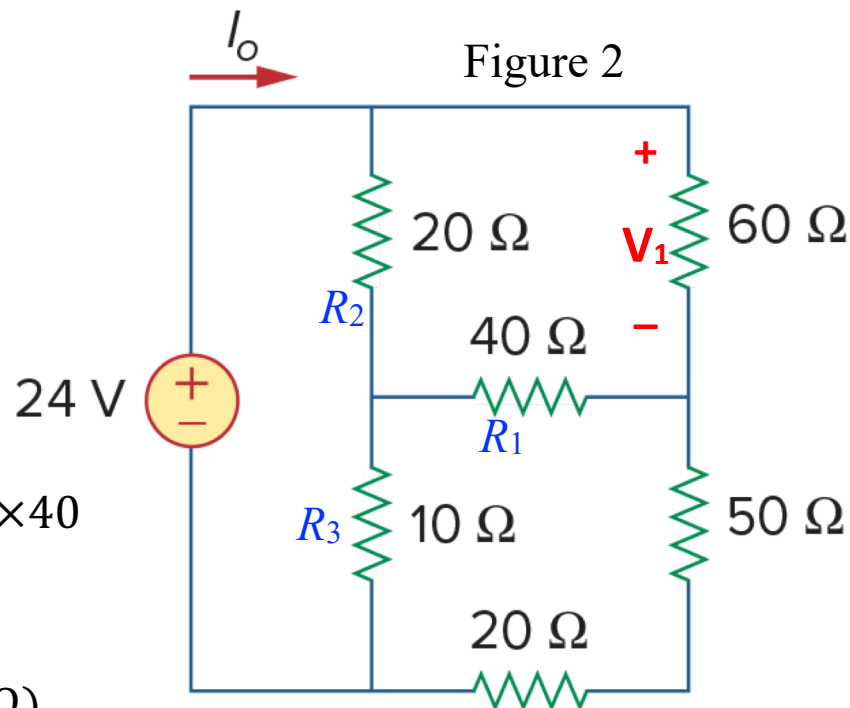
$$\begin{aligned}
 R_{AB} &= 35 // ((140 // 60) + (70 // 70)) \\
 &= 35 // (42 + 35) \\
 &= 24.0625
 \end{aligned}$$



$$\begin{aligned}
 I_o &= \frac{24}{R_{AB}} = \frac{24}{24.0625} \\
 &= 0.9974(\text{A})
 \end{aligned}$$

$$\begin{aligned}
 V_1 &= 24 \times \frac{140 // 60}{(140 // 60) + (70 // 70)} \\
 &= 24 \times \frac{42}{42 + 35} = 13.0909(\text{V})
 \end{aligned}$$

3. (20%) Calculate V and i_x in the circuit of Fig. 3.

For loop 1,

$$-10 + v + 4 = 0, \quad v = \mathbf{6 \text{ (V)}}$$

For loop 2,

$$-4 + 16 + 3 i_x = 0, \quad i_x = \mathbf{-4 \text{ (A)}}$$

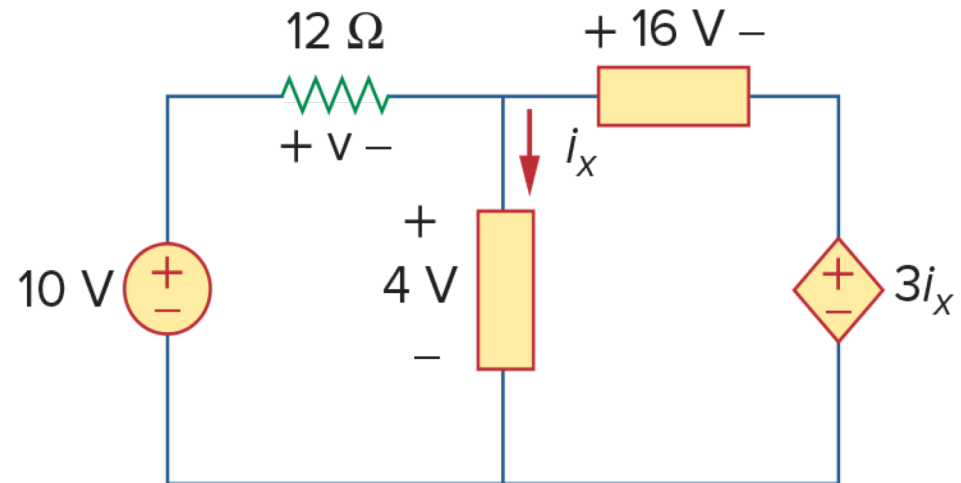


Figure 3

4. (30%) Consider the Wheatstone Bridge shown in Fig. 4.

(A) (15%) Calculate v_a , v_b , and v_{ab} ,

(B) (15%) Recalculate v_a , v_b , and v_{ab} , if the ground is placed at ***a*** instead of ***o***.

(A) Voltage division,

$$v_a = 25 \times \frac{8}{12 + 8} = 10 \text{ (V)}$$

$$v_b = 25 \times \frac{15}{10 + 15} = 15 \text{ (V)}$$

$$v_{ab} = v_a - v_b = 10 - 15 = -5 \text{ (V)}$$

(B) if the ground is placed at ***a***



$$v_a = 0 \text{ (V)}$$

$$v_{ac} = -25 \times \frac{12}{8 + 12} = -15 \text{ (V)}$$

$$v_{cb} = 25 \times \frac{10}{10 + 15} = 10 \text{ (V)}$$

$$v_{ab} = v_{ac} + v_{cb} = -15 + 10 = -5 \text{ (V)}$$
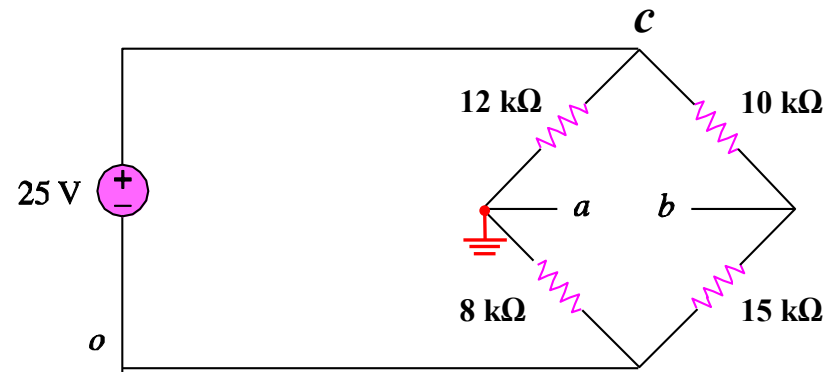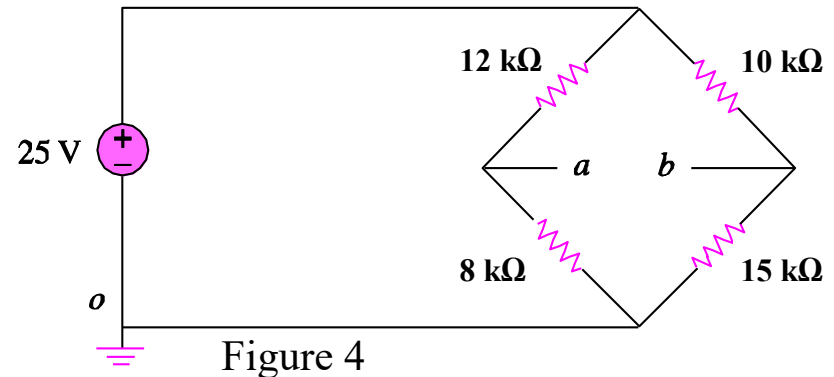
$$v_b = v_{ba} = -v_{ab} = 5 \text{ (V)}$$



5. (15%) Obtain $\mathbf{v_1}$ through $\mathbf{v_3}$ in the circuit of Fig. 5.

Applying KVL around the entire outside loop we get,


$$-24 + \mathbf{v_1} + 10 + 12 = 0 \text{ or } \mathbf{v_1 = 2V}$$

Applying KVL around the loop containing $\mathbf{v_2}$, the 10-volt source, and the 12-volt source we get,

$$\mathbf{v_2} + 10 + 12 = 0 \text{ or } \mathbf{v_2 = -22V}$$

Applying KVL around the loop containing $\mathbf{v_3}$ and the 10-volt source we get,
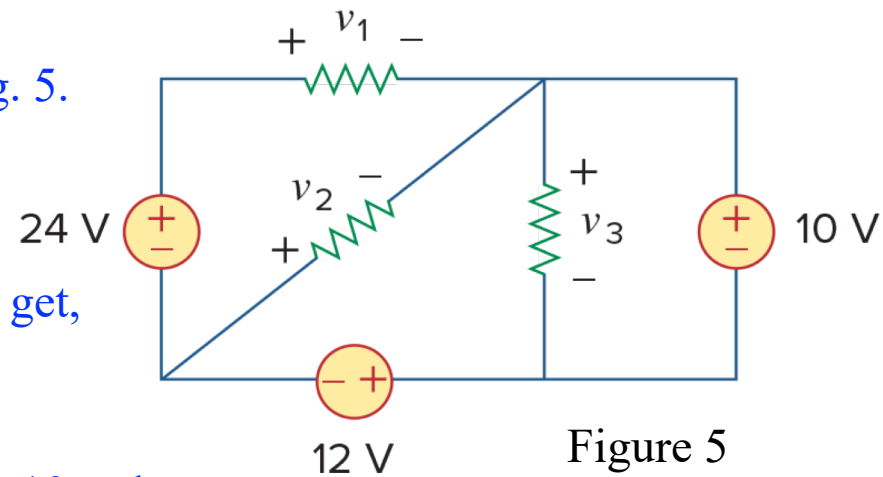
$$-\mathbf{v_3} + 10 = 0 \text{ or } \mathbf{v_3 = 10V}$$



6. (20%) Calculate V_o and I_o in the circuit of Fig. 6.

$$70//30 = \frac{70 \times 30}{70 + 30} = 21 \text{ } (\Omega)$$

$$20//5 = \frac{20 \times 5}{20 + 5} = 4 \text{ } (\Omega)$$

$$I = \frac{200}{21 + 4} = 8 \text{ (A)}$$

$$V_1 = I \times 21 = 8 \times 21 = 168 \text{ (V)}$$

$$V_o = I \times 4 = 8 \times 4 = 32 \text{ (V)}$$

$$I_1 = \frac{V_1}{70} = \frac{168}{70} = 2.4 \text{ (A)}$$

$$I_2 = \frac{V_o}{20} = \frac{32}{20} = 1.6 \text{ (A)}$$

$$I_o = I_1 - I_2 = 2.4 - 1.6 = 0.8 \text{ (A)}$$

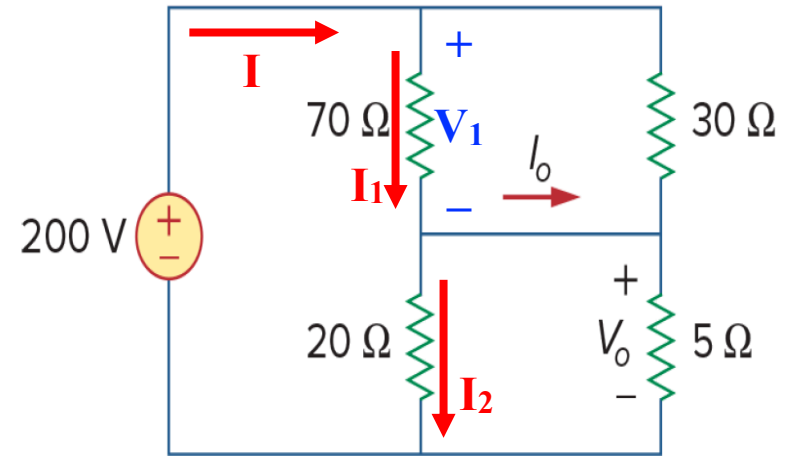


Figure 6