

# 112-1 ELECTRICAL ENGINEERING FUNDAMENTAL I


Name:

Quiz 4


2023.11.2

**Note:** Show your mathematic works and make your calculation accuracy to at least the 4<sup>th</sup> digit behind the decimal point.

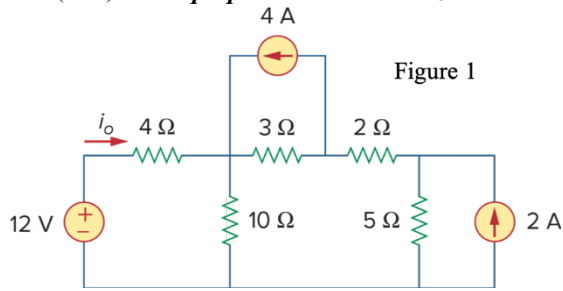
1. (30%) Use *superposition* to obtain  $i_o$  for the circuit of Fig. 1.



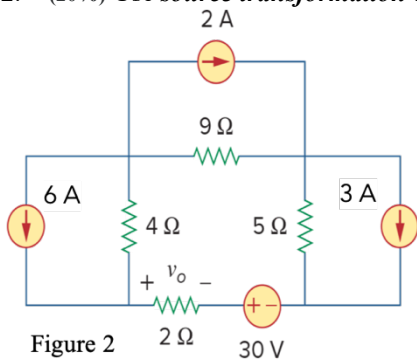2. (20%) Use *source transformation* to obtain  $v_o$  in the circuit of Fig. 2. (Draw the equivalent circuit as you convert the source.)



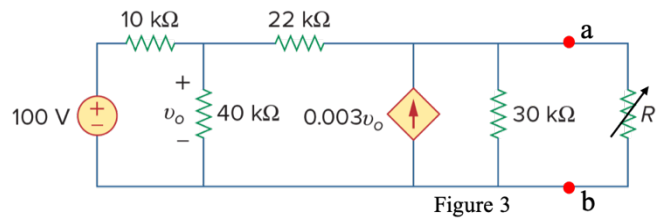3. (30%) In the circuit of Fig. 3, use the **Thevenin** theorem to find the  $V_{Th}$  and  $R_{Th}$  across the terminal a-b.



4. (30%) For the circuit in Fig. 4,
- 10% Use the Norton theorem to obtain the Norton equivalent (find  $I_{SC}$  and  $R_N$ , and draw the Norton equivalent circuit) ) at terminals a-b
  - 10% Convert the Norton equivalent circuit of (A) into its Thevenin's form.
  - 10% As the circuit is connected to a load, what is the maximal power that can be transferred to the load?

