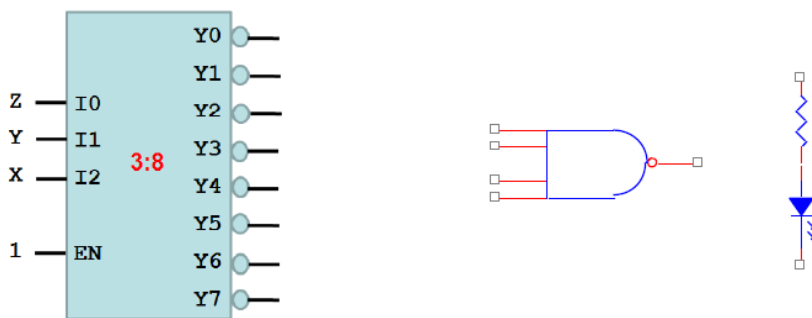


ISTM 214 Homework 7 (Due day: 11/22)


Name: _____ ID: _____

1. Draw the logic diagram of a 2-to-4-line decoder using (a) NOR gates only and (b) NAND gates only. (Include an enable input.)
2. Construct a 5-to-32-line decoder with four 3-to-8-line decoders with enable and a 2-to-4-line decoder.
3. Construct a 16 x 1 multiplexer with two 8 x 1 and one 2 x 1 multiplexers.
4. Demonstrate that you can implement any arbitrary 3-variable Boolean function using just a 3:8 decoder with active low outputs and a single 4-input NAND gate (plus some resistors and an LED).
(HINT: The LED may be connected in either a sourcing or a sinking configuration.)

(a) Complete the Schematic to implement the function $F(X,Y,Z) = X' \cdot Z + X \cdot Y \cdot Z'$



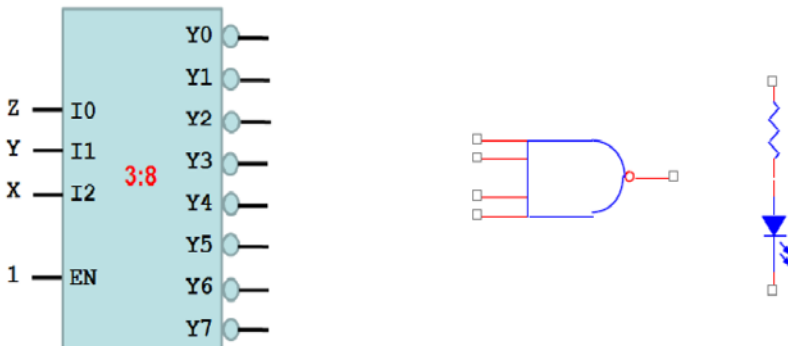(b) Complete the Schematic to implement the function $F(X,Y,Z) = X \cdot Y \cdot Z' + Y' \cdot Z + X \cdot Z'$



5. Demonstrate you can implement any arbitrary 3-variable Boolean function using only an 8:1 multiplexer by determining the data input settings (D0-D7) required to implement the function $F(X,Y,Z) = X \cdot Z' + X' \cdot (Y \oplus Z)$.

