

ISTM 214 Homework 3 (Due day: 10/11)

Name: _____ ID: _____

1. (60%) Given that a (5-volt) CMOS gate's P-channel pull-up has an "on" resistance of $80\ \Omega$ and that its N-channel pull-down has an "on" resistance of $40\ \Omega$:

(a) If the desired V_{OHmin} is 4.2 volts and the desired V_{OLmax} is 0.8 volts, what are the gate's I_{OHmax} and I_{OLmax} ratings?

$$I_{OHmax} = \underline{\hspace{1cm}} \text{ mA}$$

$$I_{OLmax} = \underline{\hspace{1cm}} \text{ mA}$$

(b) If a DCNM of 1.2 volts is desired for this CMOS gate family, what do its V_{IHmin} and V_{ILmax} specifications need to be, based on the values given in part (a)?

$$V_{IHmin} = \underline{\hspace{1cm}} \text{ V}$$

$$V_{ILmax} = \underline{\hspace{1cm}} \text{ V}$$

(c) If the I_{IH} and I_{IL} specifications for gates in this family are +0.1 mA and -0.1 mA, respectively, what is the practical fan-out for circuits constructed using these gates, based on values calculated in part (a)?

(d) Show how an LED (with forward voltage $V_{LED} = 1.5\text{ V}$) should be interfaced to gates in this family to obtain maximum brightness, and calculate the value of the current limiting resistor required along with its power dissipation.

$$\text{Current limiting resistor} = \underline{\hspace{1cm}} \Omega \quad \text{Resistor power dissipation} = \underline{\hspace{1cm}} \text{ mW}$$

2. (40%) Assume two logic families have the following D.C. characteristics:

Logic Family “A”

$V_{CC} = 5 \text{ V}$	$V_{OH} = 4.1 \text{ V}$	$V_{OL} = 0.4 \text{ V}$	$V_{IH} = 3.3 \text{ V}$	$V_{IL} = 1.3 \text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -7.5 \text{ mA}$	$I_{OL} = 7.5 \text{ mA}$	$I_{IH} = 0.25 \text{ } \mu\text{A}$	$I_{IL} = -0.25 \text{ } \mu\text{A}$

Logic Family “B”

$V_{CC} = 5 \text{ V}$	$V_{OH} = 3.4 \text{ V}$	$V_{OL} = 0.33 \text{ V}$	$V_{IH} = 2.7 \text{ V}$	$V_{IL} = 1.2 \text{ V}$
$V_{TH} = (V_{OH} - V_{OL})/2$	$I_{OH} = -900 \text{ } \mu\text{A}$	$I_{OL} = 8.8 \text{ mA}$	$I_{IH} = 13 \text{ } \mu\text{A}$	$I_{IL} = -0.13 \text{ mA}$

- (a) Calculate the following: $DCNM_{A \rightarrow B}$, $DCNM_{B \rightarrow A}$, Practical Fanout $A \rightarrow B$, Practical Fanout $B \rightarrow A$
- (b) Draw the circuit and calculate the value of the current limiting resistor for a Type “A” gate driving an LED to the maximum brightness possible in a current sourcing configuration. Assume V_{LED} is 1.5V.
- (c) Draw the circuit and calculate the value of the current limiting resistor for a Type “B” gate driving an LED to the maximum brightness possible in a current sinking configuration. Assume V_{LED} is 1.5V