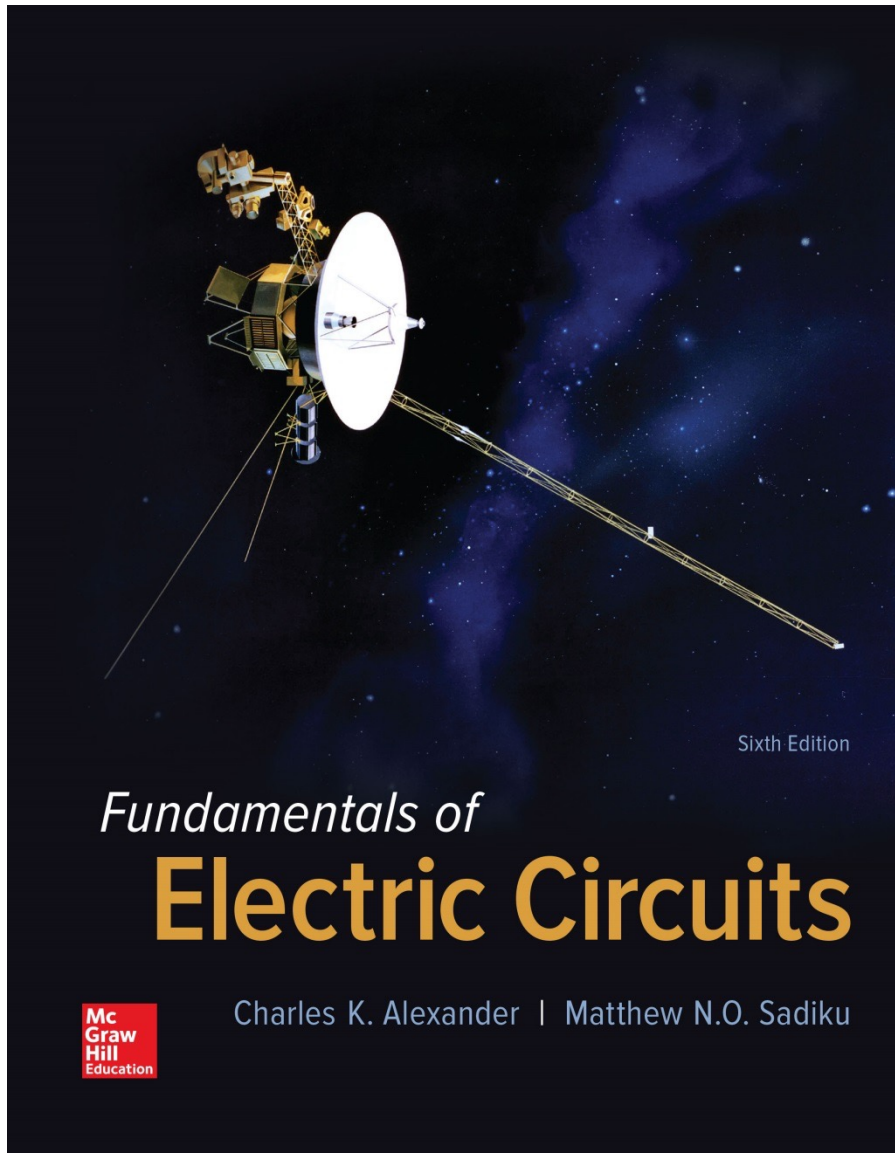


Chapter 3

Methods of Analysis



Overview

- With **Ohm's** and **Kirchhoff's law** established, they may now be applied to **circuit analysis**.
- Two techniques will be presented in this chapter:
 - **Nodal analysis**, which is based on Kirchhoff current law (**KCL**)
 - **Mesh analysis**, which is based on Kirchhoff voltage law (**KVL**)
- Any linear circuit can be analyzed using these two techniques.
- The analysis will result in a set of **simultaneous equations** which may be solved by Cramer's rule or computationally (using MATLAB for example)
- Computational circuit analysis using PSpice will also be introduced here.


3.2

Nodal Analysis

- If instead of focusing on the voltages of the circuit elements, one looks at the voltages at the nodes of the circuit, the number of simultaneous equations to solve for can be reduced.
- Given a circuit with n nodes, without voltage sources, the nodal analysis is accomplished via three steps:
 1. Select **a node as the reference node**. Assign voltages V_1, V_2, \dots, V_n to the **remaining $n-1$ nodes**, voltages are relative to the reference node.
 2. Apply **KCL** to each of the $n-1$ non-reference nodes. Use **Ohm's law** to express the **branch currents** in terms of **node voltages**
 3. **Solve the resulting $n-1$ simultaneous equations** to obtain the unknown node voltages.
- The **reference**, or datum, node is commonly referred to as the **ground** since its voltage is by default **zero**.

Current flows from a higher potential to a lower potential in a resistor.
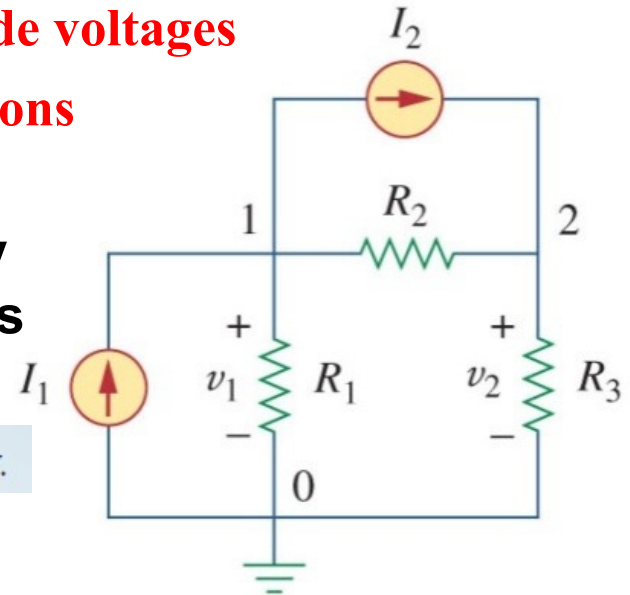
$$i = \frac{v_{\text{higher}} - v_{\text{lower}}}{R}$$





Applying Nodal Analysis

- Let's apply **nodal analysis** to this circuit to see how it works.
- This circuit has a node that is designed as ground. We will use that as the **reference node (node 0)**
- The remaining two nodes are designed **1** and **2** and assigned voltages **v_1** and **v_2** .
- Now apply **KCL** to each node:
- At node 1**

$$I_1 = I_2 + i_1 + i_2$$

- At node 2**

$$I_2 + i_2 = i_3$$

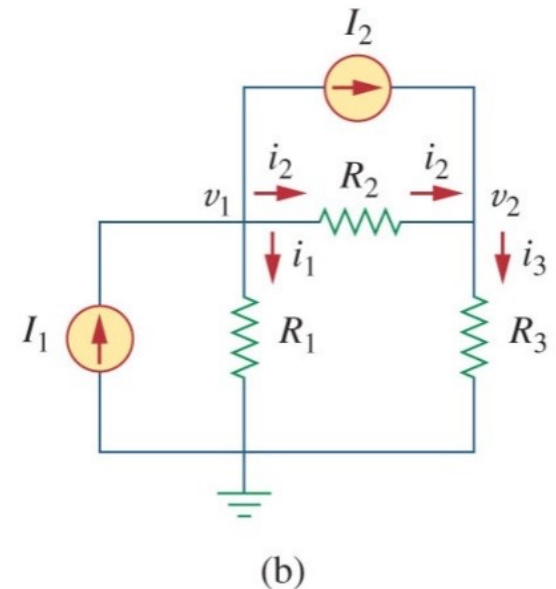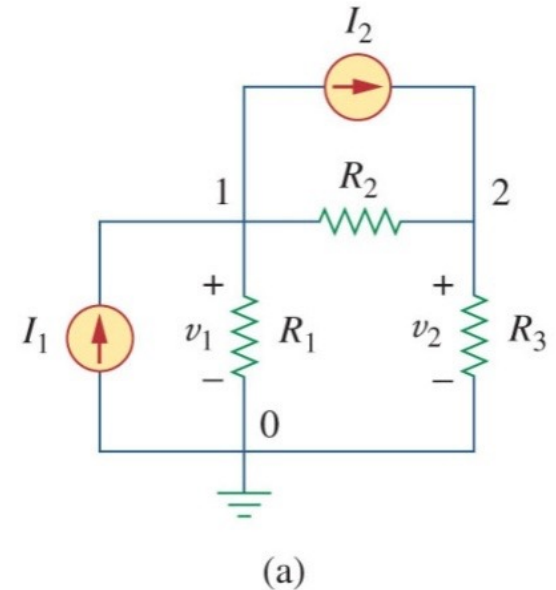

Apply Nodal Analysis II


- We can now use **OHM's law** to express the unknown currents i_1 , i_2 , and i_3 in terms of **node voltages**.
- In doing so, keep in mind that current flows from high potential to low
- From this we get:

$$i_1 = \frac{v_1 - 0}{R_1} \quad \text{or} \quad i_1 = G_1 v_1$$

$$i_2 = \frac{v_1 - v_2}{R_2} \quad \text{or} \quad i_2 = G_2 (v_1 - v_2)$$

$$i_3 = \frac{v_2 - 0}{R_3} \quad \text{or} \quad i_3 = G_3 v_2$$

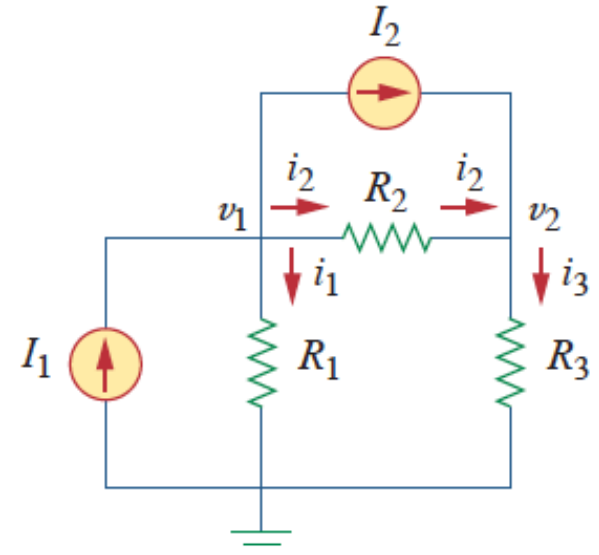$I_1 = I_2 + i_1 + i_2$
 $I_2 + i_2 = i_3$
 Substituting
 back into the
 node
 equations



$$I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2}$$

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3}$$

or

$$I_1 = I_2 + G_1 v_1 + G_2 (v_1 - v_2)$$

$$I_2 + G_2 (v_1 - v_2) = G_3 v_2$$

- The last step is to solve the system of equations: $v_1 = ?$ and $v_2 = ?$

Example 3.1

Calculate the node voltages in the circuit

At node 1, applying KCL and Ohm's law gives

$$i_1 = i_2 + i_3 \quad \Rightarrow \quad 5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2}$$

$$\Rightarrow 3v_1 - v_2 = 20$$

At node 2, we do the same thing and get

$$i_2 + i_4 = i_1 + i_5 \quad \Rightarrow \quad \frac{v_1 - v_2}{4} + 10 = 5 + \frac{v_2 - 0}{6}$$

$$\Rightarrow -3v_1 + 5v_2 = 60$$



METHOD 1 Using the elimination technique.

$$4v_2 = 80 \quad \Rightarrow \quad v_2 = 20 \text{ V}$$

$$3v_1 - 20 = 20 \quad \Rightarrow \quad v_1 = \frac{40}{3} = 13.333 \text{ V}$$

$$\Rightarrow i_1 = 5 \text{ A}, \quad i_2 = \frac{v_1 - v_2}{4} = -1.6668 \text{ A},$$
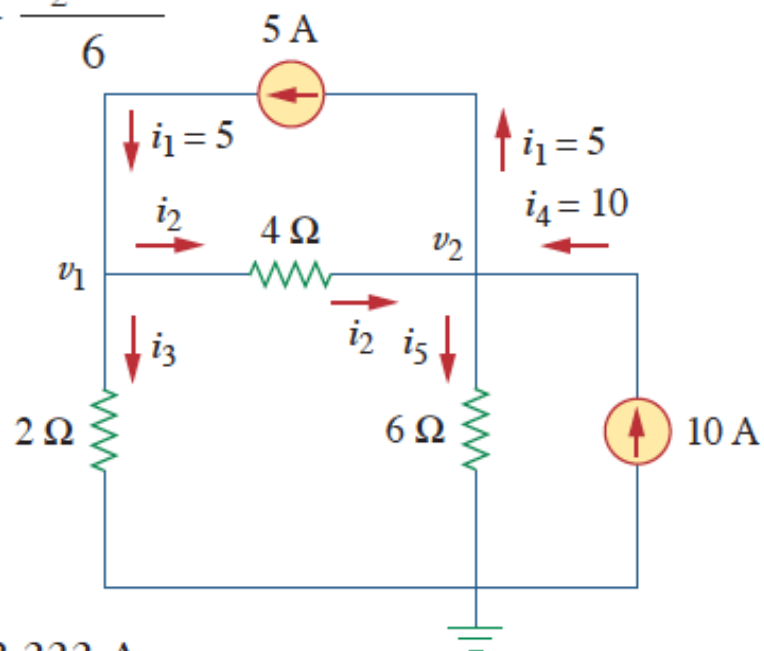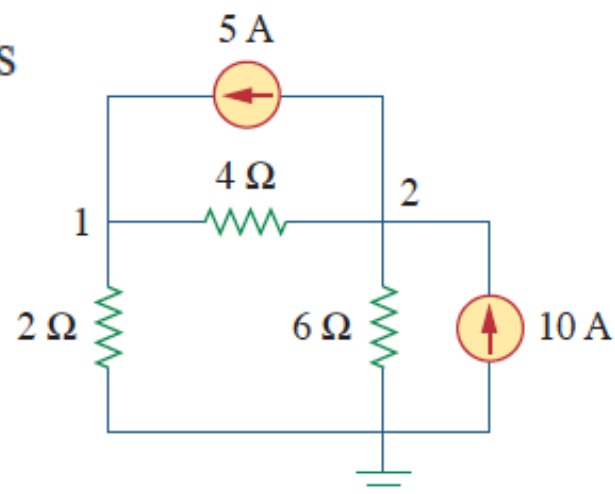
$$i_3 = \frac{v_1}{2} = 6.666 \text{ A} \quad i_4 = 10 \text{ A}, \quad i_5 = \frac{v_2}{6} = 3.333 \text{ A}$$



■ **METHOD 2** To use Cramer's rule,

$$3v_1 - v_2 = 20$$

$$-3v_1 + 5v_2 = 60$$

$$\begin{bmatrix} 3 & -1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 60 \end{bmatrix}$$

$$i_1 = 5 \text{ A}, \quad i_2 = \frac{v_1 - v_2}{4} = -1.6668 \text{ A},$$

$$\Delta = \begin{vmatrix} 3 & -1 \\ -3 & 5 \end{vmatrix} = 15 - 3 = 12$$

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 20 & -1 \\ 60 & 5 \end{vmatrix}}{\Delta} = \frac{100 + 60}{12} = 13.333 \text{ V}$$

$$v_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 3 & 20 \\ -3 & 60 \end{vmatrix}}{\Delta} = \frac{180 + 60}{12} = 20 \text{ V}$$

Example 3.2

Determine the voltages at the nodes

At node 1,

$$3 = i_1 + i_x \Rightarrow 3 = \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2}$$

$$\Rightarrow 3v_1 - 2v_2 - v_3 = 12 \quad \textcircled{1}$$

At node 2,

$$i_x = i_2 + i_3 \Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{8} + \frac{v_2 - 0}{4}$$

$$\Rightarrow -4v_1 + 7v_2 - v_3 = 0 \quad \textcircled{2}$$

At node 3,


$$i_1 + i_2 = 2i_x \Rightarrow \frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = \frac{2(v_1 - v_2)}{2}$$

$$\Rightarrow 2v_1 - 3v_2 + v_3 = 0 \quad \textcircled{3}$$

$$\textcircled{1} + \textcircled{3} \Rightarrow v_1 - v_2 = \frac{12}{5} = 2.4$$


$$\textcircled{2} + \textcircled{3} \Rightarrow v_1 = 2v_2$$
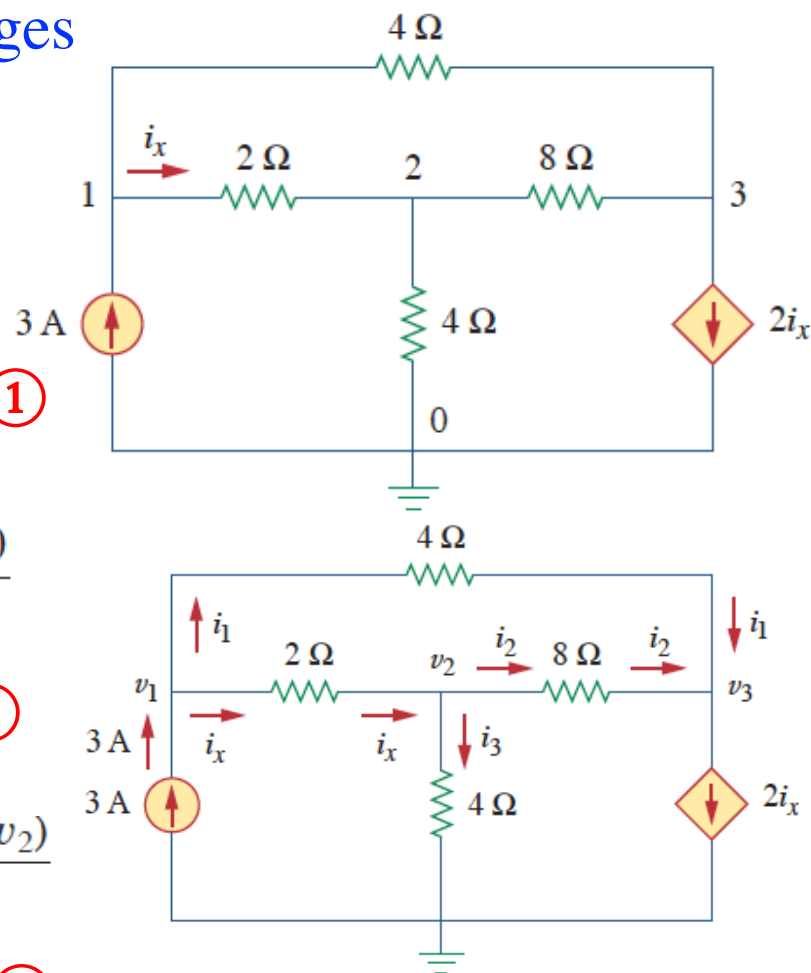
$$\Rightarrow v_2 = 2.4 \text{ V} \Rightarrow v_3 = -2.4 \text{ V}$$



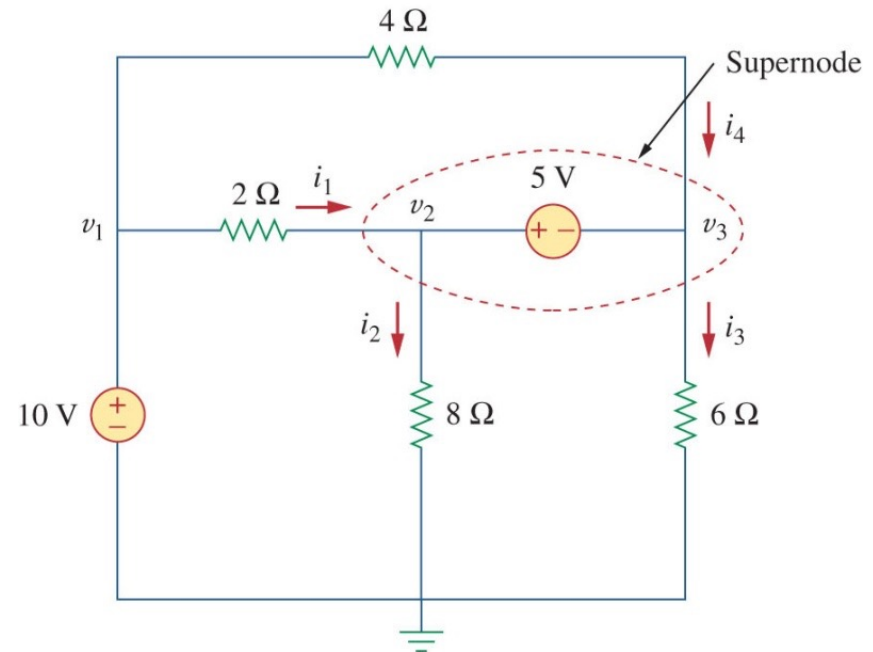3.3 Nodal Analysis with Voltage Sources

- Depending on what nodes the source is connected to, the approach varies
- Between the **reference node** and a **non-reference node**:
 - Set the voltage at the non-reference node to the voltage of the source
 - In the example circuit $v_1=10V$
- Between two **non-reference nodes**
 - The two nodes form a **supernode**.




Supernode

- A **supernode** is formed by enclosing a voltage source (dependent or independent) connected between **two non-reference nodes** and any elements connected in parallel with it.
- Why?
 - Nodal analysis requires applying **KCL**
 - The current through the voltage source cannot be known in advance (**Ohm's law does not apply**)
 - By lumping the nodes together, the current balance can still be described
- In the example circuit **node 2 and 3** form a **supernode**
- The **current balance** would be:


$$i_1 + i_4 = i_2 + i_3$$

- Or this can be expressed as:
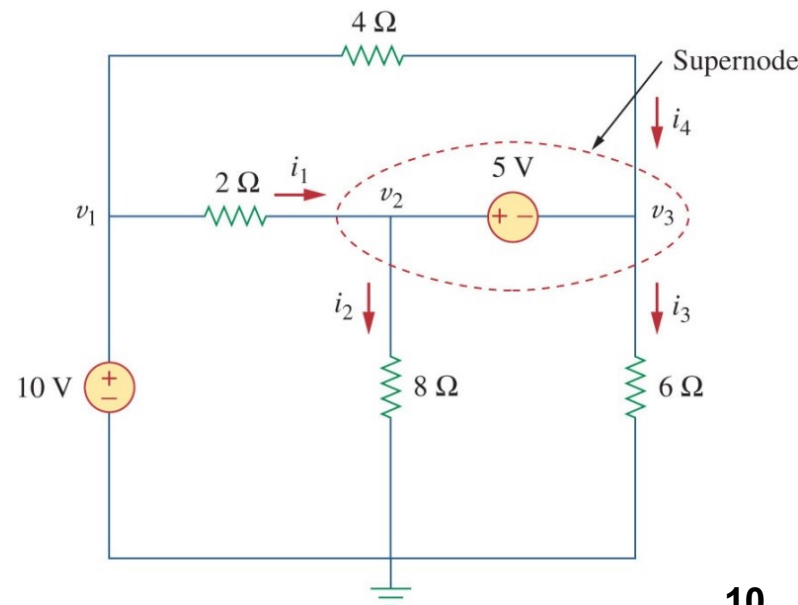
$$\frac{v_1 - v_2}{2} + \frac{v_1 - v_3}{4} = \frac{v_2 - 0}{8} + \frac{v_3 - 0}{6}$$



Analysis with a supernode

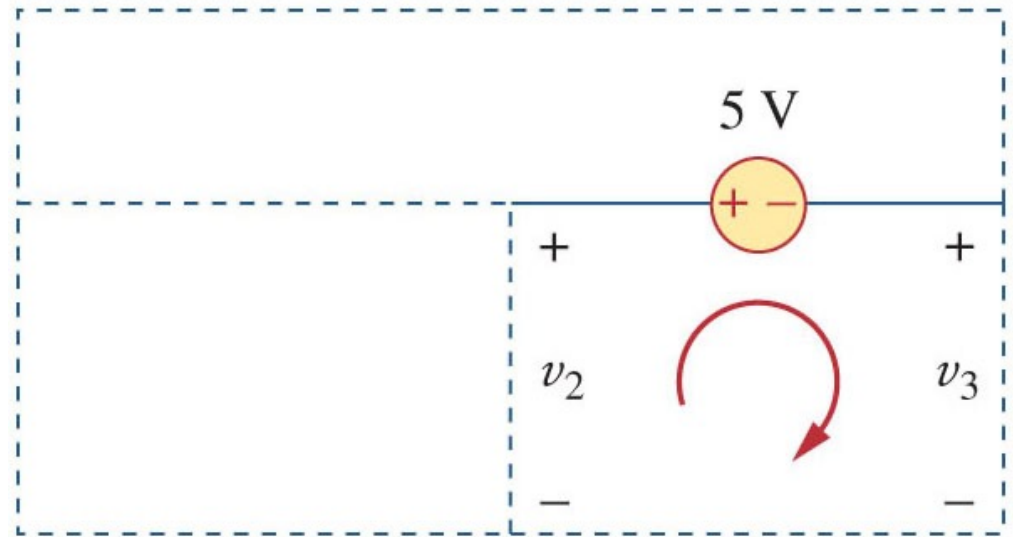

- In order to apply **KVL** to the supernode in the example, the circuit is redrawn as shown.
- Going around this loop in the clockwise direction gives:

$$-v_2 + 5 + v_3 = 0 \quad \Rightarrow \quad v_2 - v_3 = 5$$

- Note the following properties of a supernode:
 1. The voltage source inside the **supernode** provides a **constraint equation** needed to solve for the node voltages
 2. A supernode has no voltage of its own
 3. A supernode requires the application of both **KCL** and **KVL**

Example 3.3 Find the node voltages

Applying KCL to the supernode

$$\Rightarrow 2 = i_1 + i_2 + 7$$

$$2 = \frac{v_1 - 0}{2} + \frac{v_2 - 0}{4} + 7 \Rightarrow 8 = 2v_1 + v_2 + 28$$




$$\Rightarrow v_2 = -20 - 2v_1$$

apply KVL

$$-v_1 - 2 + v_2 = 0 \Rightarrow v_2 = v_1 + 2$$

$$\Rightarrow v_1 = -7.333 \text{ V}$$

$$v_2 = v_1 + 2 = -5.333 \text{ V}$$

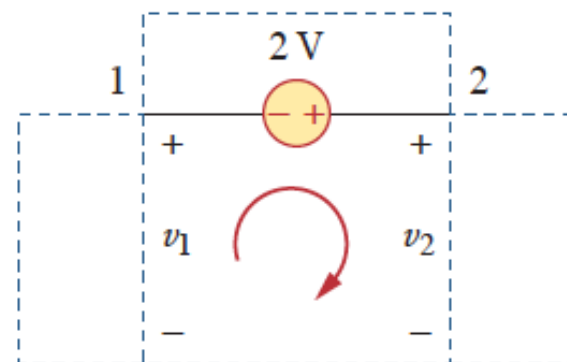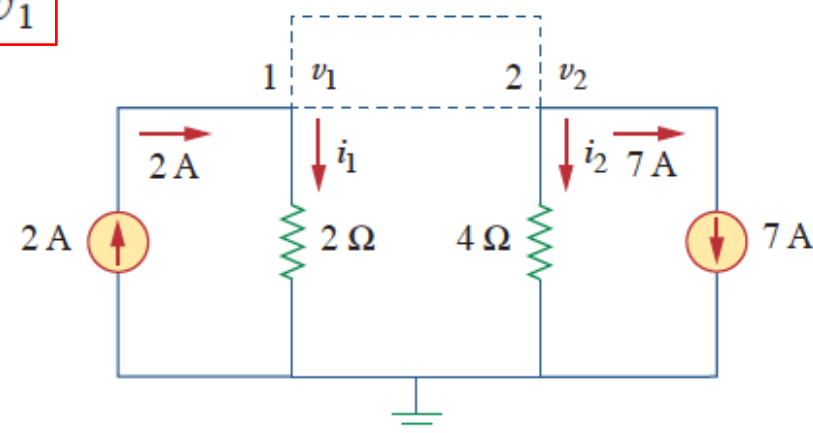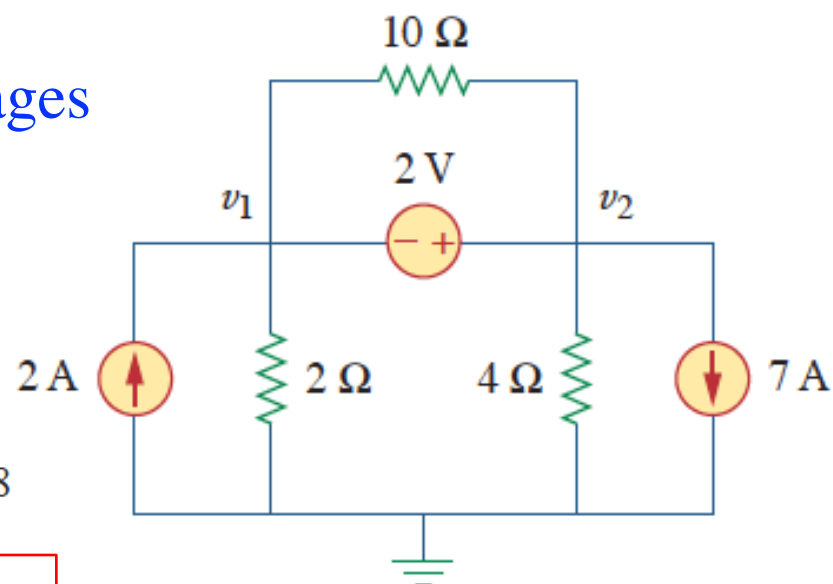

Example 3.4

Find the node voltages in the circuit

Figure 3.12

For Example 3.4.

At supernode 1-2,

$$i_3 + 10 = i_1 + i_2$$

$$\Rightarrow \frac{v_3 - v_2}{6} + 10 = \frac{v_1 - v_4}{3} + \frac{v_1}{2}$$


$$\Rightarrow 5v_1 + v_2 - v_3 - 2v_4 = 60$$

At supernode 3-4,

$$i_1 = i_3 + i_4 + i_5$$

$$\Rightarrow \frac{v_1 - v_4}{3} = \frac{v_3 - v_2}{6} + \frac{v_4}{1} + \frac{v_3}{4}$$

$$\Rightarrow 4v_1 + 2v_2 - 5v_3 - 16v_4 = 0$$

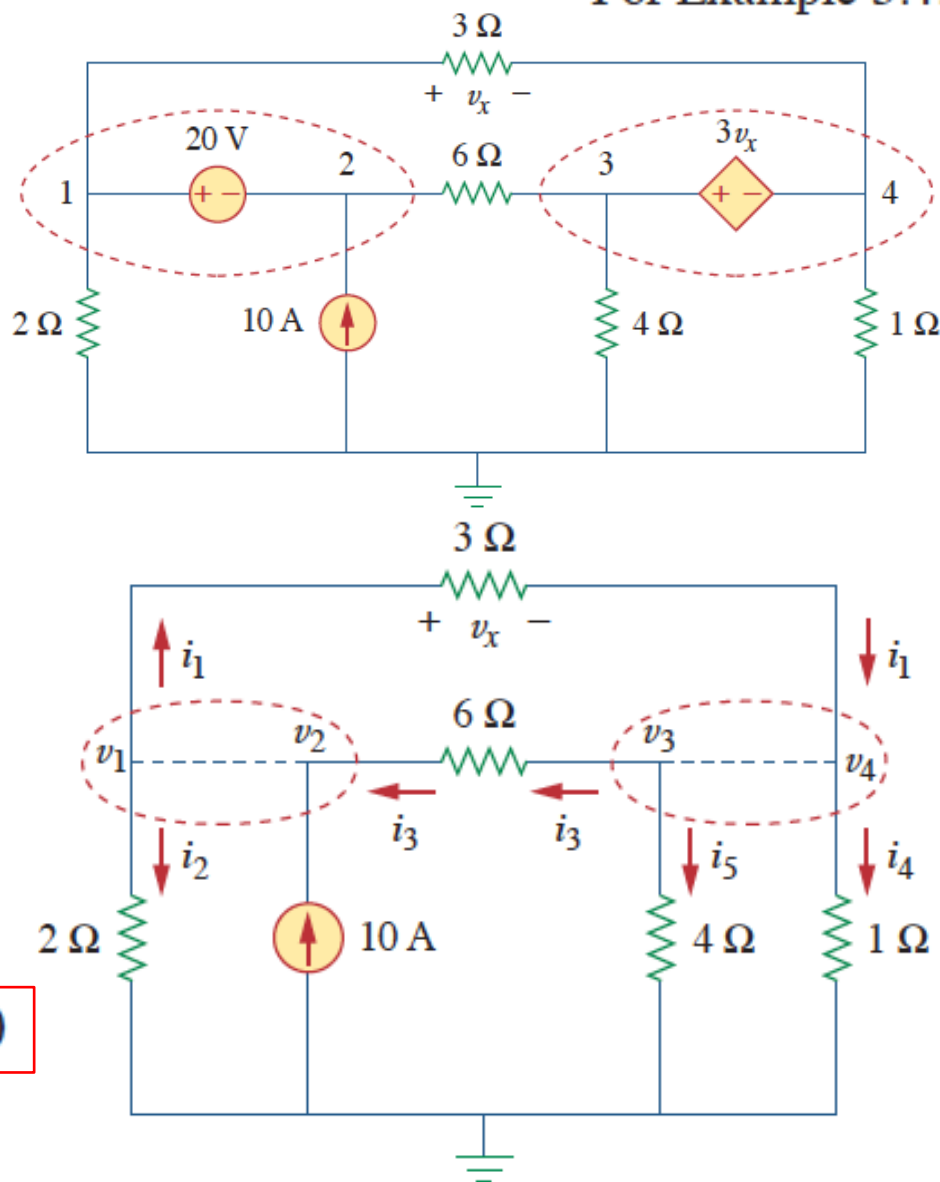

Example 3.4

Find the node voltages in the circuit

$$5v_1 + v_2 - v_3 - 2v_4 = 60 \quad (1)$$

$$4v_1 + 2v_2 - 5v_3 - 16v_4 = 0 \quad (2)$$

apply KVL to the branches

For loop 1, $-v_1 + 20 + v_2 = 0$

$$\Rightarrow v_1 - v_2 = 20$$

For loop 2, $-v_3 + 3v_x + v_4 = 0$

But $v_x = v_1 - v_4 \Rightarrow 3v_1 - v_3 - 2v_4 = 0 \quad (3)$

For loop 3, $v_x - 3v_x + 6i_3 - 20 = 0$

But $6i_3 = v_3 - v_2$ and $v_x = v_1 - v_4 \Rightarrow -2v_1 - v_2 + v_3 + 2v_4 = 20$


$$v_2 = v_1 - 20.$$

$$(3) \Rightarrow 3v_1 - v_3 - 2v_4 = 0$$

$$(1) \Rightarrow 6v_1 - v_3 - 2v_4 = 80$$

$$(2) \Rightarrow 6v_1 - 5v_3 - 16v_4 = 40$$
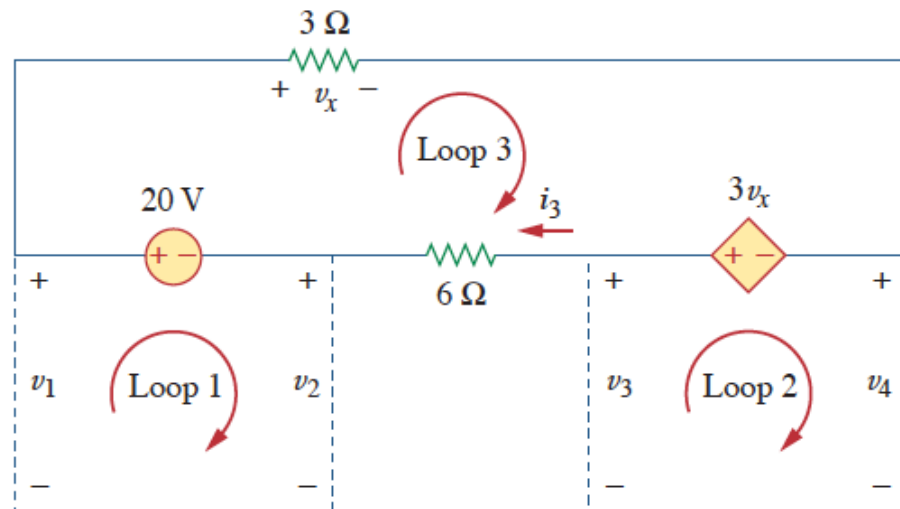
$$\Rightarrow \begin{bmatrix} 3 & -1 & -2 \\ 6 & -1 & -2 \\ 6 & -5 & -16 \end{bmatrix} \begin{bmatrix} v_1 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 80 \\ 40 \end{bmatrix}$$



Practice Problem 3.4

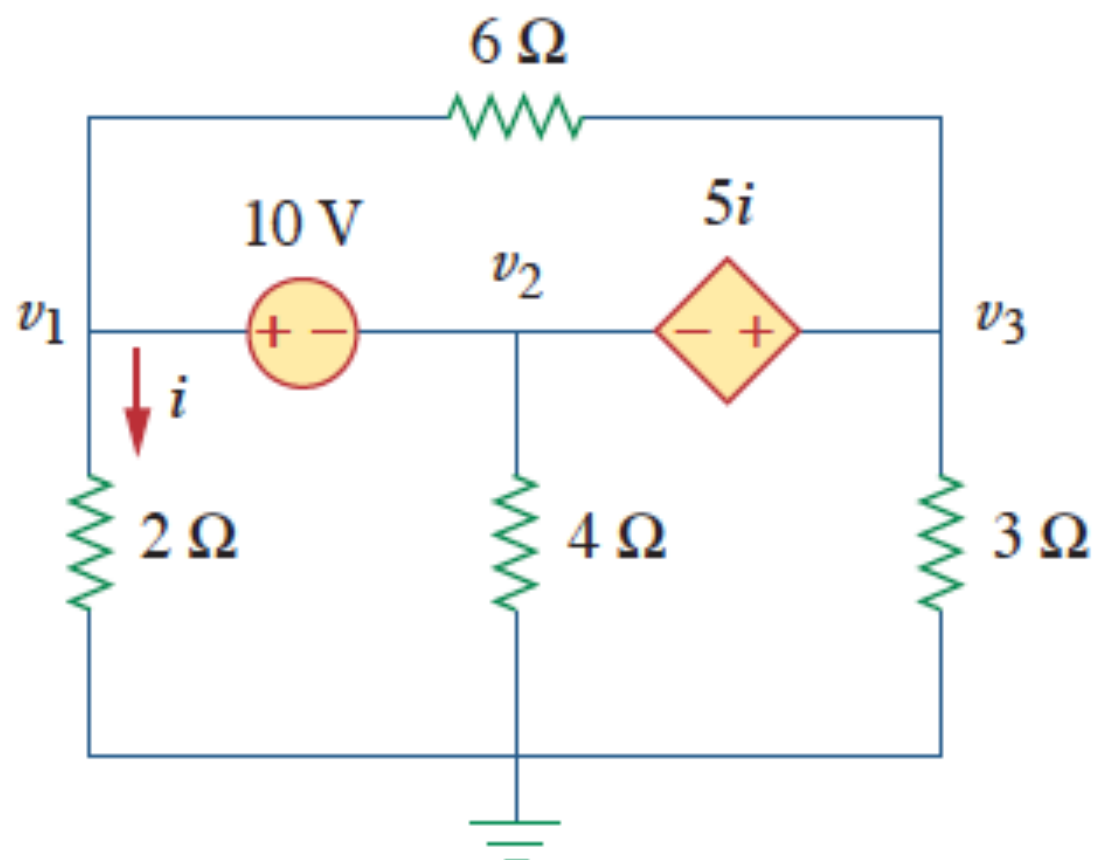



Figure 3.14

3.4


Mesh Analysis

- Another general procedure for analyzing circuits is to use the **mesh currents** as the circuit variables.
- Recall:
 - A **loop** is a closed path with no node passed more than once
 - A **mesh** is a **loop** that **does not contain any other loop within it**
- **Mesh analysis** uses **KVL** to find unknown currents
- Mesh analysis is limited in one aspect:
 - **It can only apply to circuits that can be rendered planar.**
- A **planar circuit** can be drawn such that there are no crossing branches.


Planar vs Nonplanar

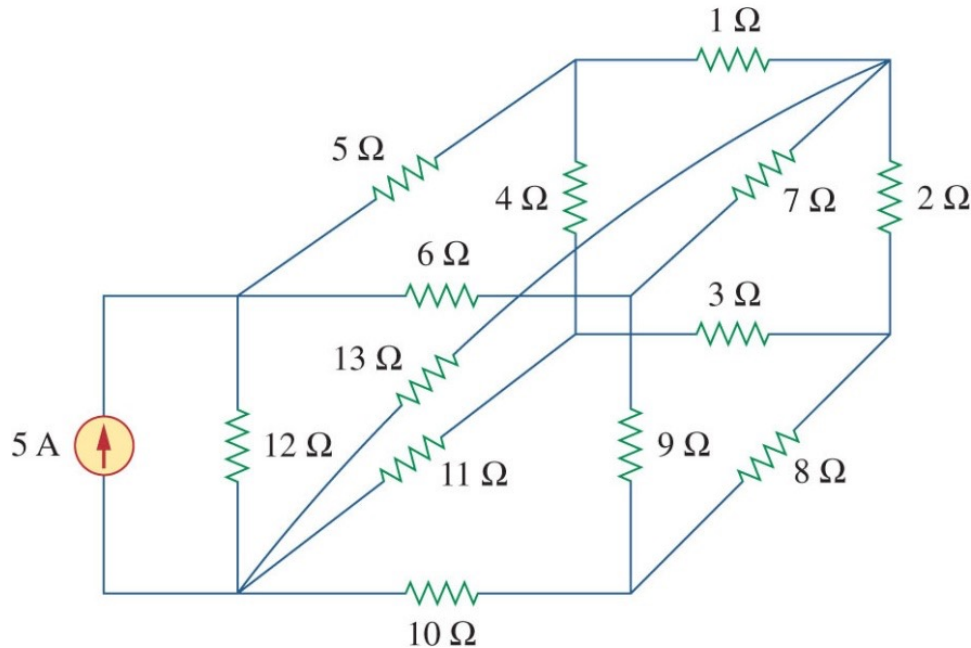

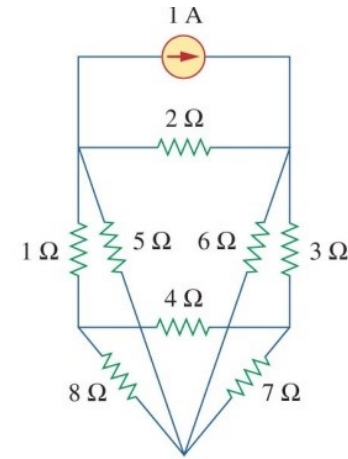The figure on the left is a **nonplanar circuit**: The branch with the 13Ω resistor prevents the circuit from being drawn without crossing branches



(a)

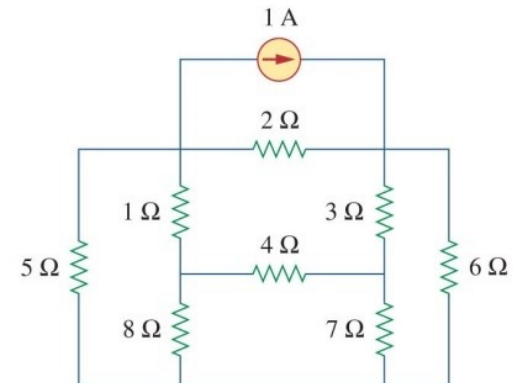


(b)

The figure on the right is a **planar circuit**: It can be redrawn to avoid crossing branches

Mesh Analysis Steps


- Mesh analysis follows these steps:

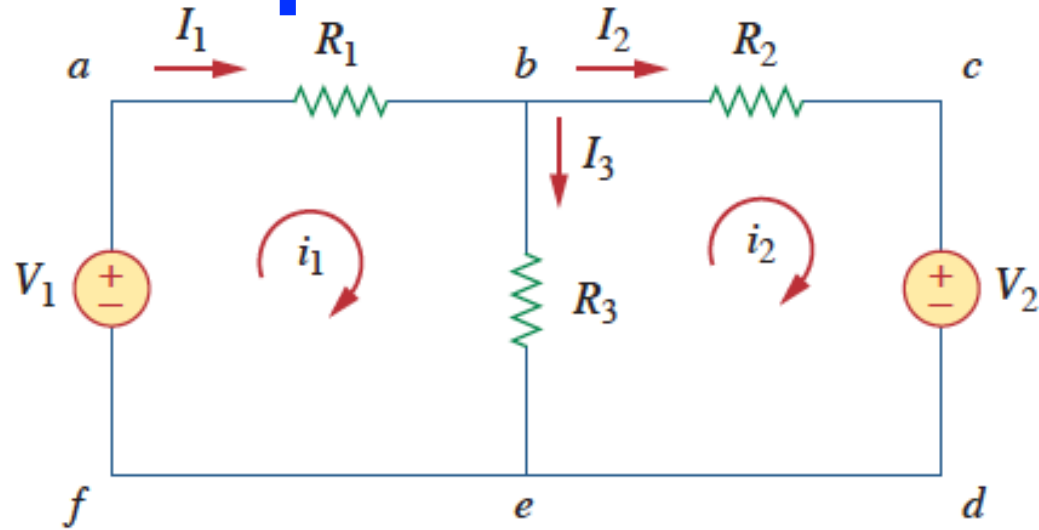

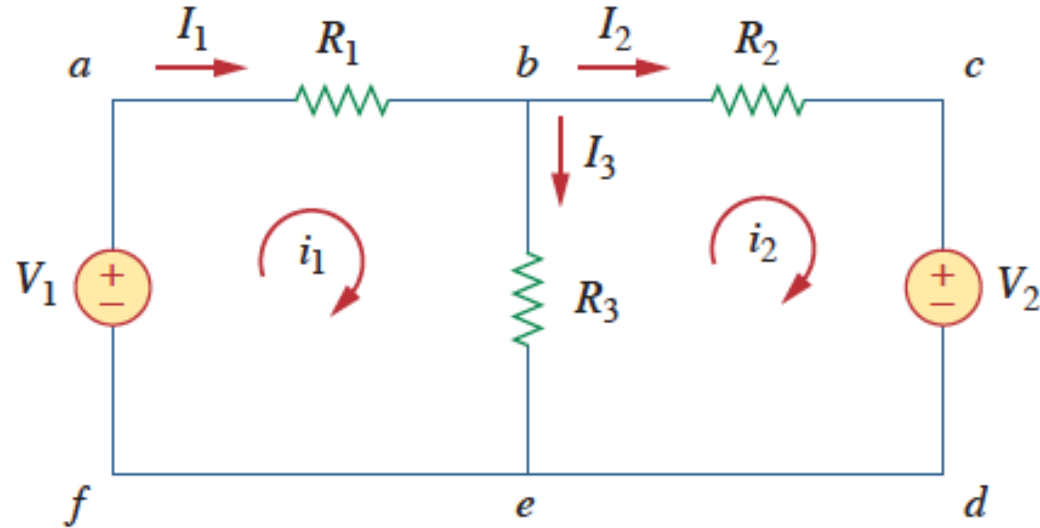1. Assign mesh currents i_1, i_2, \dots, i_n to the n meshes
2. Apply **KVL** to each of the n mesh currents.
3. Solve the resulting n simultaneous equations to get the mesh currents

Mesh Analysis Example

- The above circuit has two paths that are **meshes**:
(**abefa** and **bcdeb**)



- The outer loop (abcdefa) is a loop, but not a mesh
- First, mesh currents i_1 and i_2 are assigned to the two meshes.

- Applying KVL to the meshes:**

$$\begin{array}{cc}
 -V_1 + R_1 i_1 + R_3 (i_1 - i_2) = 0 & R_2 i_2 + V_2 + R_3 (i_2 - i_1) = 0 \\
 \Downarrow & \Downarrow
 \end{array}$$

$$(R_1 + R_3) i_1 - R_3 i_2 = V_1 \qquad -R_3 i_1 + (R_2 + R_3) i_2 = -V_2$$

Example 3.5

Find the branch currents and using mesh analysis.

For mesh 1, $-15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$

$$\Rightarrow 3i_1 - 2i_2 = 1$$

For mesh 2, $6i_2 + 4i_2 + 10(i_2 - i_1) - 10 = 0$

$$\Rightarrow i_1 = 2i_2 - 1$$

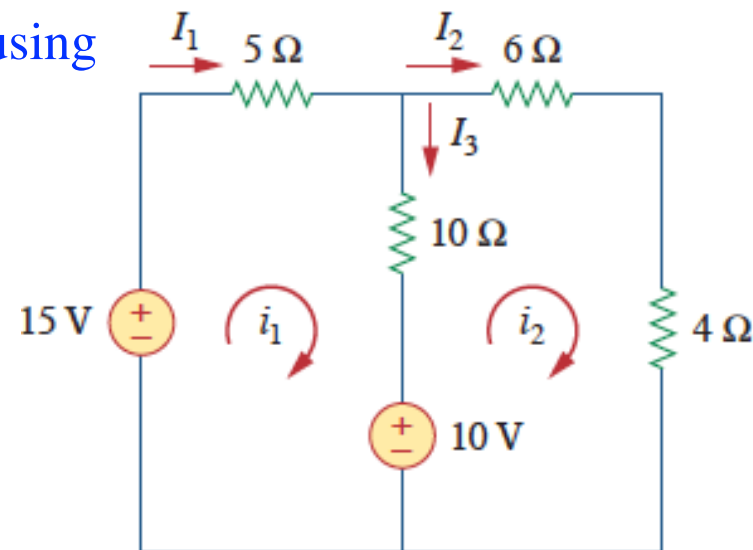


Figure 3.18

■ **METHOD 1** Using the substitution method,

$$6i_2 - 3 - 2i_2 = 1 \quad \Rightarrow \quad i_2 = 1 \text{ A}$$

$$i_1 = 2i_2 - 1 = 2 - 1 = 1 \text{ A.}$$

$$I_3 = i_1 - i_2 = 0$$

■ **METHOD 2** To use Cramer's rule,

$$\Delta = \begin{vmatrix} 3 & -2 \\ -1 & 2 \end{vmatrix} = 6 - 2 = 4$$

$$\Delta_1 = \begin{vmatrix} 1 & -2 \\ 1 & 2 \end{vmatrix} = 2 + 2 = 4,$$

$$\Delta_2 = \begin{vmatrix} 3 & 1 \\ -1 & 1 \end{vmatrix} = 3 + 1 = 4$$

$$\begin{bmatrix} 3 & -2 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$i_1 = \frac{\Delta_1}{\Delta} = 1 \text{ A,}$$

$$i_2 = \frac{\Delta_2}{\Delta} = 1 \text{ A}$$

$$I_3 = i_1 - i_2 = 0$$

Example 3.6

Use mesh analysis to find the current I_o

For mesh 1, $-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$

$$\Rightarrow 11i_1 - 5i_2 - 6i_3 = 12$$

For mesh 2, $24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$

$$\Rightarrow -5i_1 + 19i_2 - 2i_3 = 0$$

For mesh 3, $4I_o + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$

$$I_o = i_1 - i_2,$$

$$\Rightarrow 4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$

$$\Rightarrow -i_1 - i_2 + 2i_3 = 0$$

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix} \Rightarrow \begin{cases} \Delta = 192 \\ \Delta_1 = 432 \\ \Delta_2 = 144 \\ \Delta_3 = 288 \end{cases} \Rightarrow$$

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{432}{192} = 2.25 \text{ A},$$

$$i_2 = \frac{\Delta_2}{\Delta} = \frac{144}{192} = 0.75 \text{ A},$$

$$i_3 = \frac{\Delta_3}{\Delta} = \frac{288}{192} = 1.5 \text{ A}$$

$$I_o = i_1 - i_2 = 1.5 \text{ A.}$$


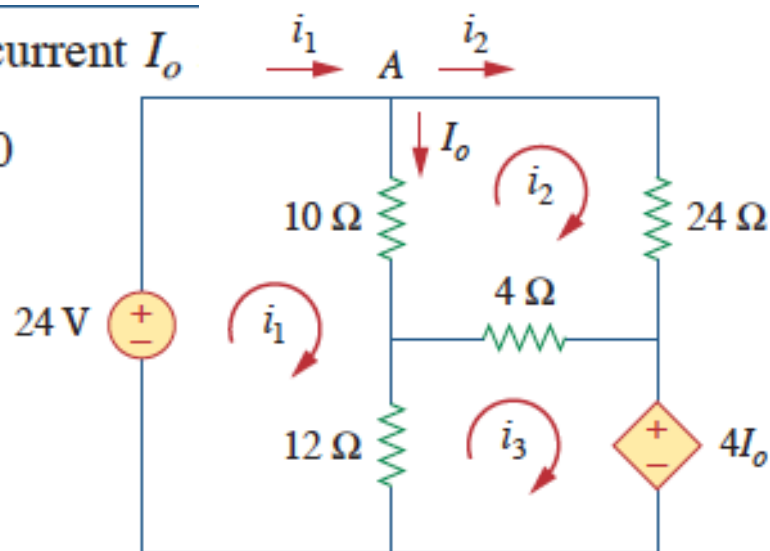


Figure 3.20

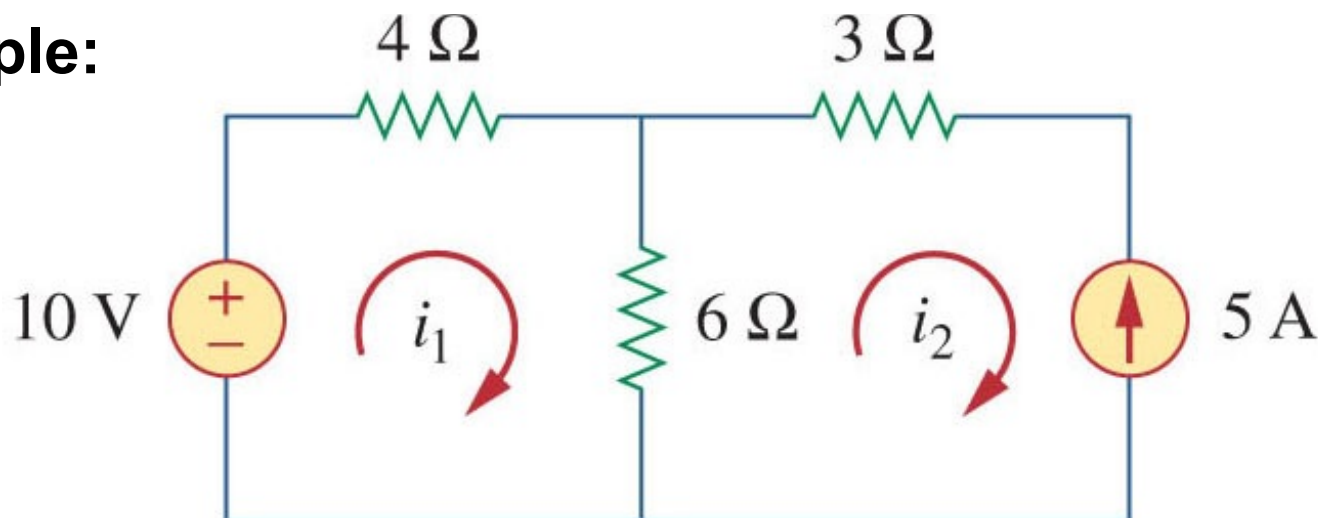3.5

Mesh Analysis with Current Sources



- The presence of a **current source** makes the mesh analysis simpler in that it reduces the number of equations.
- If the current source is located on only one mesh, the current for that mesh is defined by the source.
- For example:





- Here, the current i_2 is equal to -5A

Supermesh

- Similar to the case of nodal analysis where a voltage source shared two non-reference nodes, **current sources** (dependent or independent) that are **shared by more than one mesh** need special treatment
- **The two meshes must be joined together**, resulting in a **supermesh**.
- The **supermesh** is constructed by merging the two meshes and **excluding the shared source and any elements in series with it**
- A **supermesh** is required because mesh analysis uses KVL
- But the voltage across a current source cannot be known in advance.
- Intersecting supermeshes in a circuit must be combined to form a **larger supermesh**.

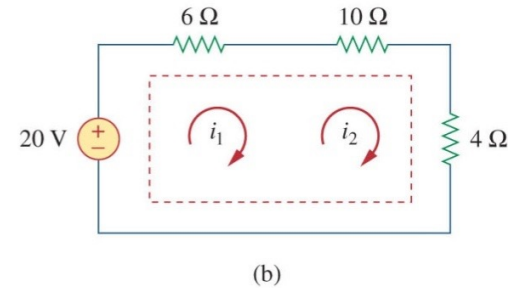
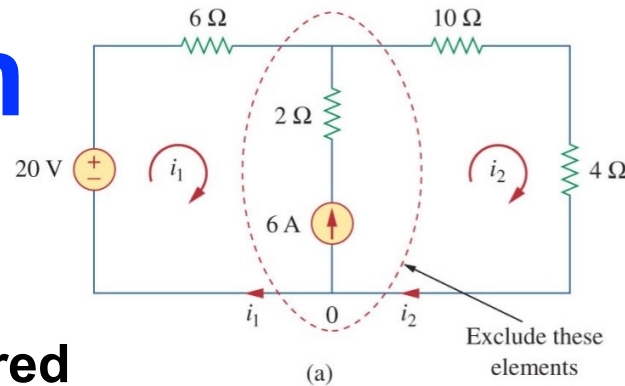


Creating a Supermesh

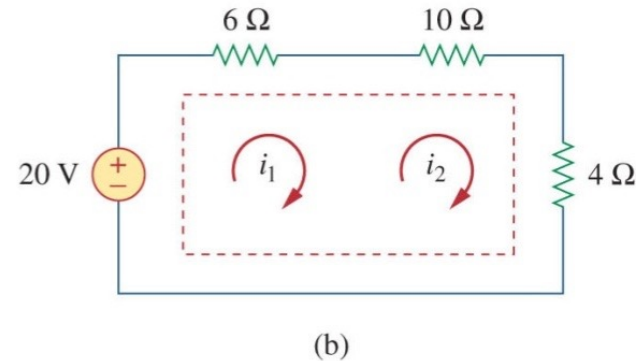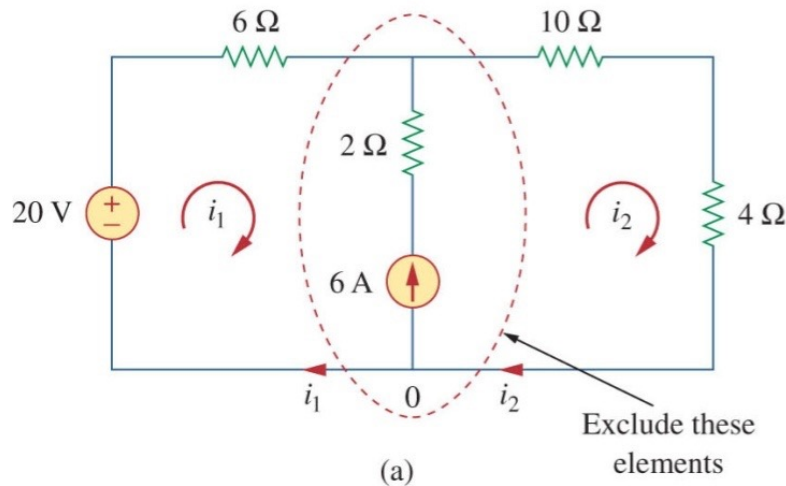

- In this example, a **6A** current source is shared between **mesh 1** and **2**.
- The **supermesh** is formed by **merging the two meshes**.
- The **current source** and the **2Ω resistor** in series with it are removed.

Supermesh Example

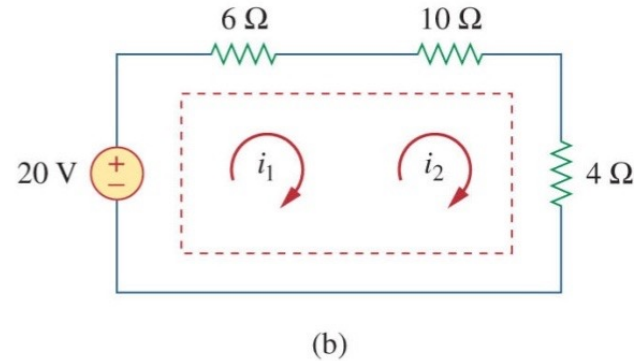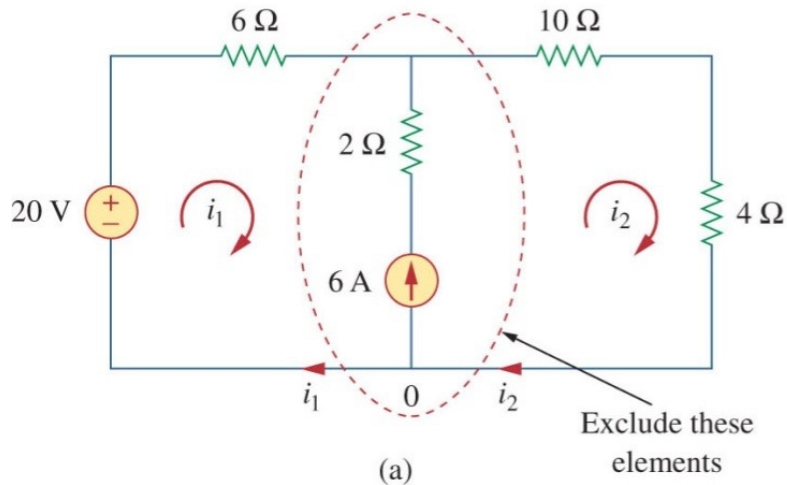

- Apply **KVL** to the supermesh

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0 \quad \text{or} \quad 6i_1 + 14i_2 = 20$$

- We next apply **KCL** to the node in the branch where the two meshes intersect.

$$i_2 = i_1 + 6$$

- Solving these two equations we get:

$$i_1 = -3.2\text{A} \quad i_2 = 2.8\text{A}$$

- Note that the supermesh required using both KVL and KCL

Example 3.7

find i_1 to i_4 using mesh analysis.

Applying KVL to the larger supermesh,

$$2i_1 + 4i_3 + 8(i_3 - i_4) + 6i_2 = 0$$

$$\Rightarrow i_1 + 3i_2 + 6i_3 - 4i_4 = 0 \quad (1)$$

KCL to node P :

$$i_2 = i_1 + 5 \quad (2)$$

KCL to node Q :

$$i_2 = i_3 + 3I_o$$

$$I_o = -i_4,$$

$$\Rightarrow i_2 = i_3 - 3i_4 \quad (3)$$

Applying KVL in mesh 4,

$$2i_4 + 8(i_4 - i_3) + 10 = 0$$

$$\Rightarrow 5i_4 - 4i_3 = -5 \quad (4)$$

$$\Rightarrow \begin{aligned} i_1 &= -7.5 \text{ A}, & i_2 &= -2.5 \text{ A}, \\ i_3 &= 3.93 \text{ A}, & i_4 &= 2.143 \text{ A} \end{aligned}$$

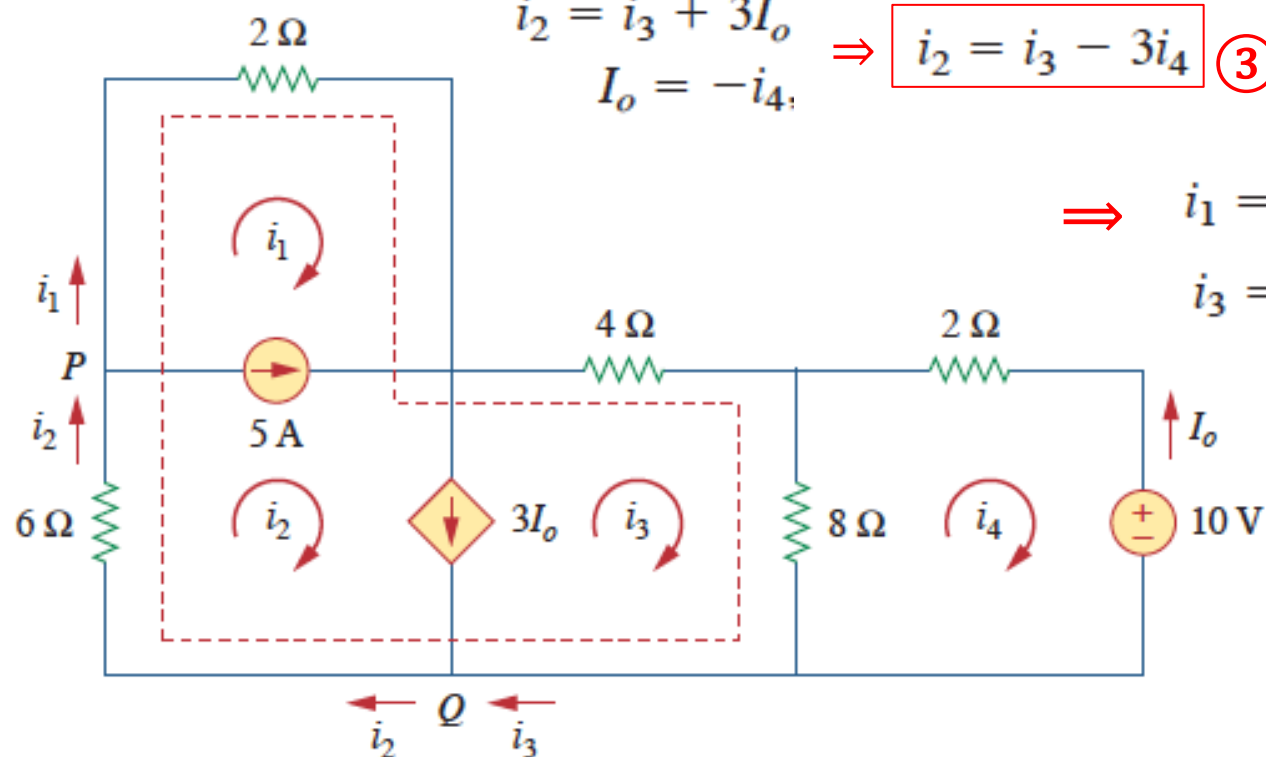


Figure 3.24

3.38 Apply mesh analysis to the circuit in Fig. 3.84 and obtain I_o .

We need 4 independent equations.

From Mesh 1:

$$i_1 = -5 \text{ A}$$

From Mesh 2:


$$\begin{aligned} 1 \cdot (i_2 - i_1) + 2 \cdot (i_2 - i_4) + 22.5 + 4 \cdot i_2 &= 0 \\ \Rightarrow 7 \cdot i_2 - i_4 &= -27.5 \end{aligned}$$

From Supermesh:

$$\begin{aligned} -60 + 4 \cdot i_3 + 3 \cdot i_4 + 1 \cdot i_4 + 2 \cdot (i_4 - i_2) + 2 \cdot (i_3 - i_1) &= 0 \\ \Rightarrow -2 \cdot i_2 + 6 \cdot i_3 + 6 \cdot i_4 &= 50 \end{aligned}$$

And: $-i_3 + i_4 = 10$
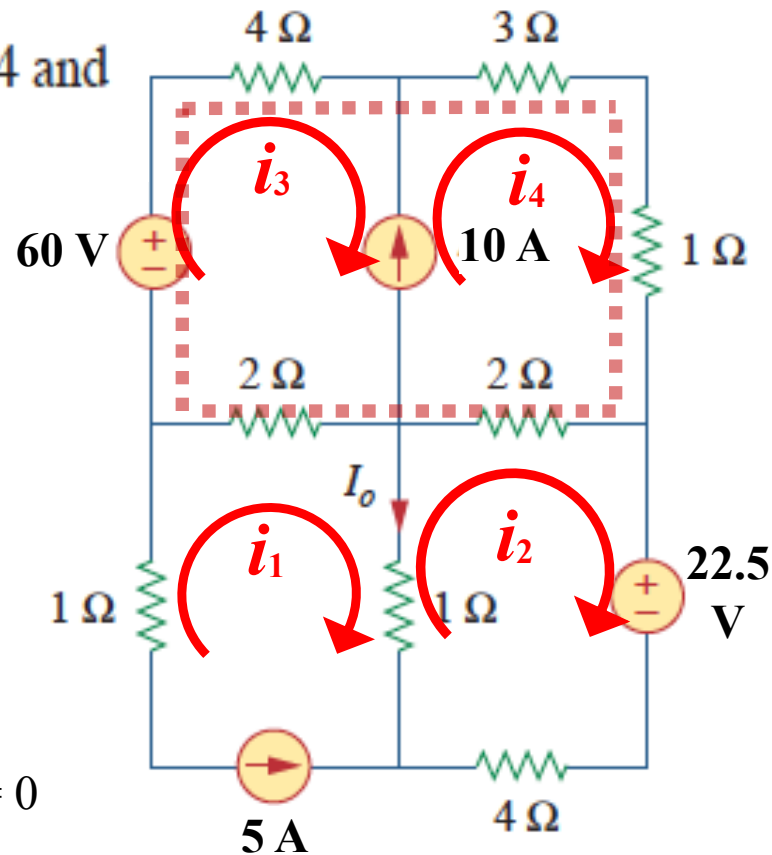
$$\begin{bmatrix} 7 & 0 & -1 \\ -2 & 6 & 6 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -27.5 \\ 50 \\ 10 \end{bmatrix}$$



$$i_1 = -5 \text{ (A)}$$

$$i_2 = -1.375 \text{ (A)}$$

$$i_3 = -10 \text{ (A)}$$

$$i_4 = 17.875 \text{ (A)}$$

$$I_o = i_1 - i_2 = -5 - 1.375 = -6.375 \text{ (A)}$$

Mesh Analysis

- There is a similarly fast way to construct a **matrix** for solving a circuit by **mesh analysis**
- It requires that **all voltage sources within the circuit be independent**
- In general, for a circuit with **N meshes**, the mesh-current equations may be written as:

$$\begin{bmatrix} R_{11} & R_{12} & \cdots & R_{1N} \\ R_{21} & R_{22} & \cdots & R_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ R_{N1} & R_{N2} & \cdots & R_{NN} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{bmatrix}$$

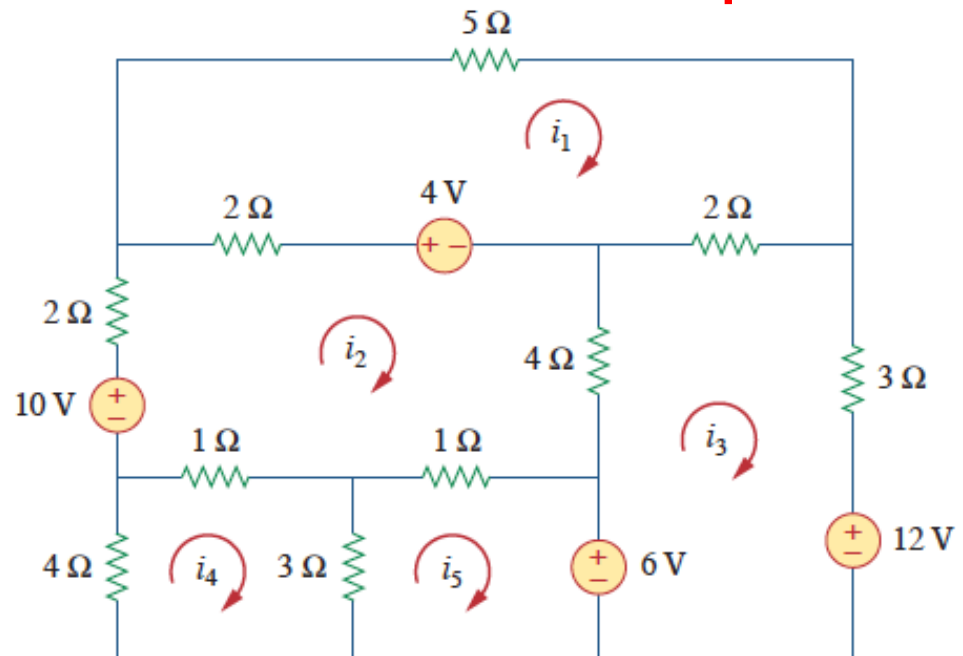


Figure 3.29

- Each **diagonal term** on the **resistance matrix** is the **sum of resistances in the mesh** indicated by the matrix index

Mesh Analysis by Inspection II

- The **off diagonal** terms, R_{jk} are the **negative** of the **sum** of all resistances in common with meshes j and k with $j \neq k$.
- The unknown mesh currents in the clockwise direction are denoted as i_k
- The **sum** taken **clockwise** of all **voltage sources** in **mesh k** are denoted as V_k . Voltage rises are treated as positive.
- This **matrix equation** can be solved for the values of the unknown **mesh currents**.

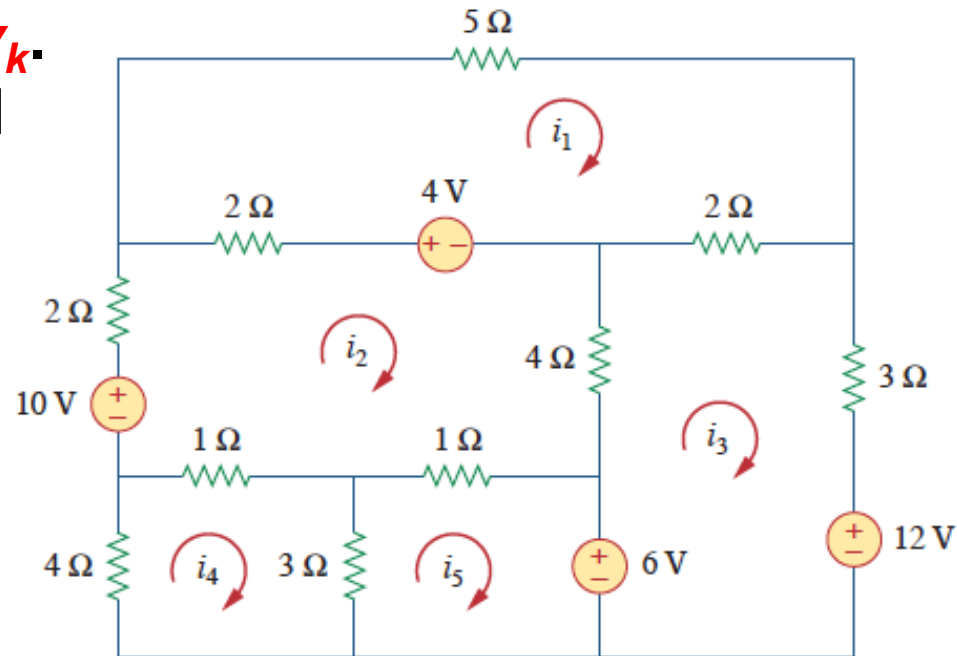


Figure 3.29

$$\begin{bmatrix} R_{11} & R_{12} & \cdots & R_{1N} \\ R_{21} & R_{22} & \cdots & R_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ R_{N1} & R_{N2} & \cdots & R_{NN} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_N \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_N \end{bmatrix}$$

diagonal

$$\begin{aligned} R_{11} &= 5 + 2 + 2 = 9, & R_{22} &= 2 + 4 + 1 + 1 + 2 = 10, \\ R_{33} &= 2 + 3 + 4 = 9, & R_{44} &= 1 + 3 + 4 = 8, \\ R_{55} &= 1 + 3 = 4 \end{aligned}$$

off diagonal R_{jk}

$$\begin{aligned} R_{12} &= -2, & R_{13} &= -2, & R_{14} &= 0 = R_{15}, \\ R_{21} &= -2, & R_{23} &= -4, & R_{24} &= -1, & R_{25} &= -1, \\ R_{31} &= -2, & R_{32} &= -4, & R_{34} &= 0 = R_{35}, \\ R_{41} &= 0, & R_{42} &= -1, & R_{43} &= 0, & R_{45} &= -3, \\ R_{51} &= 0, & R_{52} &= -1, & R_{53} &= 0, & R_{54} &= -3 \end{aligned}$$

Voltage Vector

$$\begin{aligned} v_1 &= 4, & v_2 &= 10 - 4 = 6, \\ v_3 &= -12 + 6 = -6, & v_4 &= 0, & v_5 &= -6 \end{aligned}$$

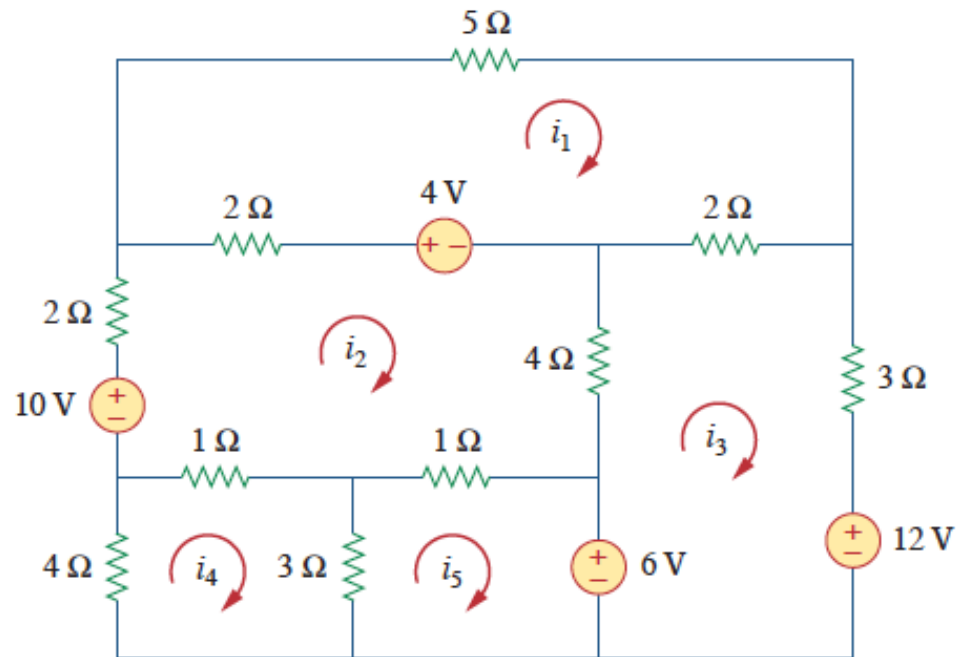


Figure 3.29

Mesh Current Equations

$$\begin{bmatrix} 9 & -2 & -2 & 0 & 0 \\ -2 & 10 & -4 & -1 & -1 \\ -2 & -4 & 9 & 0 & 0 \\ 0 & -1 & 0 & 8 & -3 \\ 0 & -1 & 0 & -3 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 4 \\ 6 \\ -6 \\ 0 \\ -6 \end{bmatrix}$$

Selecting an Appropriate Approach

- In principle both the **nodal analysis** and **mesh analysis** are useful for any given circuit.
- What then determines if one is going to be more efficient for solving a circuit problem?
- There are two factors that dictate the best choice:
 - ✓ The **nature** of the particular network is the first factor
 - ✓ The second factor is the **information** required

Mesh analysis when...

- If the network contains:
 - ✓ Many **series** connected elements
 - ✓ **Voltage** sources
 - ✓ **Supermeshes**
 - ✓ A circuit with **fewer meshes than nodes**
- If **branch** or **mesh currents** are what is being solved for.
- Mesh analysis is the only suitable analysis for **transistor circuits**
- It is **not** appropriate **for operational amplifiers** because there is no direct way to obtain the voltage across an op-amp.

Nodal analysis if...

- If the network contains:
 - ✓ Many **parallel** connected elements
 - ✓ **Current sources**
 - ✓ **Supernodes**
 - ✓ Circuits with **fewer nodes than meshes**
- If **node voltages** are what are being solved for
- **Non-planar** circuits can only be solved using **nodal** analysis
- This format is easier to solve by computer