

Name: _____ No: _____


Instructor: Shyan-Lung Lin, Prof.

FCU ISTM -PU 2+2 Program

13:10~15:00 pm, Nov. 9, 202


Note: Open text book. Please show organized math works, and make the calculation to its final form and with an accuracy of at least 4th digit behind decimal point.

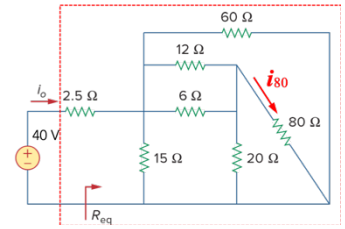1. 15% Find R_{eq} (including 2.5Ω), i_o , and i_{80} in the circuit of Figure 1.




2. 30% Given the circuit in Figure 2,

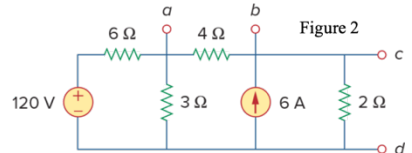- (A) (15%) apply the **Thevenin** theorem to obtain the **Thevenin** equivalent V_{Th} and R_{Th} , and find the maximal power that can be transferred to the load as viewed from terminal **a-b**;
- (B) (15%) apply the **Norton** theorem to obtain the **Norton** equivalent I_N and R_N , and find the maximal power that can be transferred to the load as viewed from terminal **c-d**.




3. 30% For the circuit in Figure 3, at terminals **a-b**,

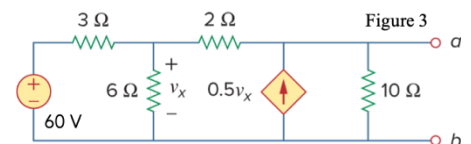
- (A) (15%) use the **Thevenin** theorem to obtain the **Thevenin** equivalent
- (B) (15%) use the **Norton** theorem to obtain the **Norton** equivalent



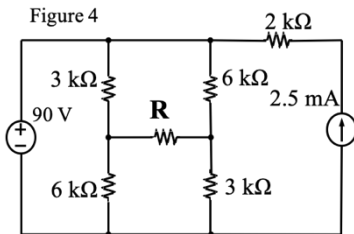4. 20% For the circuit shown in Figure 4, if the current passing through the unknown resistor \mathbf{R} is 0.5 mA, find the value of \mathbf{R} .



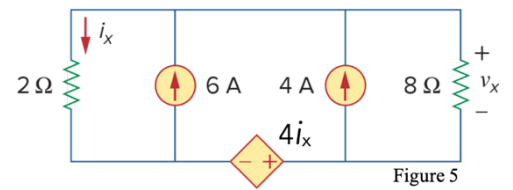5. 20% Use **superposition** to solve for $\mathbf{v_x}$ in the circuit of Figure 5.



6. 20% Use **mesh** analysis and apply **Cramer's** rule to obtain $\mathbf{i_o}$ in the circuit of Figure 6.

