

Feng Chia University
Electrical Engineering Fundamentals I Lab

Laboratory 2
Equivalent Circuit

Instructor: Prof. Shyan-Lung Lin

Student Name: 周嘉禾

Student ID: D1166506

Experiment Date: 23/11/2023


I. Introduction

- To be familiar with Thevenin equivalent, Norton equivalent
- To be familiar with maximum power transfer theorem


II. Materials

- Digital Multimeter
- Triple Output Power Supply
- Resistors
 - $2\text{ k}\Omega \times 2$, $5.6\text{ k}\Omega$, $1\text{ k}\Omega$
 - $100\text{ }\Omega$, $1\text{ k}\Omega$, $2.2\text{ k}\Omega$, $10\text{ k}\Omega$

III. Circuit diagram

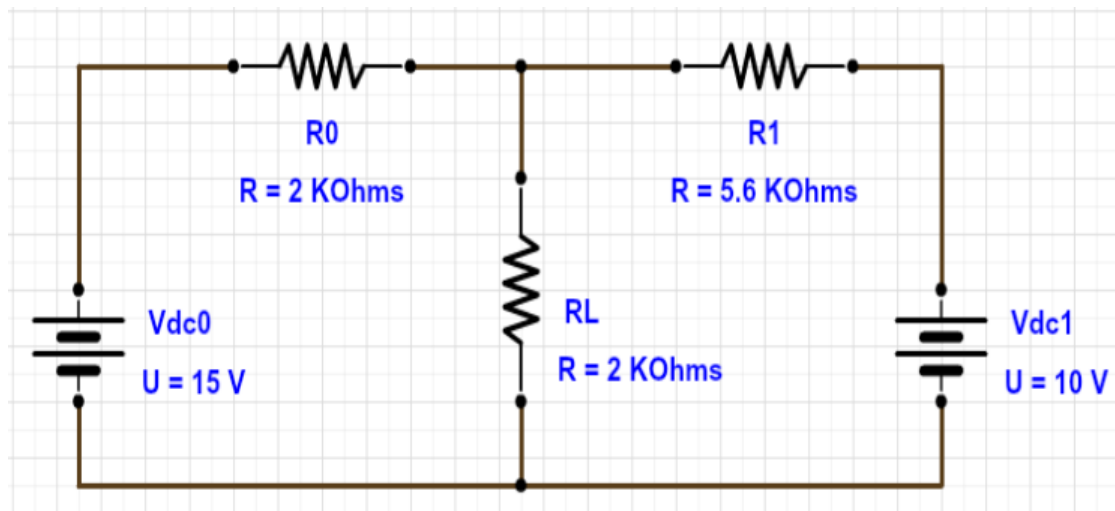

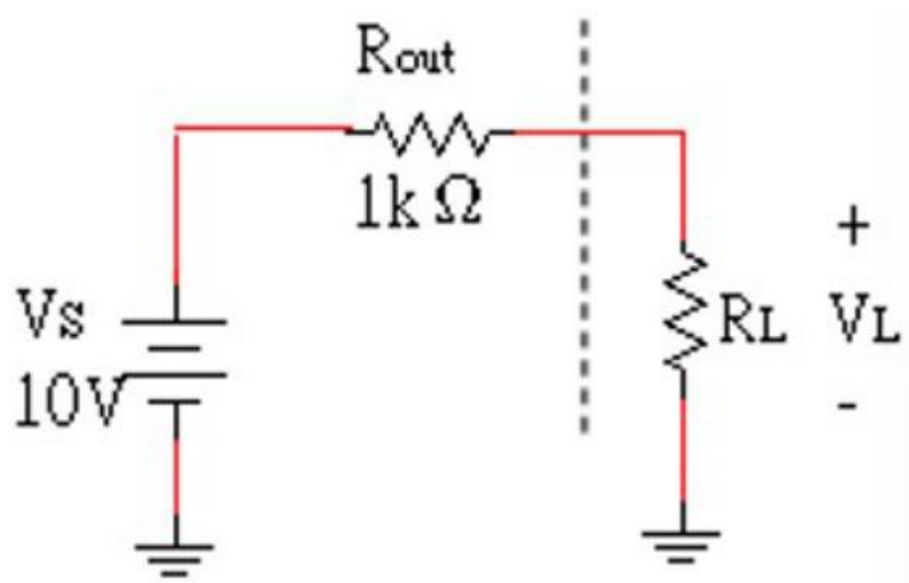▲ Figure 1. Circuit of Experiment 2.a Examples of Thevenin equivalent



▲ Figure 2. Circuit of Experiment 2.b Maximum power transfer theorem

IV. Methods

V. Experiments data

a. Experiment 2.a

Table 1: Results of the V_{Th} and R_{Th} Measurements


	Practical	Theorem	% Error
V_{Th}	13.8700 V	13.6842 V	1.36%
R_{Th}	1.5007 k Ω	1.4737 k Ω	1.83%

b. Experiment 2.b


Table 2: Results of the V_L and I_L Measurements, and calculation of P_L

R_L	100 Ω	1 k Ω	2.2 k Ω	10 k Ω
V_L	0.9049 V	4.9905 V	6.8624 V	9.0906 V
I_L	9.2188 mA	5.0675 mA	3.1713 mA	0.9176 mA
P_L	8.3421 mW	25.2894 mW	21.7627 mW	8.3415 mW

VI. Results

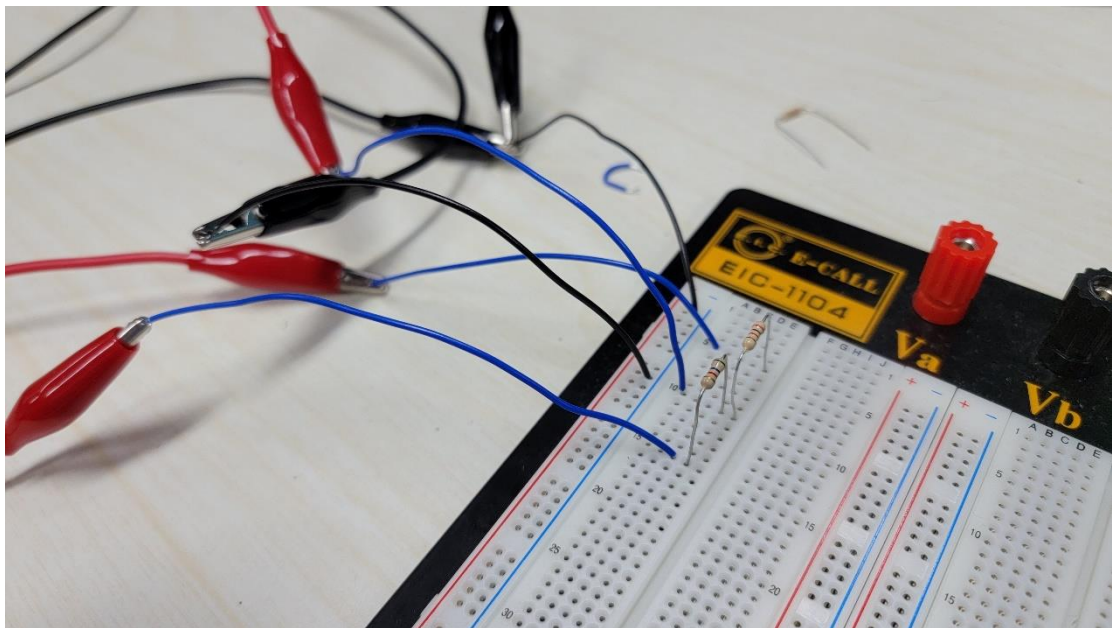

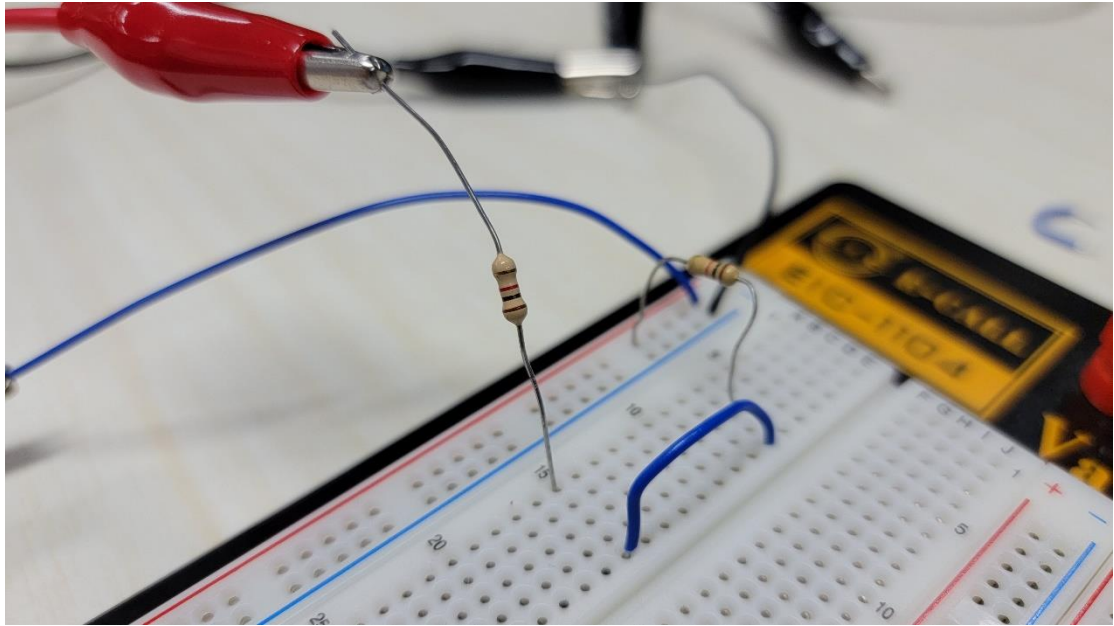▲ Figure 3. Photo of Experiment 2.a Examples of Thevenin equivalent



▲ Figure 4. Photo of Experiment 2.b Maximum power transfer theorem

VII. Discussion

With the R_L closing to R_{out} , the power dissipation will be maximum and become larger than the R_L away from R_{out} .

VIII. Conclusion

By measuring the equivalent circuit, it's easy to understand the Thevenin and Norton equivalent and maximum power transfer theorem.