
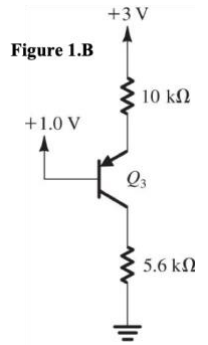




Name:

Note: Show detailed and organized mathematic works. Make your calculation accuracy to at least the 4th digit behind the decimal point.


1. (20%) For each of the circuits in Figure 1, Use, assuming the transistor is to have $\beta = 50$ and $|V_{BE}| = 0.7\text{V}$ independent of the current level, derive the node voltages and branch currents.

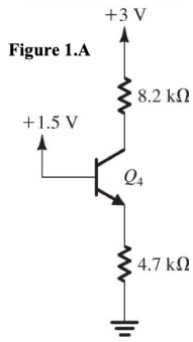


2. (20%) For the circuits in Figure 2, assuming the transistor is to have $\beta = 100$, $|V_{BE(\text{active})}| = |V_{BE(\text{sat})}| \cong 0.7\text{ (V)}$, and $|V_{CE(\text{sat})}| \cong 0.2\text{ (V)}$. Some Measurements have been made on these circuits, with the results indicated in the figure. Find the values of the other labeled voltages and currents (V_1 , I_1 , V_2 , I_2).

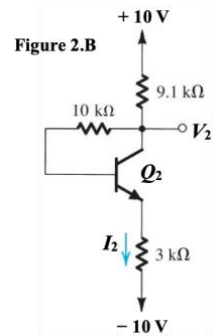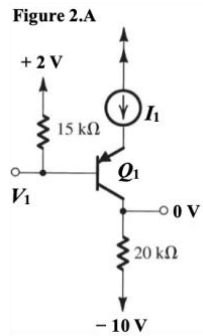

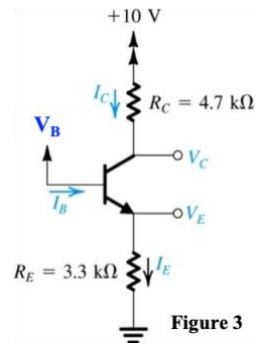3. (35%) For the circuit in Figure 3, assuming the transistor is to have $\beta = 50$, $V_{BE(\text{active})} \cong 0.7\text{ (V)}$, $V_{BE(\text{sat})} \cong 0.8\text{ (V)}$, and $V_{CE(\text{sat})} \cong 0.2\text{ (V)}$, $V_{CE(\text{EOS})} \cong 0.3\text{ (V)}$.
- (A) (10%) With $V_B = 4\text{ V}$, find all branch currents and node voltages.
- (B) (15%) With $V_B = 8\text{ V}$, find all branch currents and node voltages, and also β_{force} to verify that the transistor is in **saturation**.
- (C) (10%) Find the $V_{B(\text{min})}$ and $I_{B(\text{min})}$ required to drive the transistor into **the edge of saturation**.



4. (30%) In the circuit of Fig. 3, the transistor has $\beta = 40$, $|V_{BE(\text{active})}| = |V_{BE(\text{sat})}| \cong 0.7 \text{ (V)}$, and $|V_{CE(\text{sat})}| \cong 0.2 \text{ (V)}$.
- (A) (10%) Find the values of V_B , V_E , and V_C .
- (B) (10%) If R_B is raised to **100 k Ω** , what voltages (V_B , V_E , and V_C) result?
- (C) (10%) With R_B =**100 k Ω** , what value of β for replaced Q would return the voltages to the values first calculated in (A)?

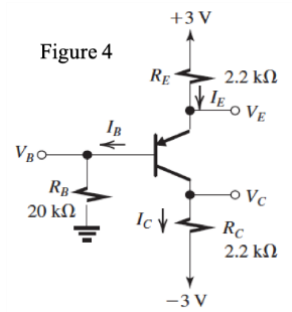

5. (30%) Assume $\beta = 100$, $|V_{BE(\text{active})}| \cong |V_{BE(\text{sat})}| \cong 0.7 \text{ (V)}$, and $|V_{CE(\text{sat})}| \cong 0.2 \text{ (V)}$ for Q_1 and Q_2 in the circuit of Figure 5, based on the defined current directions, evaluate I_B , I_L , I_{C1} , I_{C2} , and V_O with (A) $V_I = 10 \text{ V}$, (B) $V_I = 0 \text{ V}$, (C) $V_I = -5 \text{ V}$.

