
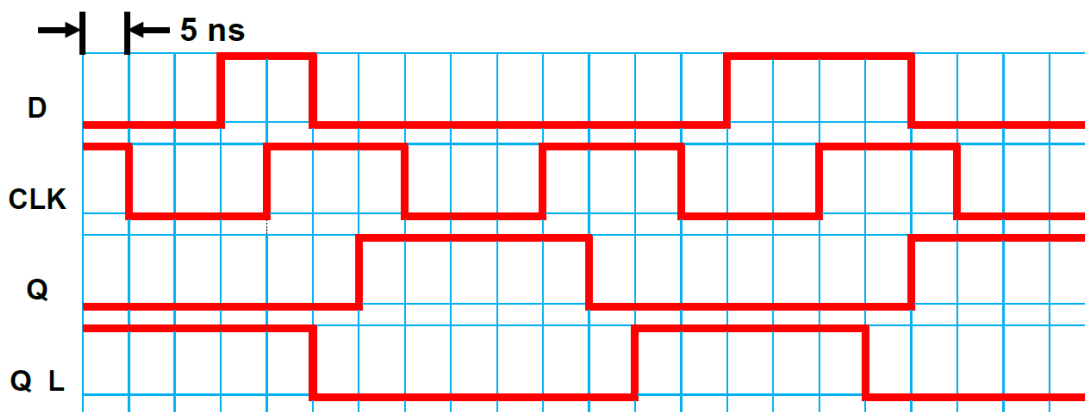


ISTM 214 Homework 8 (Due day: 12/13)

Name: _____


ID: _____

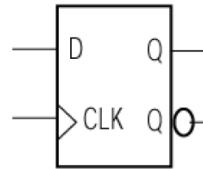
1. Given the following timing chart for an edge-triggered D flip-flop, determine the following parameters based on the excitation signals (D and CLK) depicted:



- The nominal setup time provided for the D flip-flop
 - The nominal hold time provided for the D flip-flop
 - The nominal clock pulse width provided for the D flip-flop
 - The $t_{PHL}(C \rightarrow Q)$ of the D flip-flop
 - The $t_{PLH}(C \rightarrow Q)$ of the D flip-flop
2. What Given the following circuit diagram, determine the next state equations it realizes in minimum sum-of-products form.

X(t)	Y(t)	A(t)	B(t)	X(t+τ)	Y(t+τ)
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

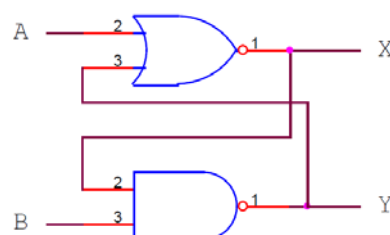

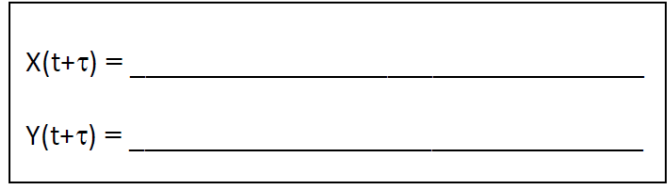

```

graph TD
    00((00)) -- "dd" --> 01((01))
    01 -- "10" --> 10((10))
    10 -- "0d" --> 01
    01 -- "00" --> 01
    11((11)) -- "d0" --> 01
    01 -- "01" --> 11
    10 -- "1d" --> 10
    11 -- "d1" --> 10
    XY((X Y)) -- "A B" --> Out(( ))
  
```

