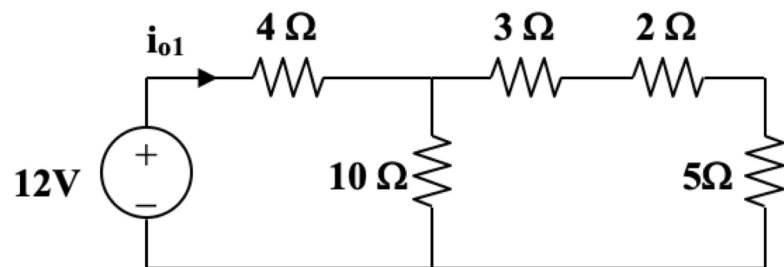


112-1
Electrical Engineering Fundamentals I

Quiz 4
Keys

1. 30% Use superposition to obtain i_o for the circuit of Fig. 1.

$i_o = i_{o1} + i_{o2} + i_{o3}$ due to the 12-V, 4-A, and 2-A sources



$$R_{eq} = 4 + 10 \parallel (3 + 2 + 5) = 9(\Omega)$$

$$i_{o1} = \frac{12}{9} = 1.3333(A)$$


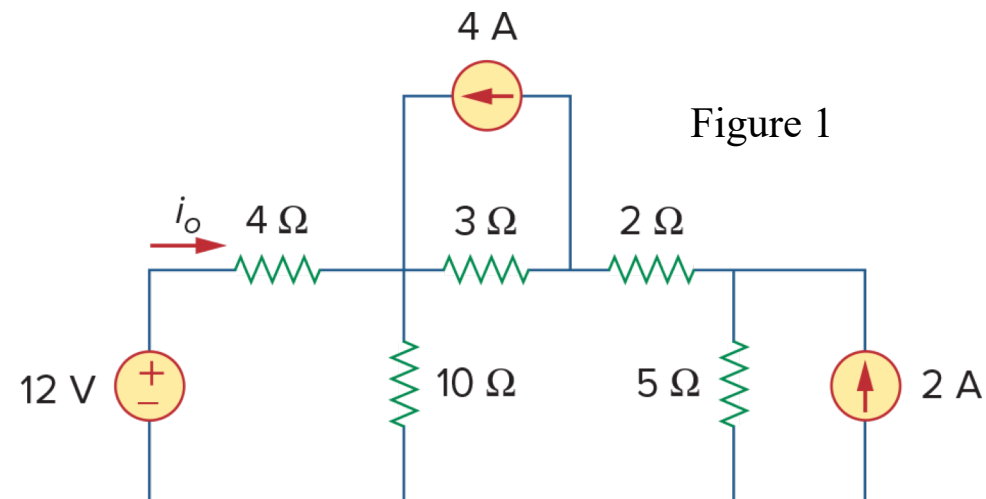



Figure 1

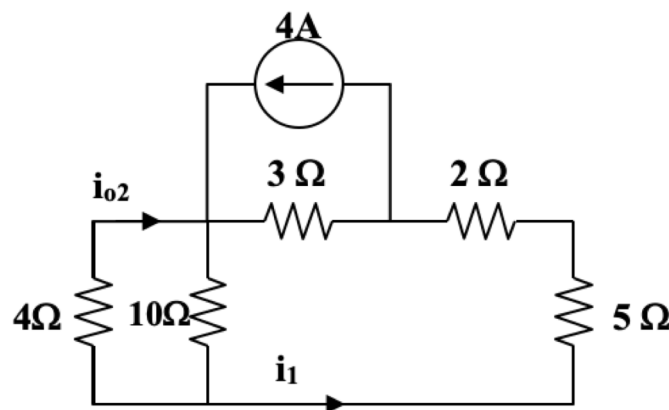

$$R_{eq} = 2 + 5 + 4 \parallel 10 = \frac{69}{7} = 9.8571(\Omega)$$

$$i_1 = 4 \times \frac{3}{3 + 9.8571} = 0.9333(A)$$
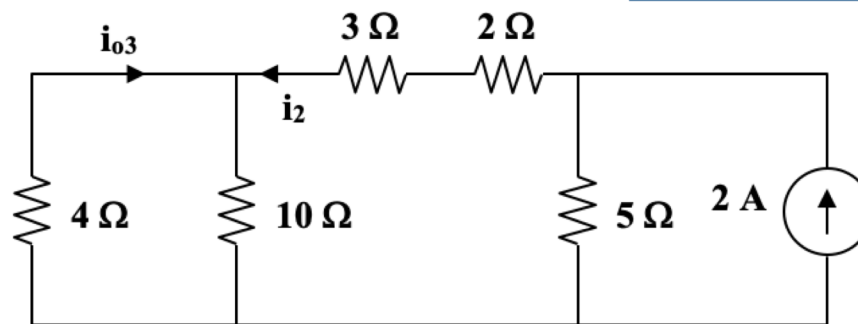
$$i_{o2} = -i_1 \times \frac{10}{10 + 4} = -0.6666(A)$$



$$R_{eq} = 2 + 3 + 4 \parallel 10 = \frac{55}{7} = 7.8571(\Omega)$$



$$i_2 = 2 \times \frac{5}{5 + 7.8571} = 0.7778(A)$$

$$i_{o3} = -i_2 \times \frac{10}{10 + 4} = -0.5556(A)$$

$$\begin{aligned} i_o &= i_{o1} + i_{o2} + i_{o3} \\ &= 1.3333 - 0.6666 - 0.5556 = 0.1111(A) \end{aligned}$$

2. 20% Use *source transformation* to obtain v_o in the circuit of Fig.
 2. (Redraw the equivalent circuit as you convert the source.)

Applying KVL to the loop gives,

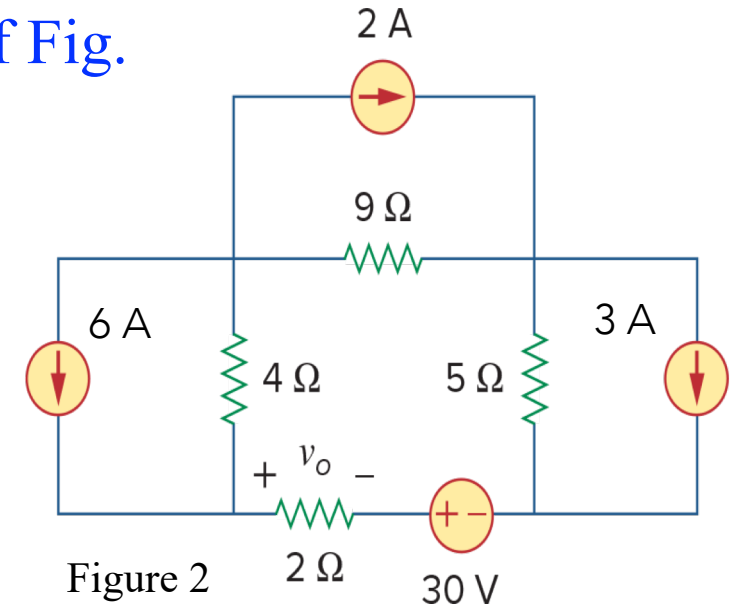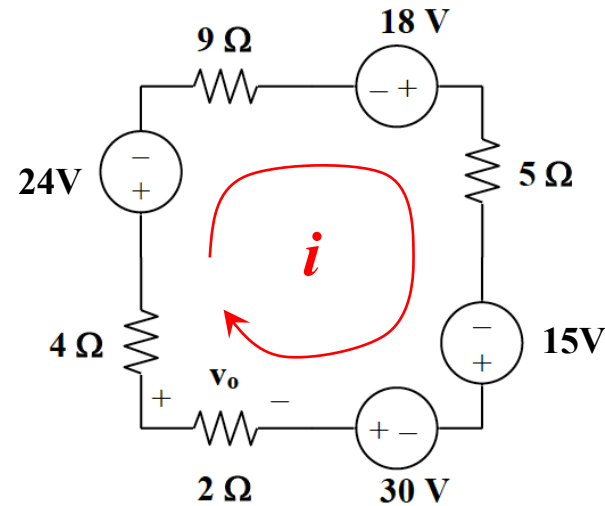


$$(9 + 5 + 2 + 4) \cdot i - 18 - 15 - 30 + 24 = 0$$

$$\Rightarrow i = \frac{39}{20} = 1.95 \text{ (A)}$$

$$\Rightarrow v_o = -i \times 2 = -3.9 \text{ (V)}$$

3. 30% In the circuit of Fig. 3, use Thevenin theorem to find the V_{Th} and R_{Th} across the terminal a-b.

Find R_{Th}

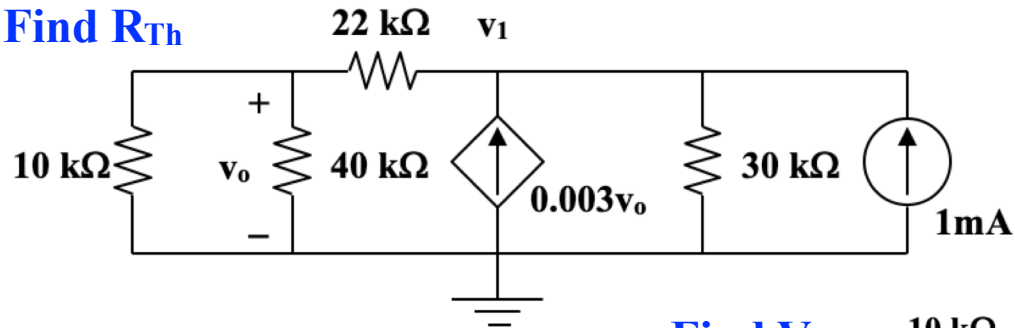

$$R_{eq} = 22 + 10 \parallel 40 = 30(k\Omega)$$

Nodal analysis on v_1 :

$$\frac{v_1}{30} + \frac{v_1}{30} = 1 + 3 \cdot v_o$$

$$\rightarrow v_1 = 15 + 45v_o$$

$$v_o = v_1 \times \frac{10 \parallel 40}{22 + 10 \parallel 40} = \frac{4v_1}{15}$$

$$\Rightarrow v_1 = 15 + 45v_o$$

$$= 15 + 45 \times \frac{4}{15} v_1$$

$$\Rightarrow v_1 = -\frac{15}{11} = -1.3636(V)$$

$$R_{Th} = \frac{v_1}{i} = -1.3636(k\Omega)$$


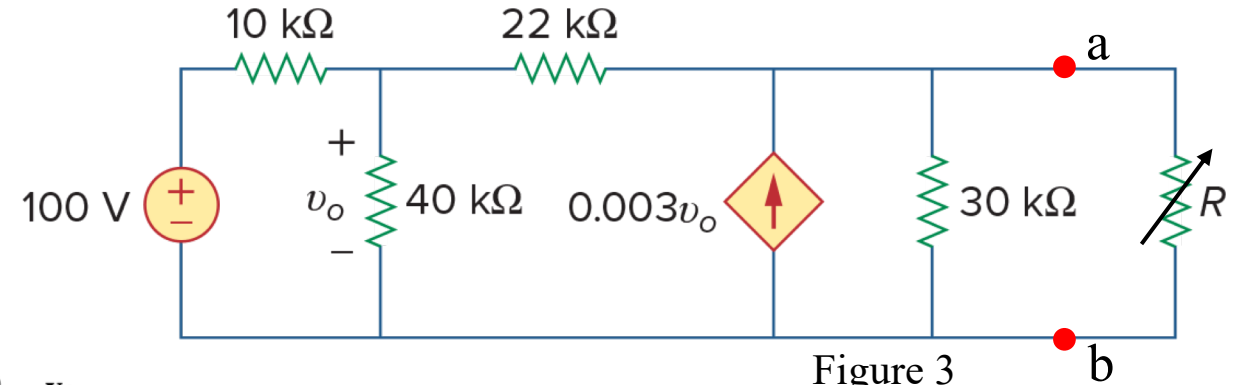


Figure 3

Find V_{Th}

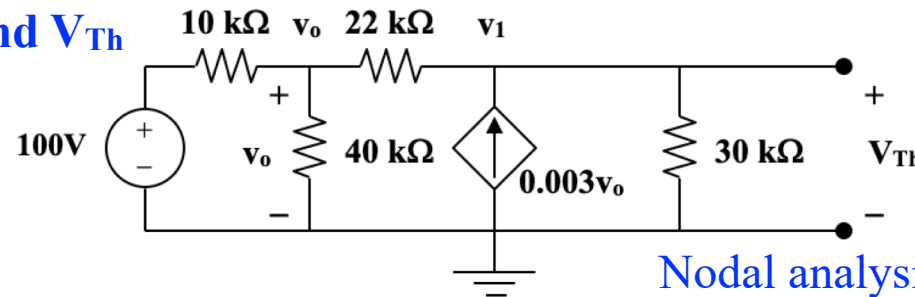

Nodal analysis on v_o :

$$\frac{100 - v_o}{10} = \frac{v_o}{40} + \frac{v_o - v_1}{22} \dots\dots (1)$$

$$\frac{v_o - v_1}{22} + 3 \cdot v_o = \frac{v_1}{30} \dots\dots\dots (2)$$

$$\Rightarrow 75v_o - 20v_1 = 4400$$

$$2010v_o - 52v_1 = 0$$

$$\Rightarrow v_1 = -243.6364(V)$$

$$v_o = -6.3030(V)$$

$$V_{Th} = v_1 = -243.6364(V)$$

4. 30% For the circuit in Fig. 4,

- (A) 10% Use the Norton theorem to obtain equivalent circuit (find I_{SC} and R_N , and draw the Norton equivalent circuit)) at terminals a-b
- (B) 10% Convert the Norton equivalent circuit of (A) into its Thevenin's form.
- (C) 10% As the circuit is connected to a load, what is the maximal power that can be transferred to the load?

