

112-1
Electrical Engineering Fundamentals I

Quiz 6
Keys

1. 30% Obtain i_1 and i_2 for $t > 0$ in the circuit of Figure 1.

At $t < 0$, $4u(t) = 0$, L shorted

$$i_1(0^-) = i_2(0^-) = 0 \text{ (A)}$$

At $t > 0$, $4u(t) = 4 \text{ (A)}$

Nodal analysis:

$$4 = \frac{1}{2} \times 1 \times \frac{di_1}{dt} + i_1 + i_2$$

$$\Rightarrow \frac{di_1}{dt} + 2i_1 + 2i_2 = 8$$

$$\Rightarrow \frac{d^2i_1}{dt^2} + 2\frac{di_1}{dt} + 2\frac{di_2}{dt} = 0$$

$$i_2 = \frac{v_{L1} - v_{L2}}{3}$$

$$\Rightarrow 3i_2 = \frac{di_1}{dt} - \frac{di_2}{dt}$$

$$\begin{aligned} \Rightarrow \frac{di_2}{dt} &= \frac{di_1}{dt} - 3i_2 \\ &= \frac{di_1}{dt} - 3\left(4 - \frac{1}{2}\frac{di_1}{dt} - i_1\right) \end{aligned}$$

$$\frac{d^2i_1}{dt^2} + 2\frac{di_1}{dt} + 2\frac{di_2}{dt} = 0$$

$$\Rightarrow \frac{d^2i_1}{dt^2} + 2\frac{di_1}{dt} + 2\left(\frac{di_1}{dt} - 12 + \frac{3}{2}\frac{di_1}{dt} + 3i_1\right) = 0$$

$$\Rightarrow \frac{d^2i_1}{dt^2} + 7\frac{di_1}{dt} + 6i_1 = 24$$

$$\Rightarrow s^2 + 7s + 6 = 0$$

$$\Rightarrow s = -1, -6$$

$$i_1(0) = i_1(0^+) = i_1(0^-) = 0 \text{ (A)}$$

$$i_2(0) = i_2(0^+) = i_2(0^-) = 0 \text{ (A)}$$

$$\frac{di_1}{dt} + 2i_1 + 2i_2 = 8 \Rightarrow \frac{di_1}{dt} = 8 - 2i_1 + 2i_2$$

$$\Rightarrow \frac{di_1(0)}{dt} = 8 - 2i_1(0) + 2i_2(0) = 8 \text{ (A/s)}$$

$$i_1(\infty) = 4 \text{ (A)} \Rightarrow I_{1SS} = 4 \text{ (A)}$$

$$i_1(t) = I_{1SS} + Ae^{s_1t} + Ae^{s_2t} = 4 + Ae^{-t} + Be^{-6t}$$

$$\frac{di_1}{dt} = -Ae^{-t} - 6Be^{-6t}$$

$$i_1(0) \rightarrow 4 + A + B = 0 \Rightarrow A + B = -4$$

$$\frac{di_1(0)}{dt} \rightarrow -A - 6B = 8$$


$$\Rightarrow \begin{cases} A = -3.2 \\ B = -0.8 \end{cases}$$

$$i_1(t) = 4 - 3.2e^{-t} - 0.8e^{-6t} \text{ (A)}$$

$$\frac{di_1}{dt} + 2i_1 + 2i_2 = 8 \Rightarrow i_2 = 4 - i_1 - 0.5\frac{di_1}{dt}$$

$$i_2(t) = 4 - (4 - 3.2e^{-t} - 0.8e^{-6t}) - 0.5(3.2e^{-t} + 4.8e^{-6t})$$
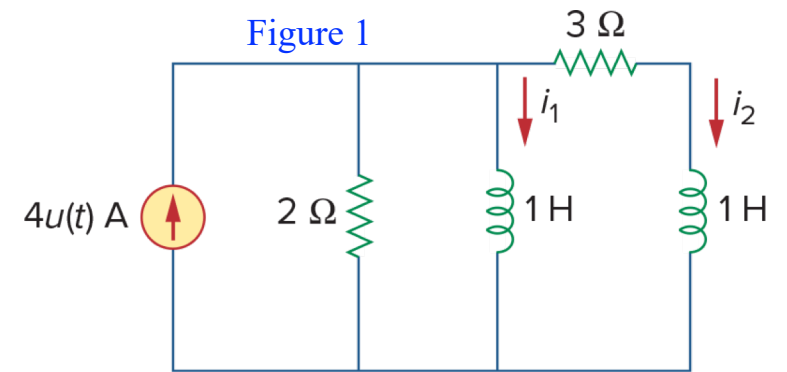
$$\begin{aligned} i_2(t) &= 1.6e^{-t} - 1.6e^{-6t} \\ &= 1.6(e^{-t} - e^{-6t}) \text{ (A)} \end{aligned}$$



2. 25% Find α and ω_0 and calculate $v(t)$ for $t > 0$ in the circuit of Fig. 2.

At $t < 0$, sw closed, L shorted & C opened

$$v_C(0^-) = 24 \times \frac{60 \parallel (15 + 25)}{12 + 60 \parallel (15 + 25)} = 24 \times \frac{24}{12 + 24} = 16 \text{ (V)}$$

$$i_L(0^-) = 0 \text{ (A)}$$

For $t > 0$, sw opened, Series RLC circuit

$$R_{eq} = 6 + 60 \parallel (15 + 25) = 6 + 24 = 30 \Omega$$

$$\alpha = \frac{R}{2L} = \frac{30}{2 \times 3} = 5$$

$$\omega_0 = \frac{1}{\sqrt{3 \times \frac{1}{27}}} = 3 \quad \alpha > \omega_0$$

\Rightarrow system is *overdamped*

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5 \pm \sqrt{5^2 - 3^2} = -9, -1$$

$$i(t) = A_1 e^{-9t} + A_2 e^{-t}$$

$$\frac{di}{dt} = -9A_1 e^{-9t} - A_2 e^{-t}$$

$$i(0) = A_1 + A_2 = 0 \dots (1)$$

$$\frac{di(0)}{dt} = -9A_1 - A_2 = \frac{-16}{3} \dots (2)$$

$$\Rightarrow \begin{cases} A_1 = \frac{2}{3} \\ A_2 = -\frac{2}{3} \end{cases}$$

$$i(t) = A_1 e^{-9t} + A_2 e^{-t}$$

$$= \frac{2}{3} e^{-9t} - \frac{2}{3} e^{-t}$$



$$v(t) = -v_L(t) - i(t) \times 30$$

$$= -L \frac{di(t)}{dt} - 30i(t)$$

$$= -3 \left(-6e^{-9t} + \frac{2}{3} e^{-t} \right) - 20e^{-9t} + 20e^{-t}$$

$$= -2e^{-9t} + 18e^{-t}$$

Figure 2

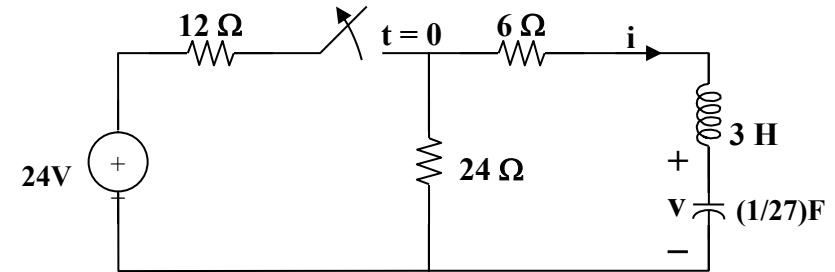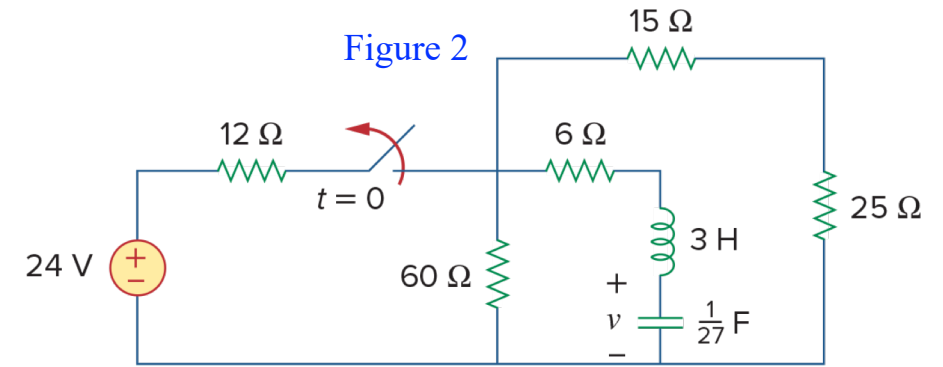

$$v_C(0^+) = v_C(0^-) = 16 \text{ (V)}$$

$$i(0^+) = i_L(0^+) = i_L(0^-) = 0 \text{ (A)}$$

$$v_L(0^+) = -i(0^+) \times (6 + 24) - v_C(0^+)$$

$$= -0 \times (6 + 24) - 16 \text{ (V)}$$


$$\frac{di(0^+)}{dt} = \frac{1}{L} v_L(0^+) = \frac{-16}{3} \text{ (V)}$$

3. 45% For each of the circuits Fig. 3.A~3.C, assume all diodes are *ideal*.

(A) Derive v_O in terms of v_I ;



(B) Sketch transfer characteristics v_O vs v_I ;

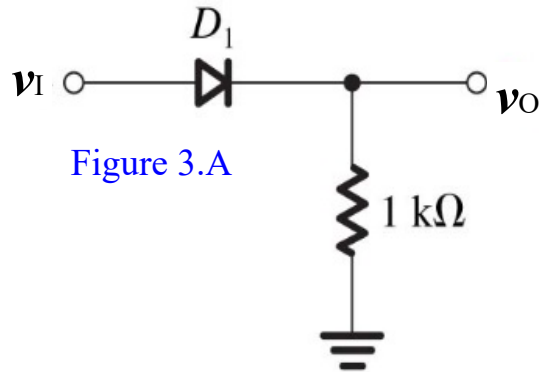(C) Draw output waveforms $v_O(t)$, as v_I is a 1-kHz, 5-V peak sine wave.





$$\begin{cases} \text{As } v_I \geq 0 \rightarrow D_1 \text{ on} \rightarrow v_O = v_I \\ \text{As } v_I \leq 0 \rightarrow D_1 \text{ off} \rightarrow v_O = 0 \end{cases}$$
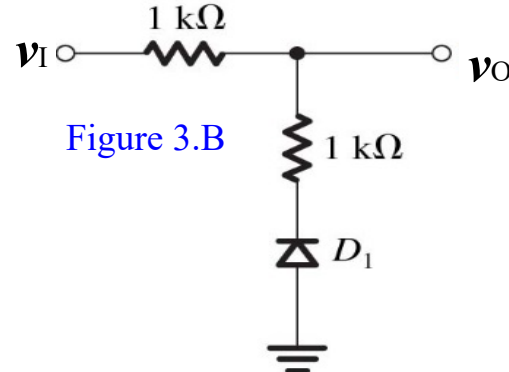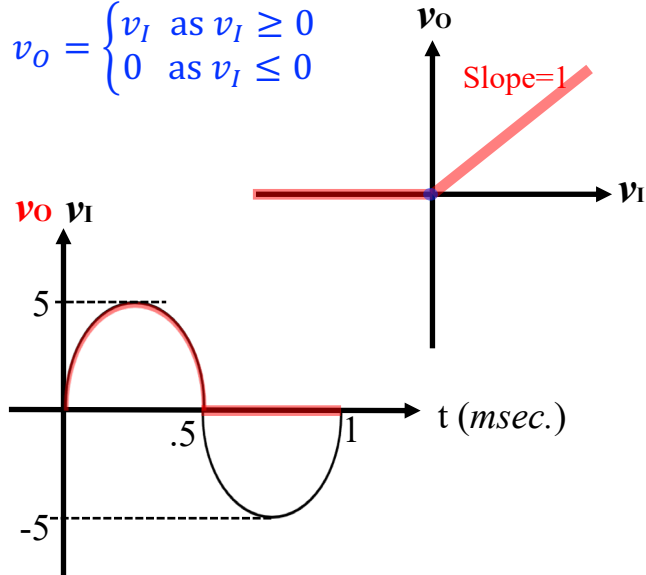
$$\Rightarrow v_O = \begin{cases} v_I & \text{as } v_I \geq 0 \\ 0 & \text{as } v_I \leq 0 \end{cases}$$





$$\begin{cases} \text{As } v_I \geq 0 \rightarrow D_1 \text{ off} \rightarrow v_O = v_I \\ \text{As } v_I \leq 0 \rightarrow D_1 \text{ on} \rightarrow v_O = v_I \times \frac{1}{1+1} = \frac{1}{2} \cdot v_I \end{cases}$$
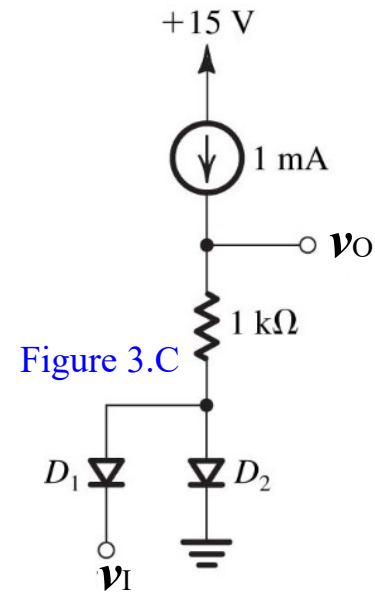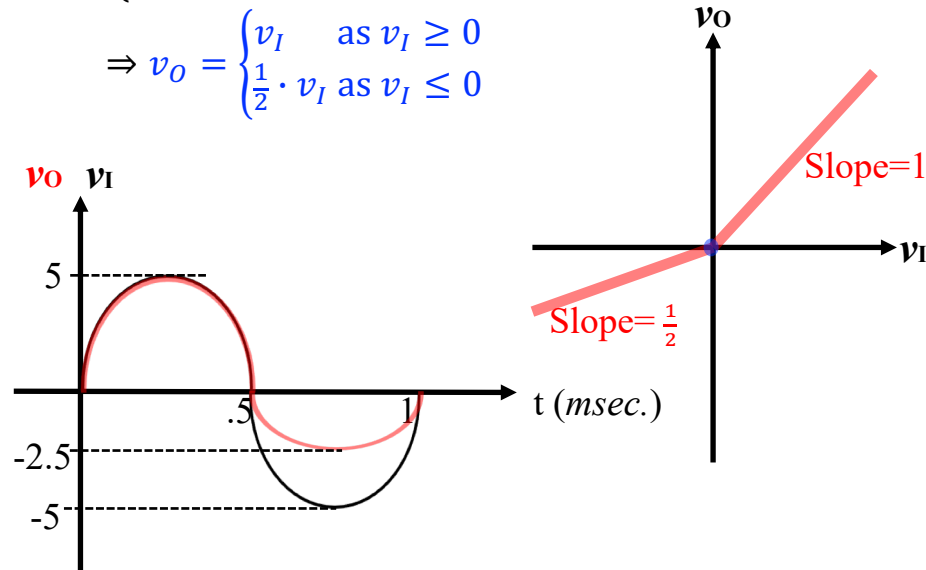
$$\Rightarrow v_O = \begin{cases} v_I & \text{as } v_I \geq 0 \\ \frac{1}{2} \cdot v_I & \text{as } v_I \leq 0 \end{cases}$$











$$\begin{cases} \text{As } v_I \geq 0 \rightarrow D_1 \text{ off}, D_2 \text{ on} \\ \text{As } v_I \leq 0 \rightarrow D_1 \text{ on}, D_2 \text{ off} \end{cases}$$
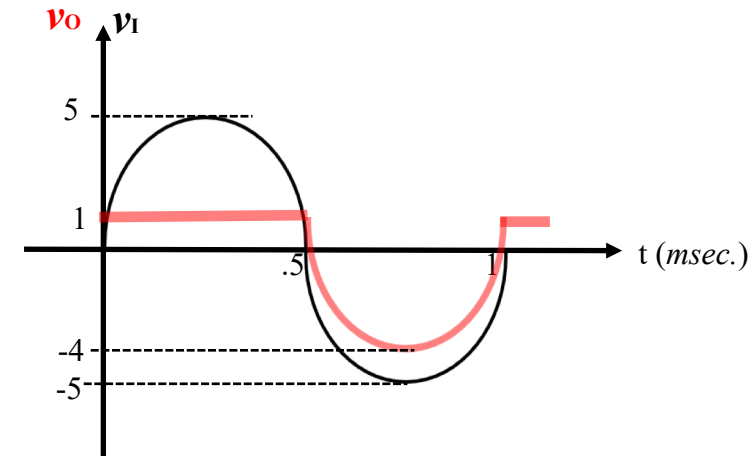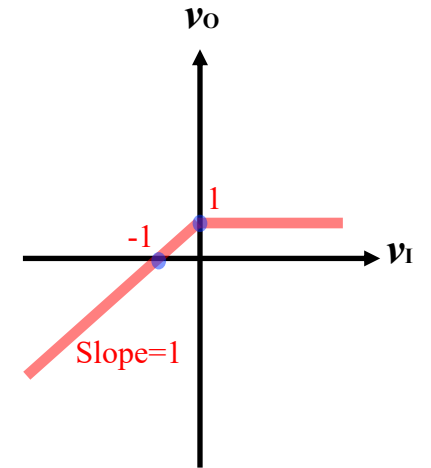
$$\Rightarrow v_O = \begin{cases} 1(mA) \times 1(k\Omega) = 1(V) & \text{as } v_I \geq 0 \\ 1 \times 1 + v_I = 1 + v_I & \text{as } v_I \leq 0 \end{cases}$$



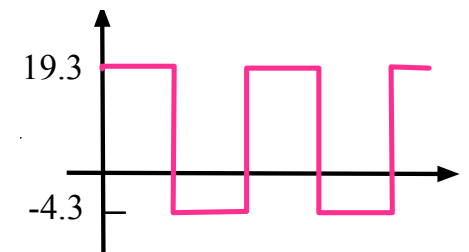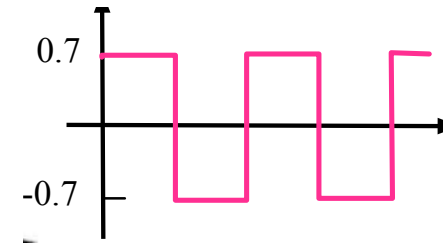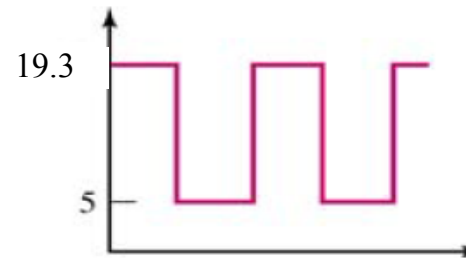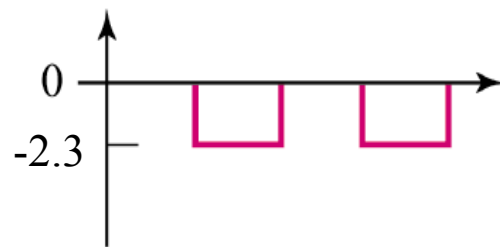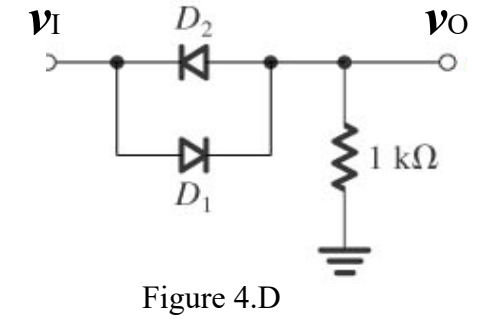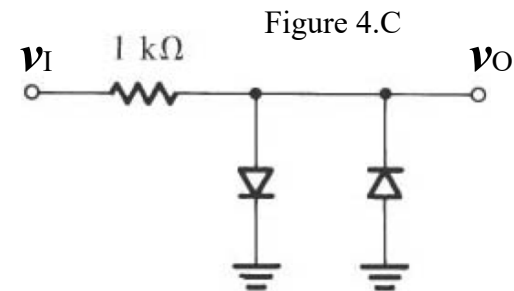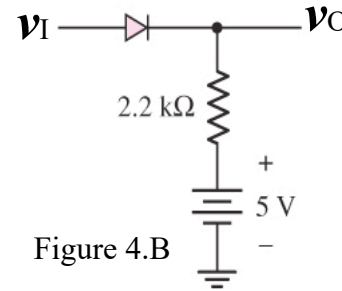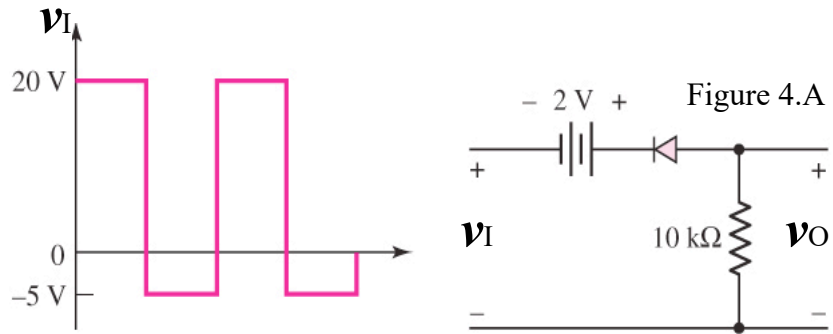4. 20% Assume the diodes have a constant voltage drop $V_D=0.7$ (V) while conducting (Constant voltage drop model). For Figure 4.A~D, with the shown input v_I , sketch the output waveform v_O .



5. 20% In Figure 5, assuming that the diodes are ideal, find V and I for the circuit Figure 5.A and 5.B.

(a) Assume $\begin{cases} D_1 \\ D_2 \end{cases}$ are both on

$$\Rightarrow V_A = 0 \text{ and } V = V_A = 0$$

$$\Rightarrow I_{12k} = \frac{3 - V_A}{12k} = \frac{3 - 0}{12k} = 0.25(\text{mA})$$

$$\Rightarrow I_{D2} = I_{6k} = \frac{V - (-3)}{6k} = \frac{0 + 3}{6k} = 0.5(\text{mA})$$

$$\Rightarrow I = I_{12k} - I_{6k} = 0.25 - 0.5 = -0.25(\text{mA})$$

\Rightarrow Impossible



\Rightarrow assumption on D_1 is incorrect

$$\Rightarrow \begin{cases} D_1 \text{ is off} \\ D_2 \text{ is on} \end{cases} \Rightarrow I = 0$$

$$\Rightarrow I_{12k} = I_{D2} = I_{6k} = \frac{3 - (-3)}{12k + 6k} = \frac{1}{3}(\text{mA}) = 0.3333(\text{mA})$$

$$\Rightarrow V = I_{6k} \times 6(k) + (-3) = \frac{1}{3}(\text{mA}) \times 6(k) - 3 = -1(V)$$
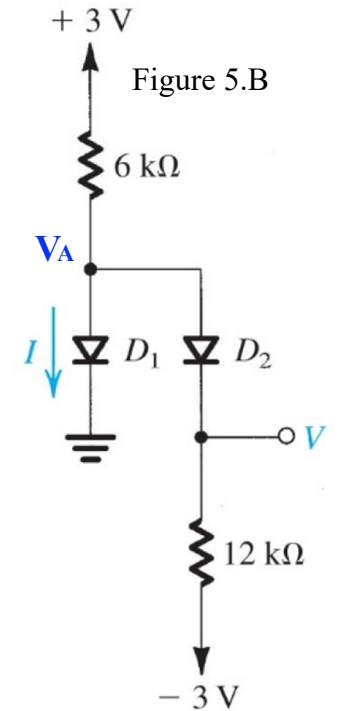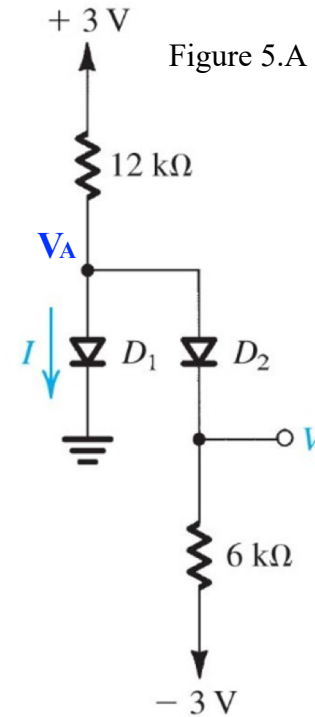
$$\Rightarrow \begin{cases} I = 0 \\ V = -1(V) \end{cases}$$



(b) Assume $\begin{cases} D_1 \\ D_2 \end{cases}$ are both on

$$\Rightarrow V_A = 0 \text{ and } V = V_A = 0$$

$$\Rightarrow I_{6k} = \frac{3 - V_A}{6k} = \frac{3 - 0}{6k} = 0.5(\text{mA})$$

$$\Rightarrow I_{D2} = I_{12k} = \frac{V - (-3)}{12k} = \frac{0 + 3}{12k} = 0.25(\text{mA}) \text{ assumption is correct!}$$

$$\Rightarrow I = I_{6k} - I_{12k} = 0.5 - 0.25 = 0.25(\text{mA})$$

$$\Rightarrow \begin{cases} I = 0.25(\text{mA}) \\ V = 0(V) \end{cases}$$