

112-1  
Electrical Engineering Fundamentals I

Quiz 5  
Keys


1. 15% (A) The voltage  $v_C(t)$  across a 10-mF capacitor is shown in Fig. 1(A), determine the current  $i_C(t)$  through the capacitor.

15% (B) If the voltage  $v_L(t)$  waveform in Fig. 1(B) is applied to a 10-mH inductor, find the inductor current  $i_L(t)$  for  $0 < t < 2$  (s). Assume  $i_L(0)=0$ .

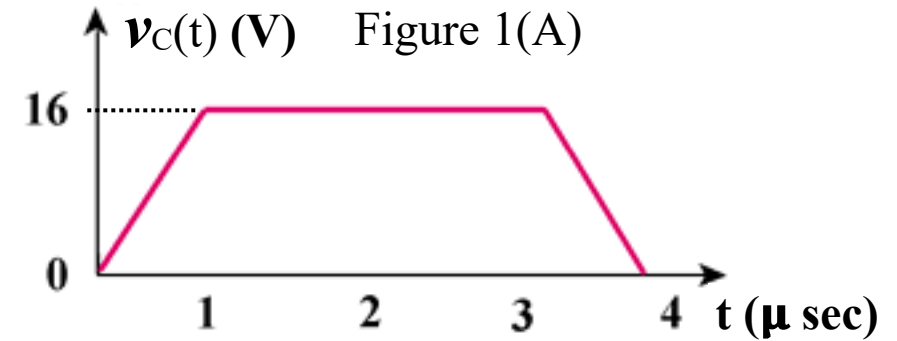**(A)  $C = 10$  (mF)**

$$v(t) = \begin{cases} 16 \times 10^6 \cdot t & 0 < t < 1 \mu s \\ 16 & 1 < t < 3 \mu s \\ 64 - 16 \times 10^6 \cdot t & 3 < t < 4 \mu s \end{cases} \quad \frac{dv}{dt} = \begin{cases} 16 \times 10^6, & 0 < t < 1 \mu s \\ 0, & 1 < t < 3 \mu s \\ -16 \times 10^6, & 3 < t < 4 \mu s \end{cases}$$

$$i_C(t) = C \cdot \frac{dv_C(t)}{dt} = 10 \times 10^{-3} \times \frac{dv_C(t)}{dt} = \begin{cases} 160 \text{ (kA)} & 0 < t < 1 (\mu s) \\ 0 & 1 < t < 3 (\mu s) \\ -160 \text{ (kA)} & 3 < t < 4 (\mu s) \end{cases}$$



**(B)  $L = 10$  (mH)**

$$i_L(t) = \frac{1}{L} \cdot \int_0^t v_L(t) dt + i_L(0)$$


For  $0 < t < 1$ ,  $v_L(t) = 5t$

$$\begin{aligned} i_L(t) &= \frac{1}{10 \times 10^{-3}} \cdot \int_0^t 5t dt + 0 \\ &= \frac{1}{10 \times 10^{-3}} \cdot \times \frac{5t^2}{2} \\ &= 250t^2 \text{ (A)} \end{aligned}$$

For  $1 < t < 2$ ,  $v_L(t) = -10 + 5t$



$$i_L(1) = 250 \text{ (A)} = 0.25 \text{ (kA)}$$

$$\begin{aligned} i_L(t) &= \frac{1}{10 \times 10^{-3}} \cdot \int_1^t (-10 + 5t) dt + i_L(1) \\ &= \int_1^t (t/2 - 1) dt + i_L(1) \text{ (kA)} = \left( \frac{t^2}{4} - t \right) \Big|_1^t + 0.25 \text{ (kA)} = \frac{t^2}{2} - 2t + 1 \text{ (kA)} \end{aligned}$$


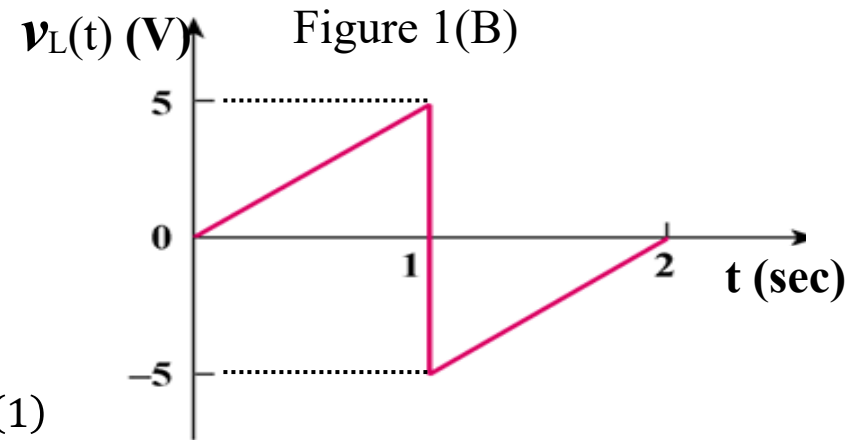


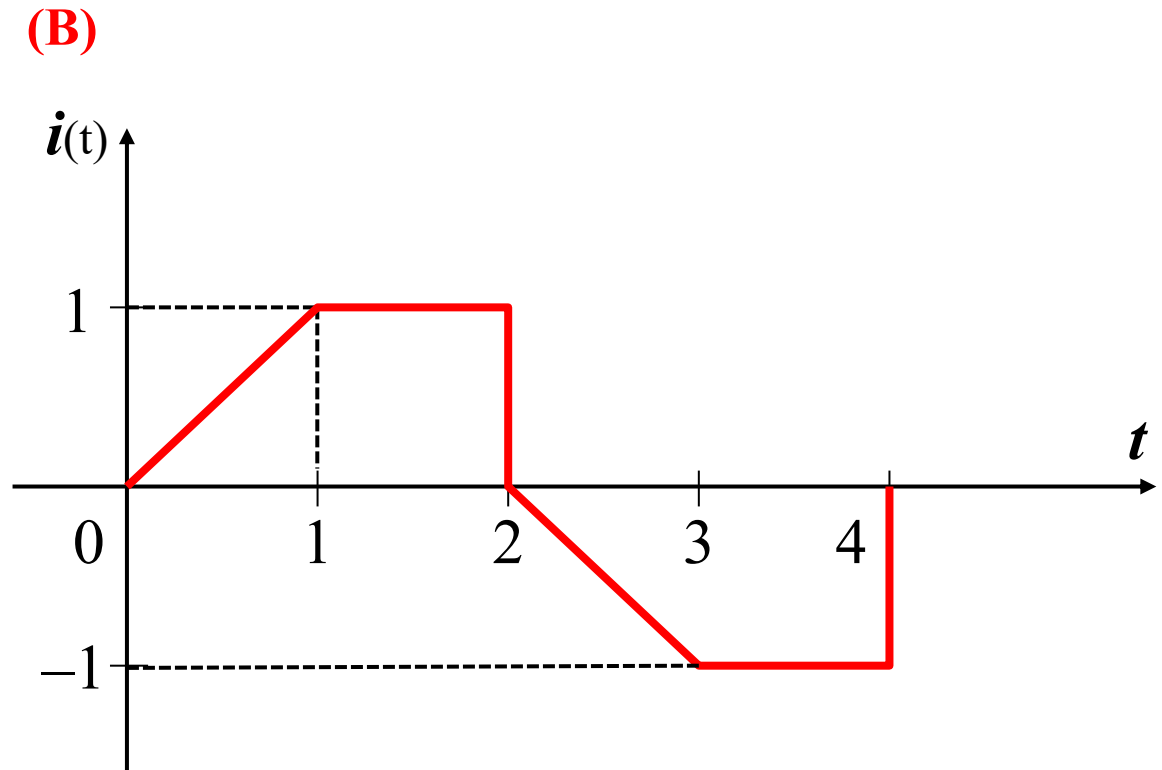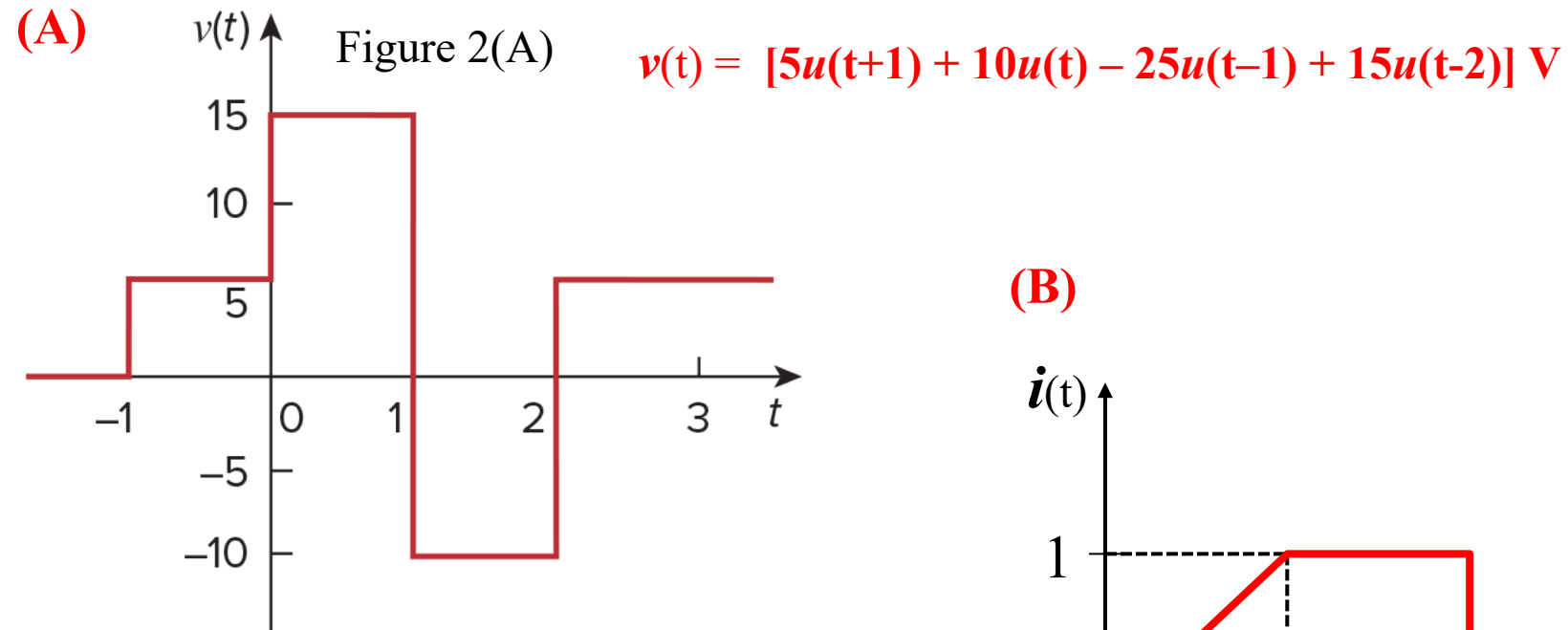2. 10% (A) Express  $v(t)$  in Fig. 2(A) in terms of step functions.

10% (B) Sketch the waveform represented by  $i(t) = r(t) - r(t-1) - u(t-2) - r(t-2) + r(t-3) + u(t-4)$



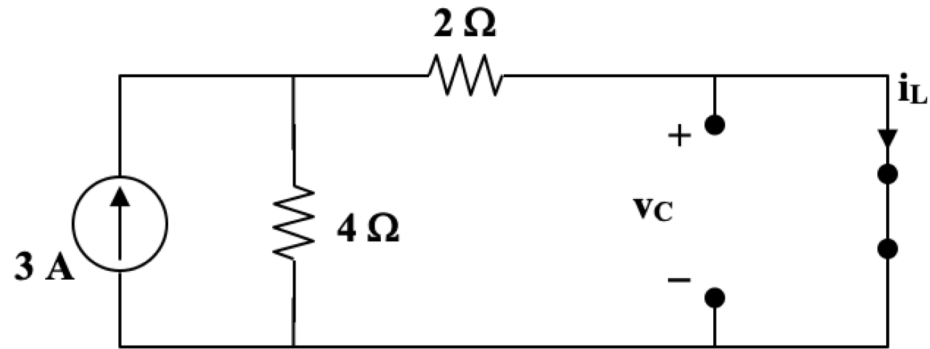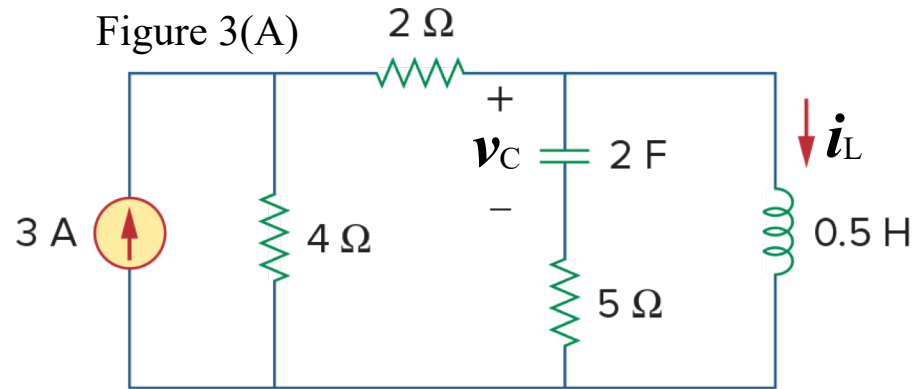3. 30% Under steady-state dc conditions, find  $i_L$ ,  $v_C$  and the energy stored in the capacitor and inductor in the circuit in Fig. 3(A) and Fig.3(B).





$$i_L = 3 \cdot \frac{4}{4 + 2} = 2 \text{ (A)}$$

$$v_C = 0 \text{ (V)}$$

$$w_L = \frac{1}{2} \cdot L \cdot i_L^2 = \frac{1}{2} \times 0.5 \cdot 2^2 = 1 \text{ (J)}$$
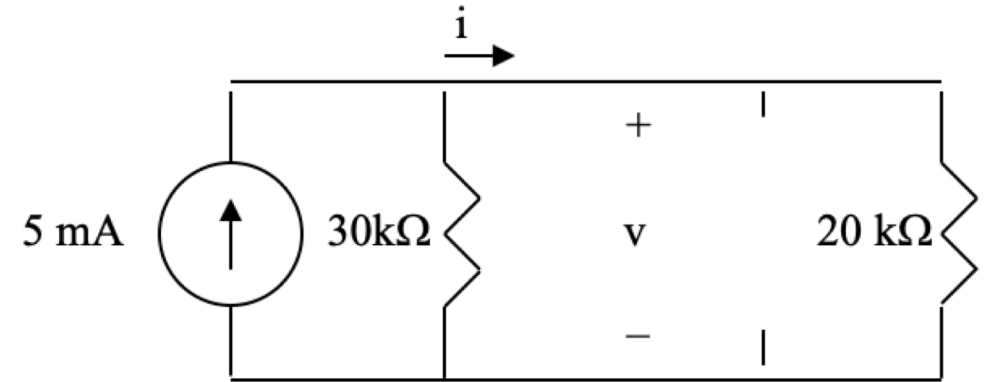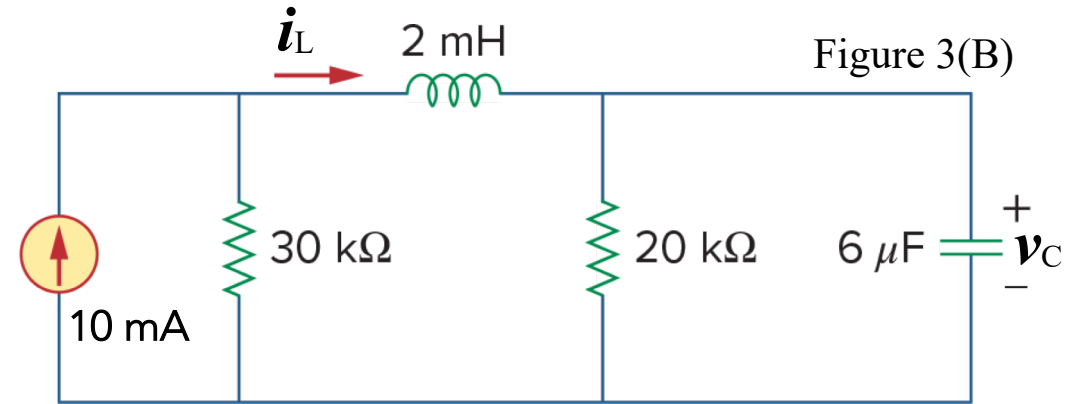
$$w_C = \frac{1}{2} \cdot C \cdot v_C^2 = \frac{1}{2} \times 2 \cdot 0^2 = 0 \text{ (J)}$$



$$i_L = 10 \cdot \frac{30}{30 + 20} = 6 \text{ (mA)}$$


$$v_C = 6 \text{ (mA)} \times 20 \text{ (k)} = 120 \text{ (V)}$$

$$w_L = \frac{1}{2} \cdot L \cdot i_L^2 = \frac{1}{2} \times 2 \times 10^{-3} \times (6 \times 10^{-3})^2 = 36 \text{ (nJ)}$$

$$w_C = \frac{1}{2} \cdot C \cdot v_C^2 = \frac{1}{2} \times 6 \times 10^{-6} \times 120^2 = 0.0432 \text{ (J)}$$

4. 30% For the network shown in Fig. 4, find  $v(t)$  for  $t > 0$ .

$t < 0$ , L short-circuited to dc

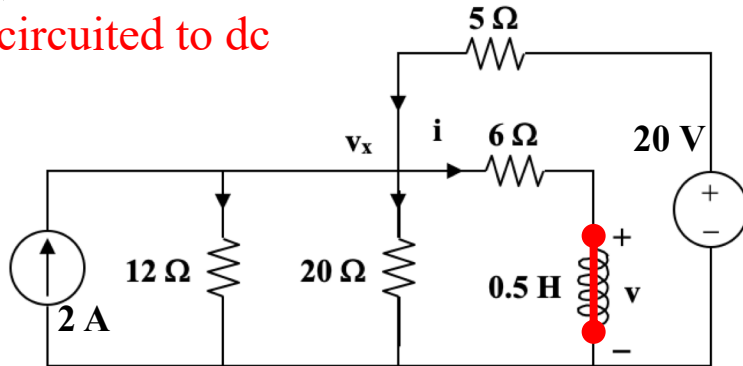

Nodal analysis:


$$2 + \frac{20 - v_x}{5} = \frac{v_x}{12} + \frac{v_x}{20} + \frac{v_x}{6} \longrightarrow v_x = 12$$

$$i(0) = \frac{v_x}{6} = 2 \text{ A}$$

$t \rightarrow \infty$ , L short-circuited to dc :

$$i(\infty) = \frac{20 \times \frac{20 \parallel 6}{5 + 20 \parallel 6}}{6} = 1.6 \text{ (A)}$$

Figure 4

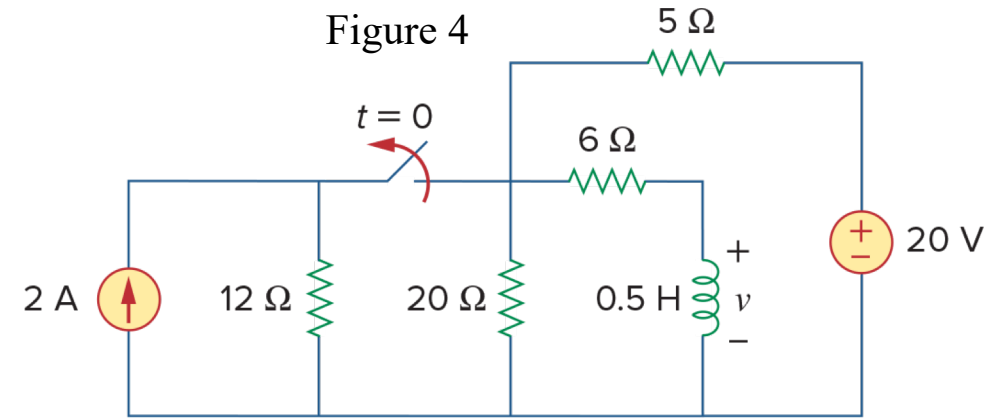


$t > 0$ , switch open:

$$R_{eq} = 6 + 20 \parallel 5 = 10 \Omega \quad \tau = \frac{L}{R} = 0.05$$

$$\begin{aligned} i(t) &= i(\infty) + (i(0) - i(\infty))e^{-t/\tau} \\ &= 1.6 + (2 - 1.6)e^{-\frac{t}{0.05}} \\ &= 1.6 + 0.4e^{-20t} \end{aligned}$$

$$\begin{aligned} v(t) &= L \cdot \frac{di(t)}{dt} \\ &= 0.5 \times \frac{d(1.6 + 0.4e^{-20t})}{dt} \\ &= 0.5 \times 0.4 \times (-20) \cdot e^{-20t} \\ &= -4 \cdot e^{-20t} \end{aligned}$$

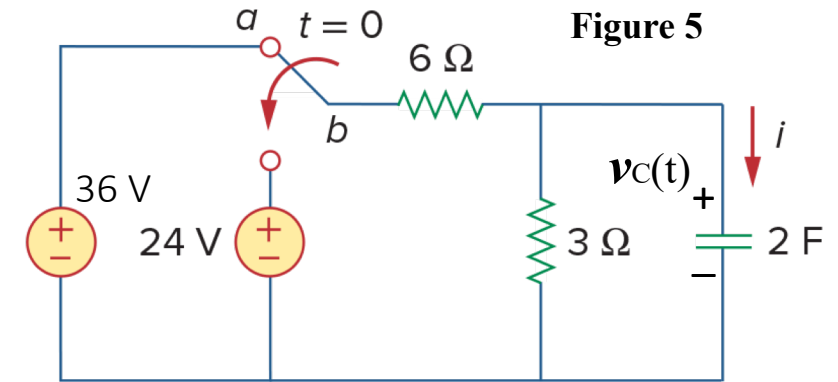5. 30% The switch in Fig. 3 has been in position **a** for a long time. At  $t = 0$ , it moves to position **b**. (A) 20% Derive  $v_C(t)$  and  $i(t)$  for all  $t > 0$ . (B) 10% Sketch the waveform of  $v_C(t)$  for  $t > 0$ , and label the time constant on the waveform.



(A)  $v_C(t) = v(\infty) + [v(0) - v(\infty)] \cdot e^{-\frac{t}{\tau}}$

$t < 0$ , switch at **a**; capacitor  $\rightarrow$  open to 36 V dc.

$$v_C(0) = v(0^-) = 36 \times \frac{3}{6+3} = 12 \text{ (V)}$$

$$v(0) = v(0^+) = v(0^-) = 12 \text{ (V)} \quad \text{3\%}$$

$t > 0$ , switch at **b**;  $\rightarrow$  24 V RC circuit

$$R_{eq} = 6 \parallel 3 = 2\Omega$$

$$\tau = R_{eq} \cdot C = 2 \times 2 = 4 \text{ (s)} \quad \text{3\%}$$

$$v(\infty) = 24 \times \frac{3}{6+3} = 8 \text{ (V)} \quad \text{3\%}$$

$$v_C(t) = v(\infty) + [v(0) - v(\infty)] \cdot e^{-\frac{t}{\tau}}$$

$$= 8 + (12 - 8) \cdot e^{-\frac{t}{4}}$$

$$= 8 + 4 \cdot e^{-0.25t} \text{ (V)} \quad \text{6\%}$$

$$i(t) = C \frac{dv_C(t)}{dt} = 2 \times \frac{d(8 + 4 \cdot e^{-0.25t})}{dt}$$

$$= 2 \times 4 \times (-0.25) \cdot e^{-0.25t}$$

$$= -2 \cdot e^{-0.25t} \text{ (A)} \quad \text{5\%}$$

