


ISTM 214 Homework 5 (Due day: 11/8)

Name: _____

ID: _____

1. For the circuit shown below, derive the following formal descriptions:

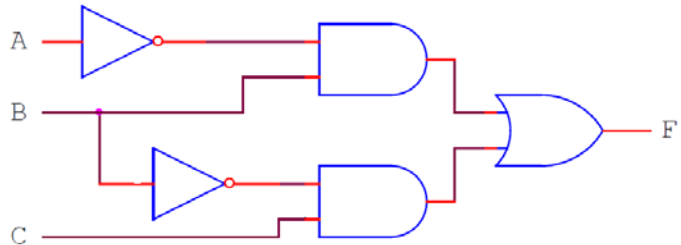- (a) $F(A,B,C)$
- (b) minimum SoP expression.
- (c) K-map
- (d) truth table
- (e) ON set
- (f) OFF set



2. If the function $F(X,Y,Z)$ is represented by the ON SET $\Sigma_{X,Y,Z}(1,2,4,7)$,

- (a) express the complement of this function, $F'(X,Y,Z)$, as an ON set.
- (b) express the dual of this function, $F^D(X,Y,Z)$, as an OFF set.

3. Express the complement of the following function as an ON SET and draw a NAND-NAND circuit realization:

$$F(X,Y,Z) = Y + X \cdot Z'$$

4. Express the complement of the following function as an OFF SET and draw a NOR-NOR circuit realization:

$$F(X,Y,Z) = Y' + X' \cdot Z$$

5. For the function mapped below:

		W'		W		
Y'		1	1	0	1	Z'
		0	0	0	1	Z
Y		1	1	0	0	Z'
		1	1	0	1	Z
		X'		X		X'

- (a) Write a minimal sum-of-products expression and calculate its cost:
- (b) Write a minimal product-of-sums expression and calculate its cost: