

# ELECTRICAL ENGINEERING FUNDAMENTAL II

Name: \_\_\_\_\_

Test 1

2024.3.22

**Note: Make your calculation accuracy to at least the 2<sup>nd</sup> digit behind the decimal point.**

**1. (20%)** Convert the following pairs of sinusoid signals  $v$  and  $i$  into **phasors** and complete the following information.

(A)  $v(t) = 10 \cos(4t - 60^\circ)$   $\Rightarrow V = \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}$  (polar)  $= \underline{\hspace{2cm}}$  (rectangular)

$i(t) = 4 \sin(4t + 50^\circ)$   $\Rightarrow I = \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}$  (polar)  $= \underline{\hspace{2cm}}$  (rectangular)

$\Rightarrow \mathbf{i(t)}$  **leads**  $\mathbf{v(t)}$  by  $\underline{\hspace{1cm}}^\circ$

(B)  $v(t) = -13 \cos(2t) + 5 \sin(2t)$   $\Rightarrow V = \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}$  (polar)  $= \underline{\hspace{2cm}}$  (rectangular)

$i(t) = 15 \cos(2t - 40^\circ)$   $\Rightarrow I = \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}$  (polar)  $= \underline{\hspace{2cm}}$  (rectangular)

$\Rightarrow \mathbf{v(t)}$  **leads**  $\mathbf{i(t)}$  by  $\underline{\hspace{1cm}}^\circ$

**2. (20%)** Evaluate the following complex numbers and express results in both **polar** and **rectangular** forms. (show math. works)


(A)  $\frac{60 \angle 45^\circ}{7.5 - j10} + j2 =$

(B)  $\frac{(10 \angle 30^\circ)(35 \angle -50^\circ)}{(2 + j6)^* - (5 + j)} =$


**3. (15%)** Solve the following integrodifferential equation to get  $v(t)$  using the phasor approach.

$$\frac{dv(t)}{dt} + 5v(t) + 4 \int v(t) dt = 20 \sin(4t + 10^\circ)$$

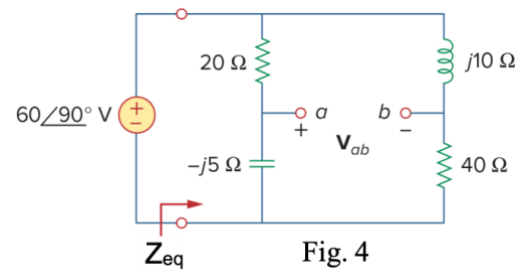
**4. (20%)** For the circuit in Fig. 4, calculate  $Z_{eq}$  and  $V_{ab}$ .



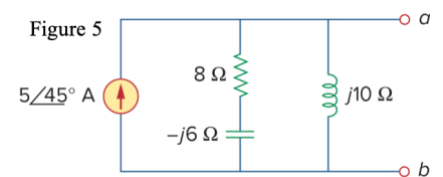5. (15%) For the circuit depicted in Fig. 5, find the Thevenin equivalent circuit at terminals a-b.



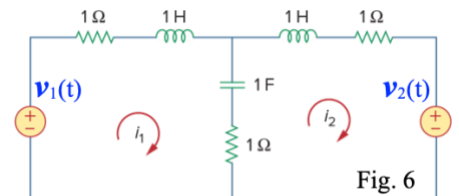6. (20%) In the circuit of Fig. 6, determine the mesh currents  $i_1$  and  $i_2$  with mesh analysis. Let  $v_1 = 10 \cos 4t$  (V) and  $v_2 = 20 \cos (4t - 60^\circ)$  (V).



7. (20%) Determine  $i_o$  in the circuit of Fig. 7. Let  $v_1(t) = 24$  (V),  $v_2(t) = 10 \sin (t + 60^\circ)$  (V),  $i(t) = 2 \cos (2t)$  (A).

