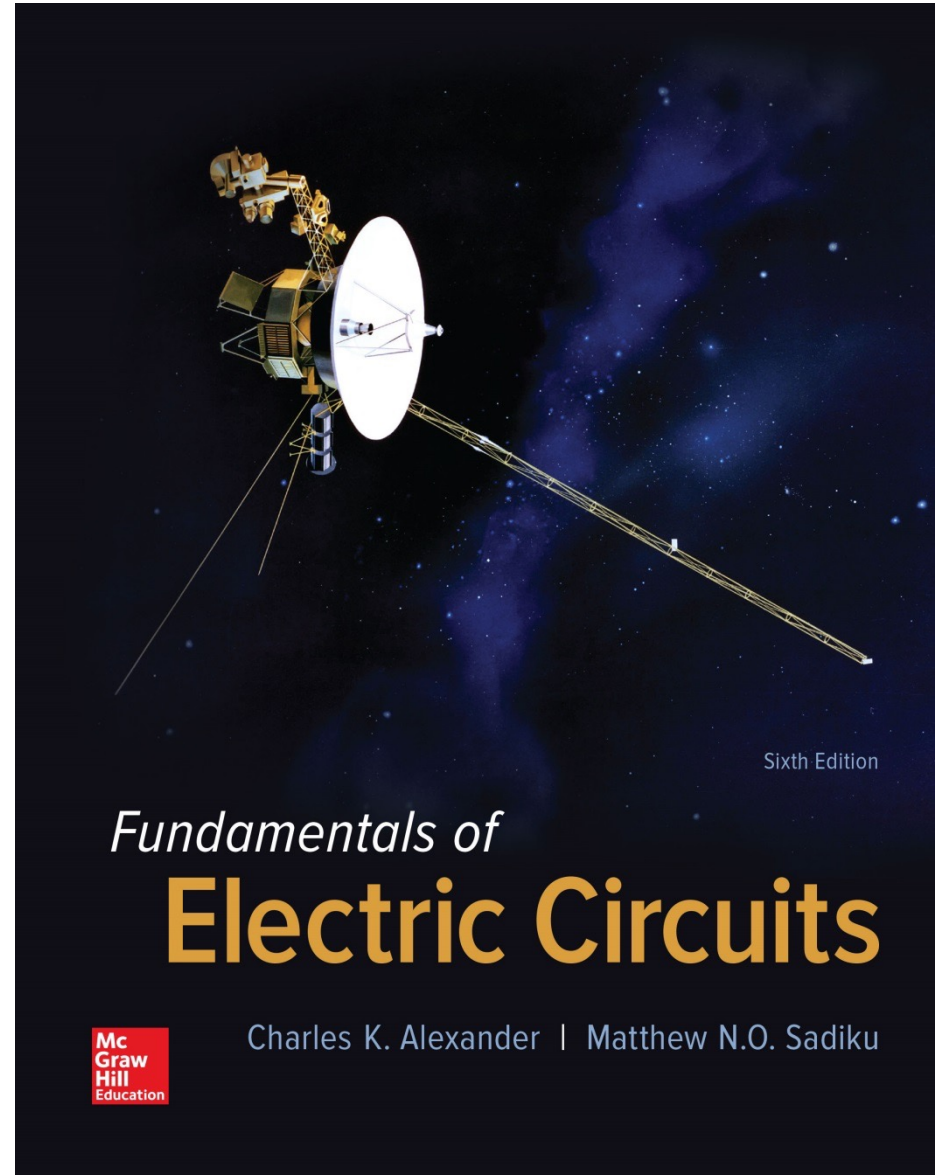


Fundamentals of
Electric Circuits
Chapter 6


**Capacitors
and
Inductors**



6.1 Introduction

- This chapter will introduce two new **linear circuit elements**:
 - ✓ The **capacitor**
 - ✓ The **inductor**
- Unlike resistors, these elements **do not dissipate energy**
- They instead **store energy**
- We will also look at how to analyze them in a circuit

6.2 Capacitors

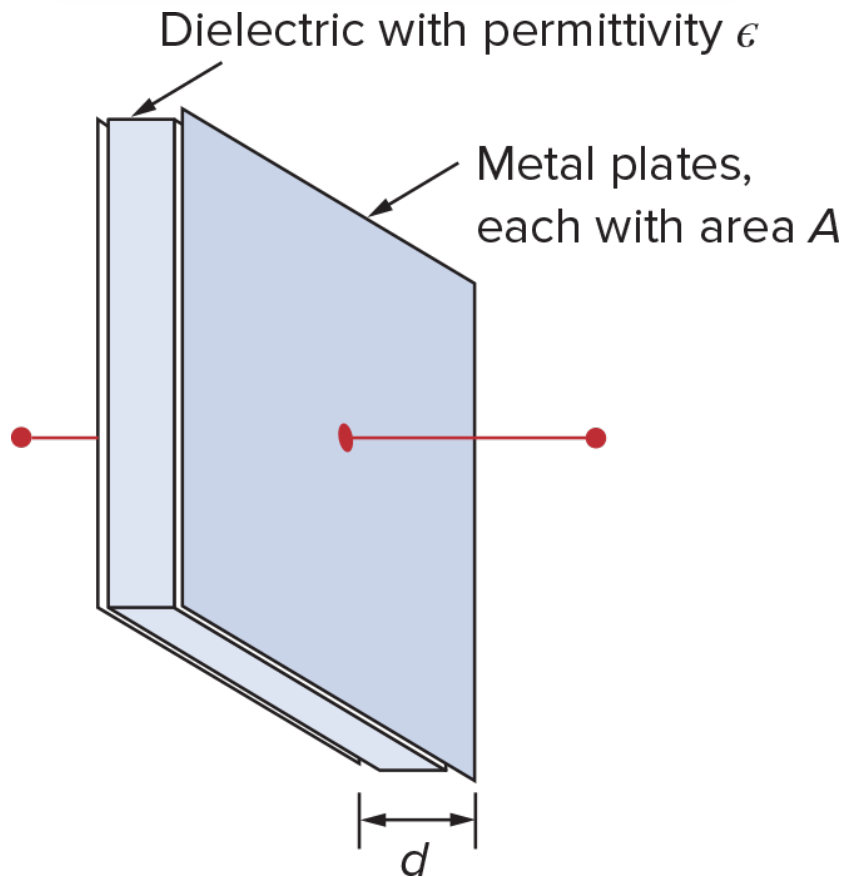


- A **capacitor** is a passive element that **stores energy** in its electric field
- It consists of two **conducting plates** separated by an **insulator** (or dielectric)
- The plates are typically aluminum foil
- The dielectric is often **air**, ceramic, paper, plastic, or mica

Capacitors


- When a voltage source v is connected to the **capacitor**, the source deposits a positive charge q on one plate and a negative charge $-q$ on the other.
- The charges will be equal in magnitude
- The amount of **charge** is proportional to the voltage:

$$q = Cv$$

where **C** is the **capacitance**

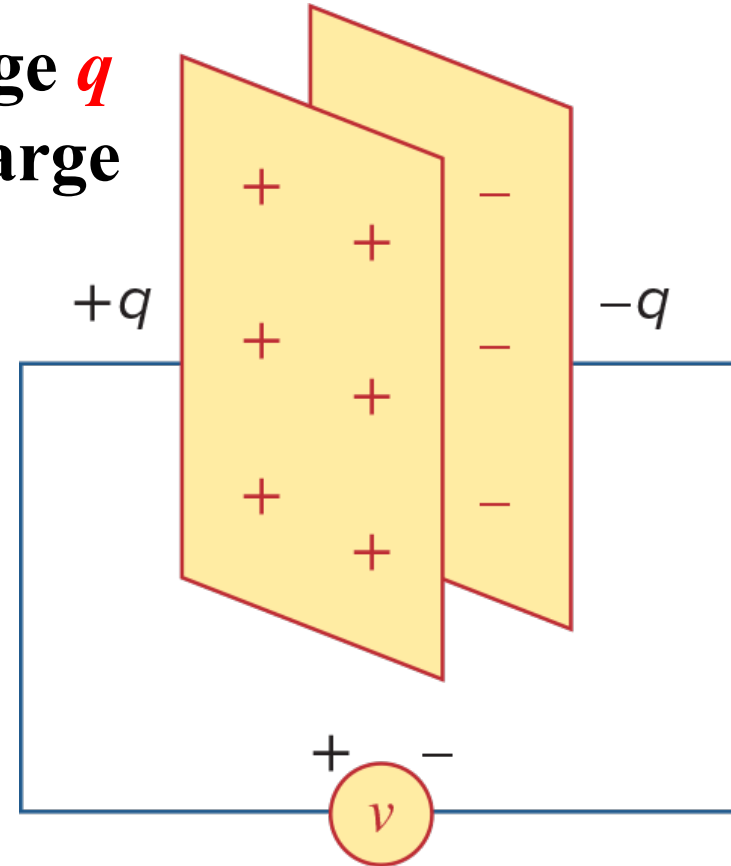

Capacitance


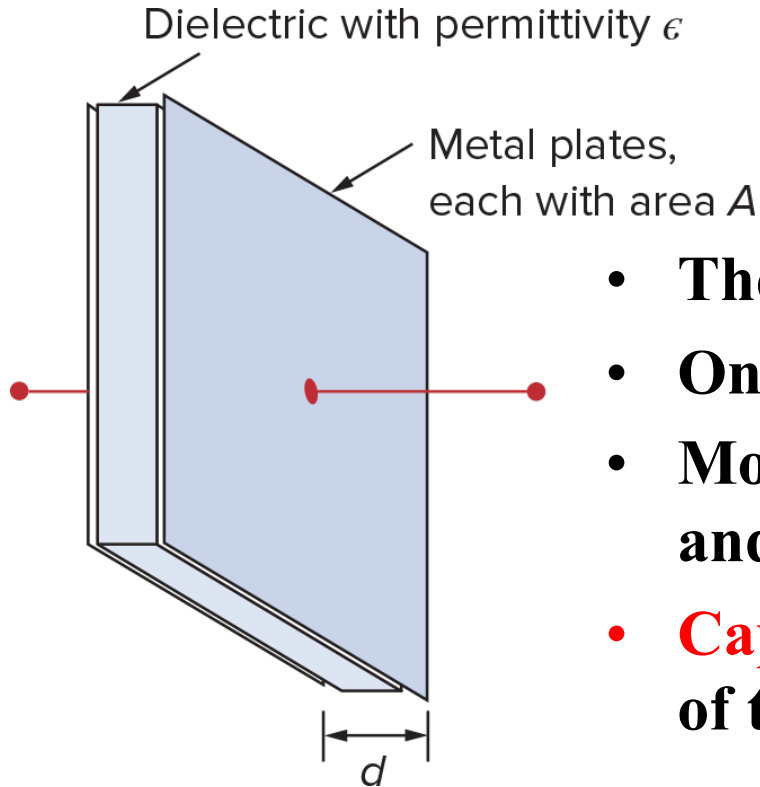


$$q = Cv$$

$$C = \frac{q}{v}$$

- The unit of **capacitance** is the **Farad (F)**
 - One **Farad** is 1 **Coulomb/Volt**
 - Most capacitors are rated in picofarad (**pF**) and microfarad (**μ F**)
 - **Capacitance** is determined by the **geometry** of the capacitor:
 - Proportional to the area of the plates (**A**)
 - Inversely proportional to the space between them (**d**)
- $$C = \frac{\epsilon A}{d}$$
- **ϵ** is the permittivity of the dielectric


Applications for Capacitors

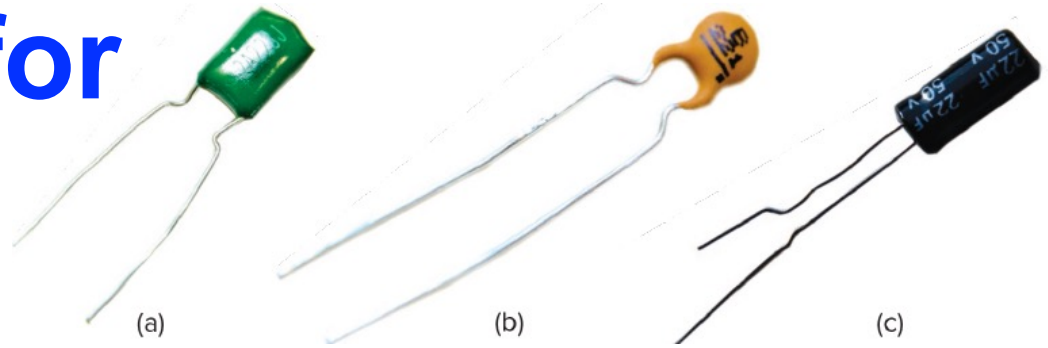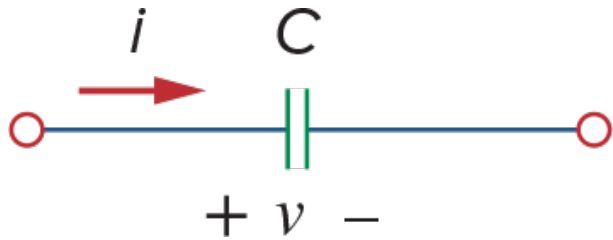

Fixed capacitors: (a) polyester capacitor, (b) ceramic capacitor, (c) electrolytic capacitor.

- Capacitors have a wide range of applications, some of which are:

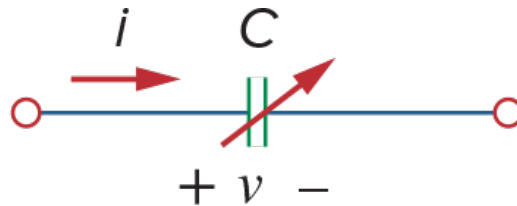- Blocking DC
- Passing AC
- Shift phase
- Store energy
- Suppress noise
- Start motors




Variable capacitors

Current Voltage Relationship


- Using the formula for the charge stored in a **capacitor**, we can find the **current voltage relationship**
- Take the first derivative with respect to time gives:

$$i = \frac{dq}{dt} \quad i = C \frac{dv}{dt}$$

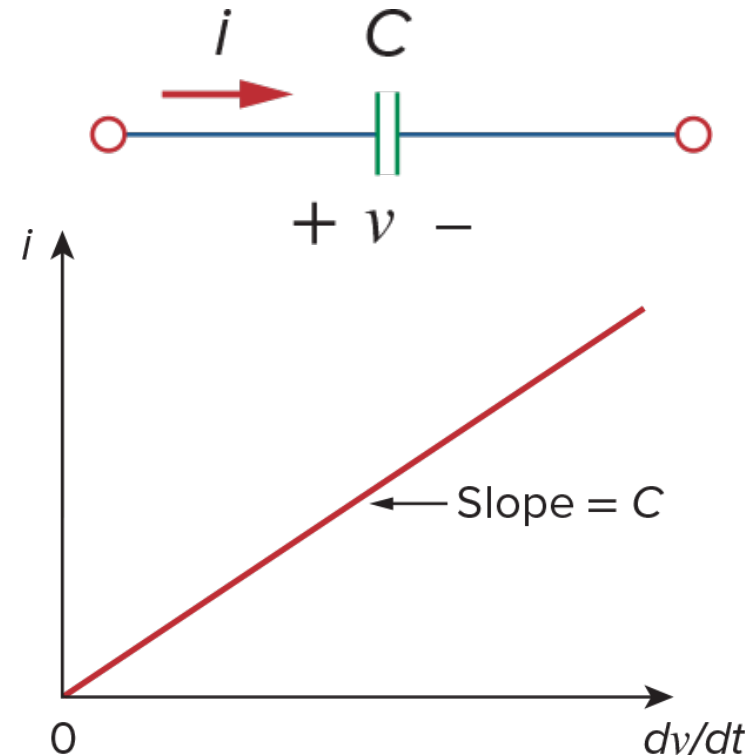- This assumes the **passive sign convention**



Stored Charge

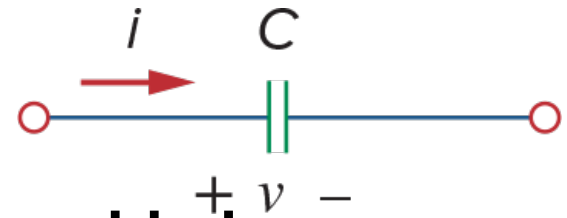

- Similarly, the **voltage-current** relationship is:

$$i = C \frac{dv}{dt} \qquad v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

- This shows the capacitor has a memory, which is often exploited in circuits
- The instantaneous **power** delivered to the capacitor is

$$p = vi = Cv \frac{dv}{dt}$$

- The **energy** stored in a capacitor is:

$$w = \int_{-\infty}^t p(\tau) d\tau = C \int_{-\infty}^t v \frac{dv}{d\tau} d\tau = C \int_{v(-\infty)}^{v(t)} v dv = \frac{1}{2} C v^2 \Big|_{v(-\infty)}^{v(t)}$$

$$w = \frac{1}{2} C v^2 \qquad w = \frac{q^2}{2C}$$



Properties of Capacitors

- **Ideal capacitors** all have these characteristics:

$$i = C \frac{dv}{dt}$$


Voltage across a capacitor:

- ✓ When the **voltage** is not changing, the **current** through the **cap** is **zero**.
- ✓ This means that with **DC** applied to the terminals **no current** will flow.
- ✓ Except, the voltage on the capacitor's plates **can't change instantaneously**.
- ✓ An **abrupt change** in voltage would require an **infinite current**!
- ✓ This means if the **voltage** on the **cap** does not equal the applied voltage, **charge will flow** and the **voltage** will finally reach the applied voltage.

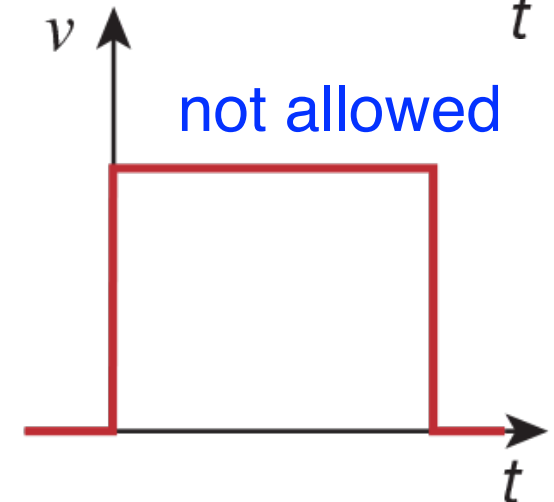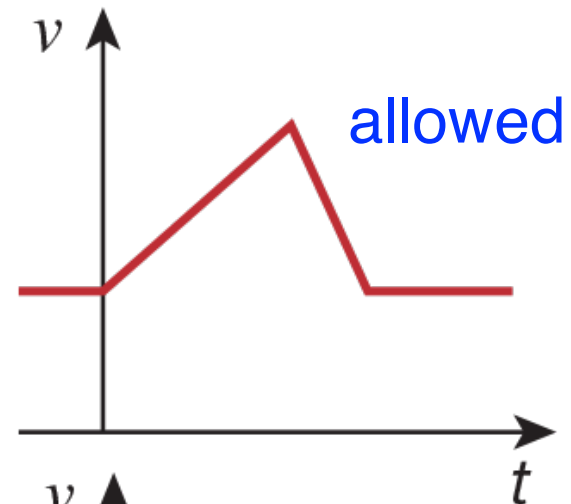

Properties of capacitors

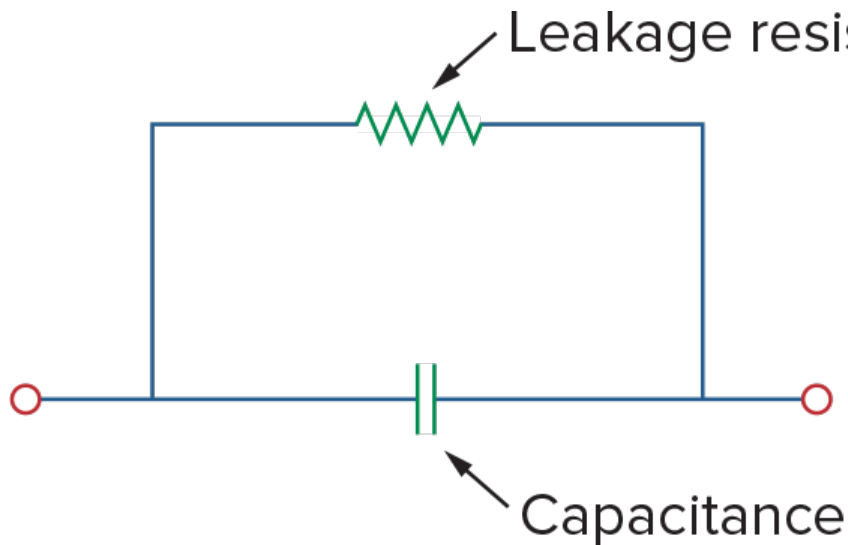- ✓ An ideal capacitor **does not dissipate energy**, meaning **stored energy** may be retrieved later
- ✓ A real capacitor has a parallel-model **leakage resistance**, leading to a **slow loss of the stored energy** internally



- ✓ This **resistance** is typically very **high**, on the order of **100 MΩ** and thus **can be ignored** for many circuit applications.


Example 6.1

(a) Calculate the charge stored on a 3-pF capacitor with 20 V across it.

$$q = Cv = 3 \times 10^{-12} \times 20 = 60 \text{ pC}$$

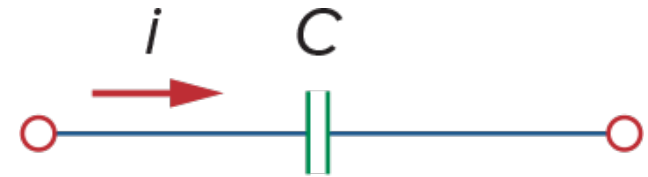(b) Find the energy stored in the capacitor.

$$w = \frac{1}{2} Cv^2 = \frac{1}{2} \times 3 \times 10^{-12} \times 400 = 600 \text{ pJ}$$



$$i = C \frac{dv}{dt}$$

Example 6.2

The voltage across a 5- μ F capacitor is

$$v(t) = 10 \cos 6000t \text{ V}$$

Calculate the current through it.


$$\begin{aligned} i(t) &= C \frac{dv}{dt} = 5 \times 10^{-6} \frac{d}{dt} (10 \cos 6000t) \\ &= -5 \times 10^{-6} \times 6000 \times 10 \sin 6000t \\ &= -0.3 \sin 6000t \text{ A} \end{aligned}$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

Example 6.3

Determine the voltage across a $2\text{-}\mu\text{F}$ capacitor if the current through it is

$$i(t) = 6e^{-3000t} \text{ mA}$$

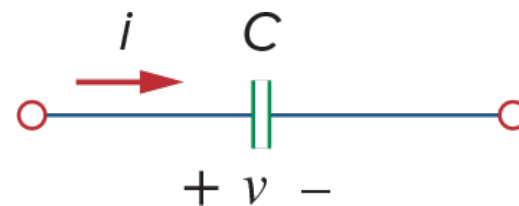



Assume that the initial capacitor voltage is zero.

$$i = C \frac{dv}{dt}$$

$$\begin{aligned} v(t) &= \frac{1}{C} \int_0^t i \, d\tau + v(0) \\ &= \frac{1}{2 \times 10^{-6}} \int_0^t 6e^{-3000\tau} \, d\tau \\ &= \frac{6 \times 10^6}{2 \times (-3000)} e^{-3000\tau} \Big|_0^t \\ &= -10^3 (e^{-3000t} - 1) \\ &= (1 - e^{-3000t}) \times 10^3 (\text{mV}) \\ &= (1 - e^{-3000t}) (\text{V}) \end{aligned}$$

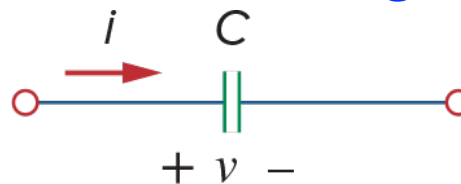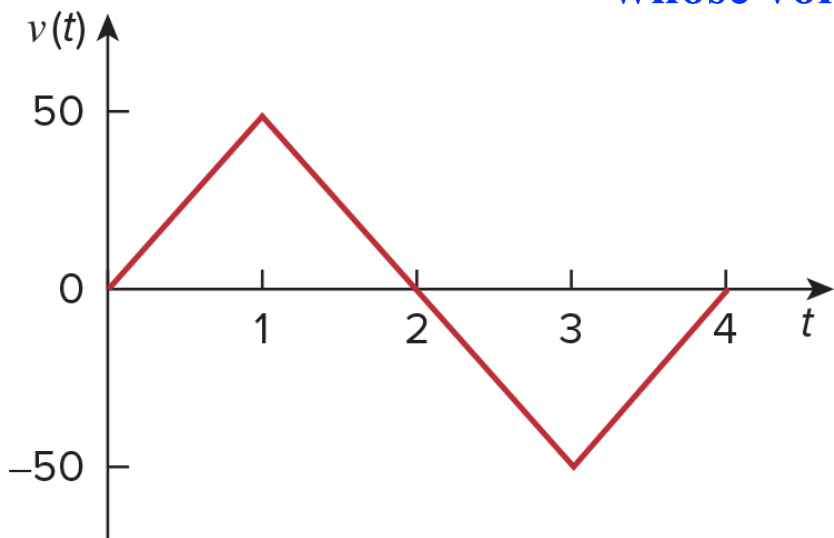Example 6.4

Determine the current through a 200- μF capacitor whose voltage is shown in the figure.




$$i = C \frac{dv}{dt}$$

$$v(t) = \begin{cases} 50t \text{ (V)} & 0 < t < 1 \\ 100 - 50t \text{ (V)} & 1 < t < 3 \\ -200 + 50t \text{ (V)} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

$$i(t) = C \frac{dv(t)}{dt} = 200 \times 10^{-6} \begin{cases} 50 \text{ (A)} & 0 < t < 1 \\ -50 \text{ (A)} & 1 < t < 3 \\ 50 \text{ (A)} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

$$= \begin{cases} 10 \text{ (mA)} & 0 < t < 1 \\ -10 \text{ (mA)} & 1 < t < 3 \\ 10 \text{ (mA)} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

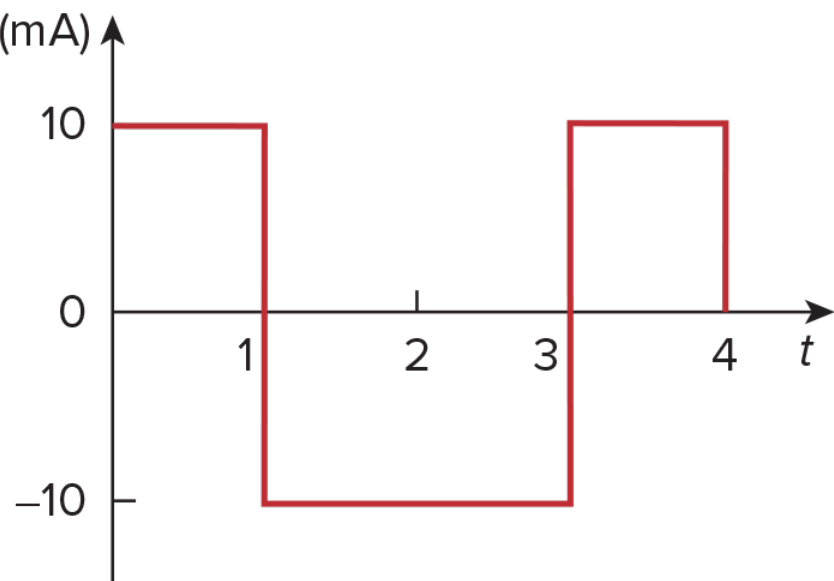



Example 6.5 Obtain the energy stored in each capacitor under dc conditions

dc $\rightarrow i_c = C \frac{dv_c}{dt} \rightarrow$ capacitor \rightarrow open circuit

$$i = \frac{3}{3 + 2 + 4} (6 \text{ mA}) = 2 \text{ mA}$$

$$v_1 = 2000i = 4 \text{ V}$$

$$v_2 = 4000i = 8 \text{ V}$$

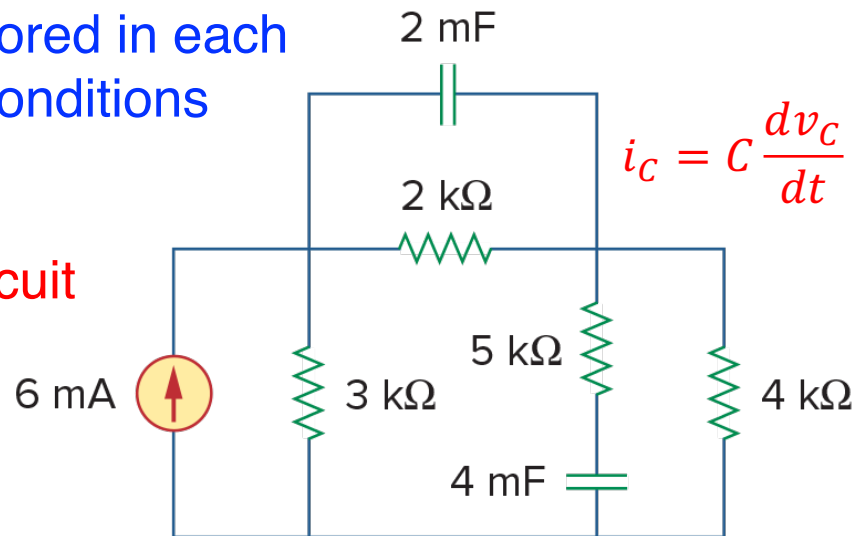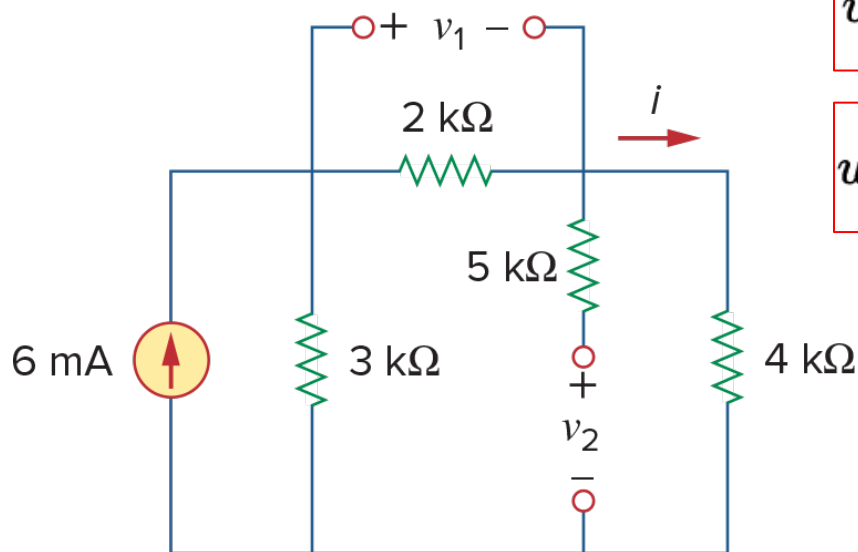


$$w_1 = \frac{1}{2} C_1 v_1^2 = \frac{1}{2} (2 \times 10^{-3}) (4)^2 = 16 \text{ mJ}$$

$$w_2 = \frac{1}{2} C_2 v_2^2 = \frac{1}{2} (4 \times 10^{-3}) (8)^2 = 128 \text{ mJ}$$

6.3 Series and Parallel Capacitors


Parallel Capacitors

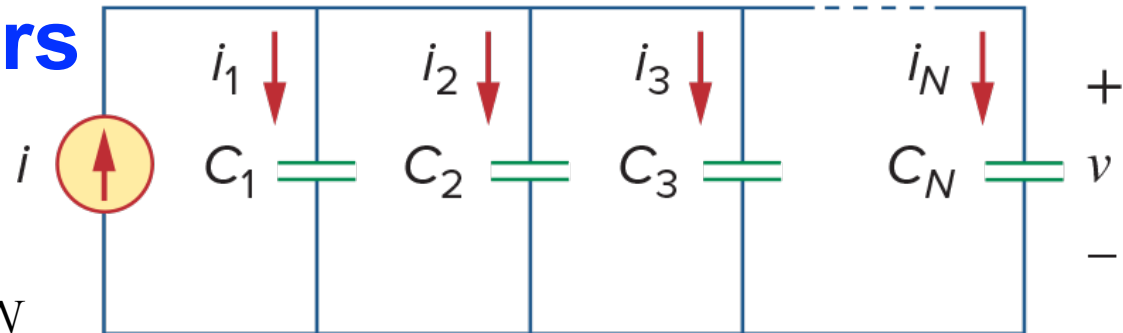

$$i = i_1 + i_2 + i_3 + \dots + i_N$$

$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt}$$
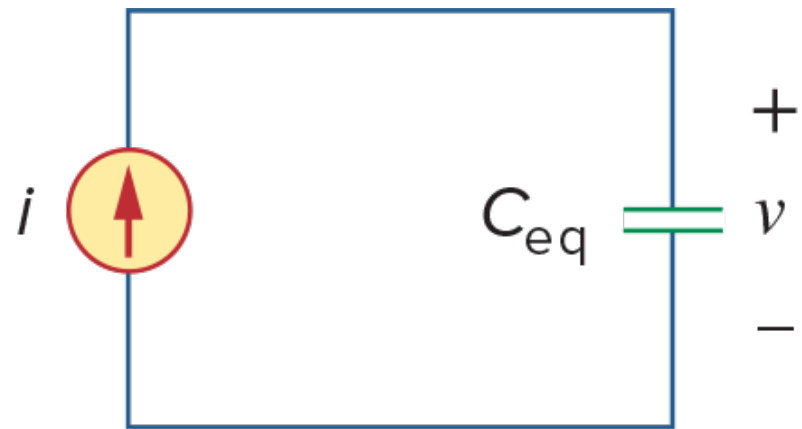
$$= \left(\sum_{k=1}^N C_k \right) \frac{dv}{dt} = C_{eq} \frac{dv}{dt}$$




$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

parallel capacitors combine as the sum of all capacitance

6.3 Series and Parallel Capacitors

Series Capacitors

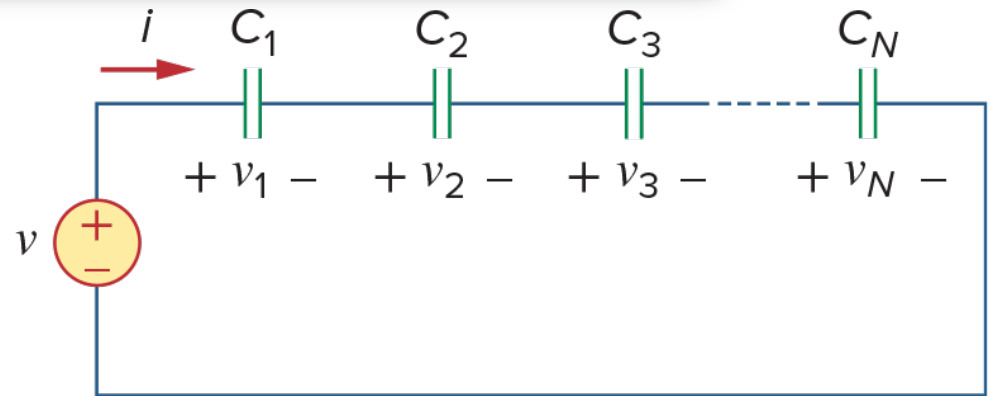


$$v = v_1 + v_2 + v_3 + \dots + v_N$$

$$v = \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau + v_2(t_0) + \frac{1}{C_3} \int_{t_0}^t i(\tau) d\tau + v_3(t_0) + \dots + \frac{1}{C_N} \int_{t_0}^t i(\tau) d\tau + v_N(t_0)$$

$$= \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i(\tau) d\tau + v_1(t_0) + v_2(t_0) + v_3(t_0) + \dots + v_N(t_0)$$

$$= \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$
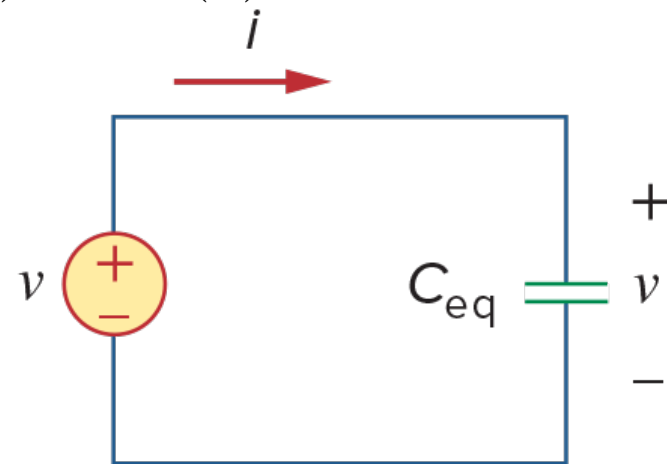
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$



series combination of capacitors
resembles the parallel combination of resistors.

Series and Parallel Caps

$$C = \frac{\epsilon A}{d}$$

- Another way to think about the combinations of capacitors is this:
 - A **parallel** combining is equivalent to
 - **increasing** the **surface area** of the capacitors:
 - This would lead to an **increased overall capacitance**


$$C_{eq} = C_1 + C_2 + C_3 + \dots + C_N$$

- A **series** combination can be seen as
 - **increasing** the total **plate separation**
 - This would result in a **decrease in capacitance**

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_N}$$

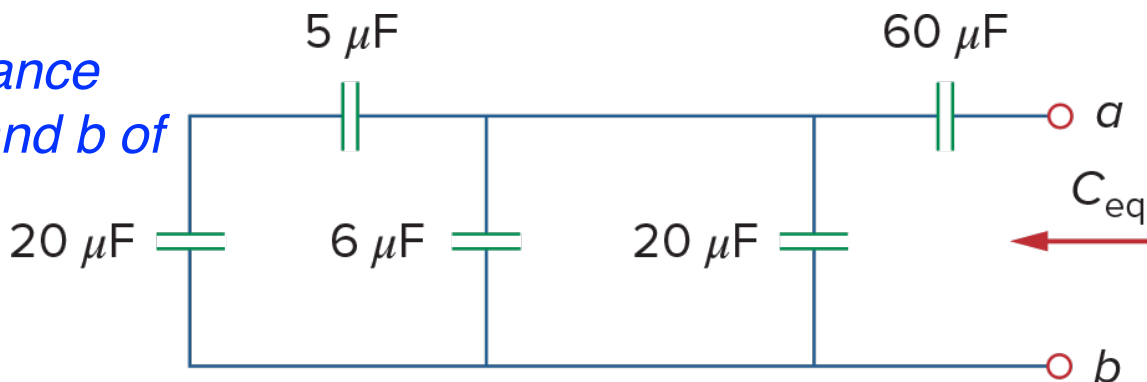Example 6.6

Find the equivalent capacitance seen between terminals a and b of the circuit



The $20\text{-}\mu\text{F}$ and $5\text{-}\mu\text{F}$ capacitors are in series:

$$\frac{20 \times 5}{20 + 5} = 4\ \mu\text{F}$$

This $4\text{-}\mu\text{F}$ capacitor is in parallel with the $6\text{-}\mu\text{F}$ and $20\text{-}\mu\text{F}$ capacitors:


$$4 + 6 + 20 = 30\ \mu\text{F}$$

This $30\text{-}\mu\text{F}$ capacitor is in series with the $60\text{-}\mu\text{F}$ capacitor

$$C_{eq} = \frac{30 \times 60}{30 + 60} = 20\ \mu\text{F}$$

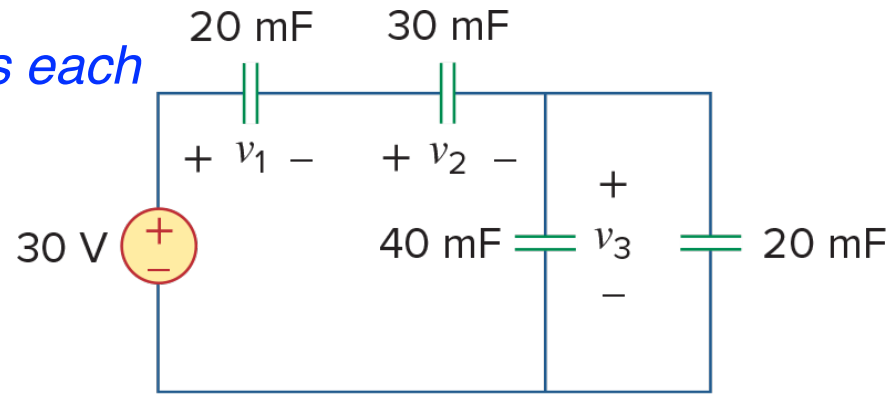Example 6.7 *find the voltage across each capacitor*

$$C_{\text{eq}} = \frac{1}{\frac{1}{60} + \frac{1}{30} + \frac{1}{20}} \text{ mF} = 10 \text{ mF}$$



total charge $q = C_{\text{eq}}v = 10 \times 10^{-3} \times 30 = 0.3 \text{ C}$


Charge acts like current, since $i = dq/dt$

$$v_1 = \frac{q}{C_1} = \frac{0.3}{20 \times 10^{-3}} = 15 \text{ V}$$

$$v_2 = \frac{q}{C_2} = \frac{0.3}{30 \times 10^{-3}} = 10 \text{ V}$$

$$v_3 = 30 - v_1 - v_2 = 5 \text{ V}$$

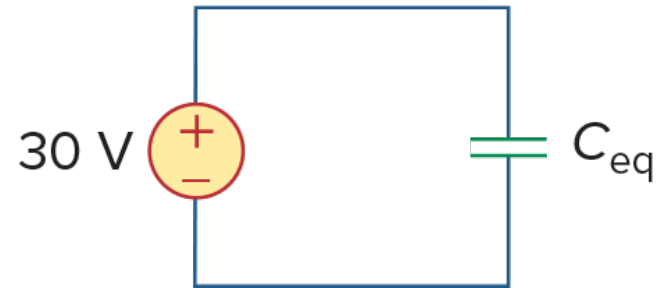or $v_3 = \frac{q}{60 \text{ mF}} = \frac{0.3}{60 \times 10^{-3}} = 5 \text{ V}$




6.4 Inductors


- An **inductor** is a passive element that **stores energy** in its **magnetic field**
- They have applications in power supplies, transformers, radios, TVs, radars, and electric motors.
- Any **conductor** has **inductance**, but the effect is typically enhanced by coiling the wire up.



(a)

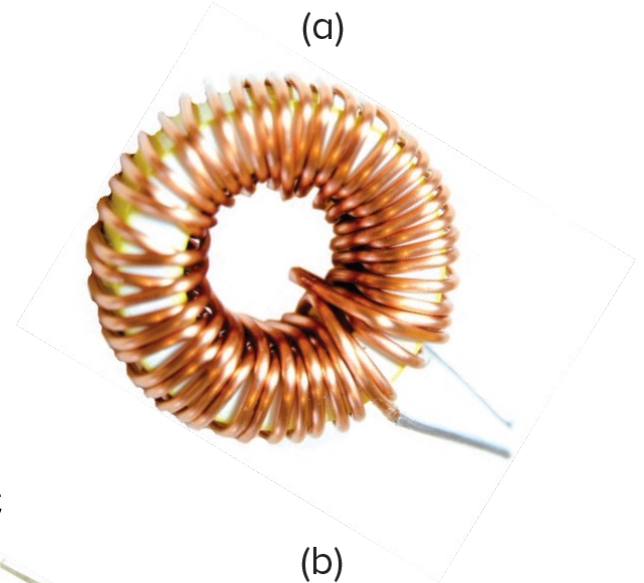


(b)

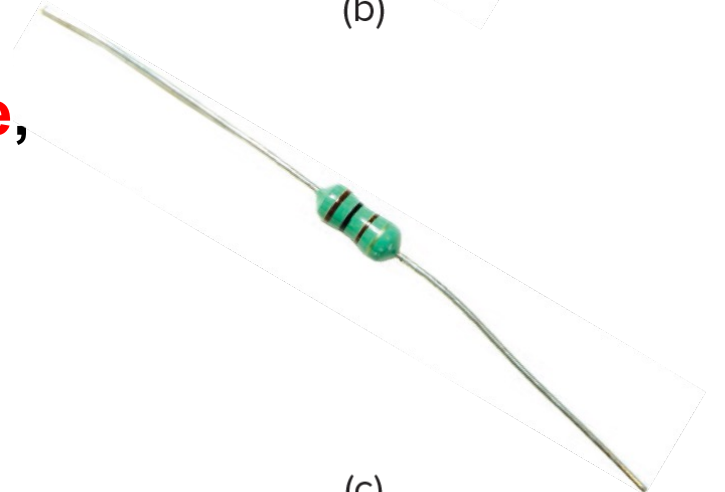


(c)

Inductors

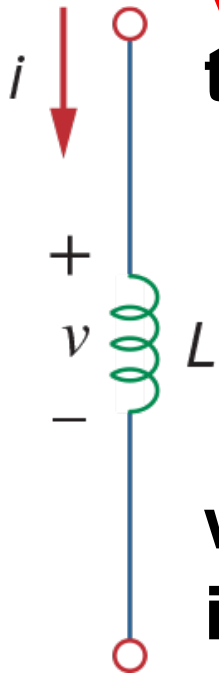- If a **current** is passed through an **inductor**, the **voltage** across it is directly proportional to the **time rate of change in current**



$$v = L \frac{di}{dt}$$

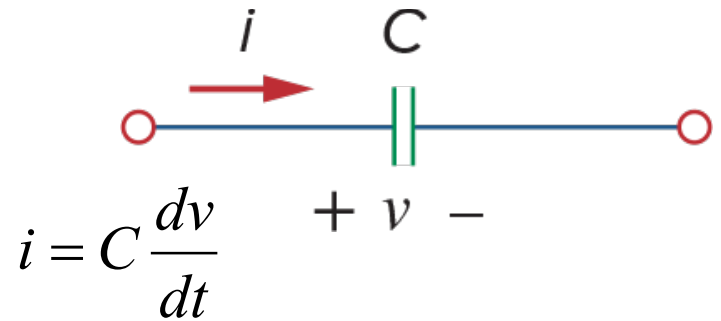

$$i = C \frac{dv}{dt}$$

where, **L**, is the unit of **inductance**, measured in **Henries, H**.

- One Henry is 1 **volt-second per ampere (V-s/A)**.
- The voltage developed tends to **oppose a changing flow of current**.


Inductors

- Calculating the inductance depends on the geometry:
- For example, for a solenoid the **inductance** is:

$$L = \frac{N^2 \mu A}{l}$$

here **N** is the number of turns of the wire around the core of cross sectional area **A** and length **l** .

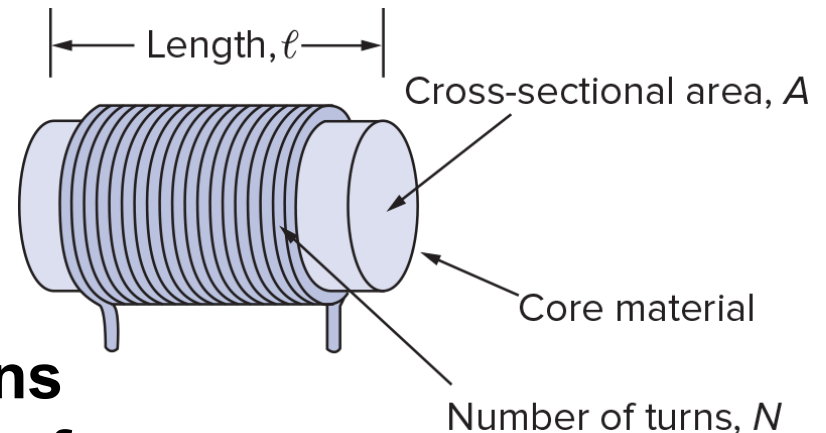
- The **material** used for the core has a **magnetic property** called the **permeability**, **μ** .



Current in an Inductor

- The **current voltage relationship** for an inductor is:
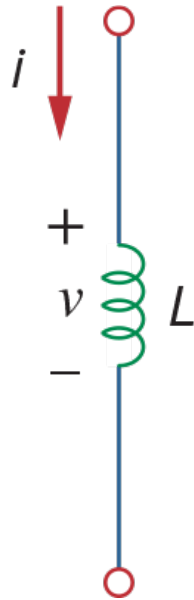
$$I = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0) \quad v = L \frac{di}{dt}$$



- The power delivered to the inductor is:


$$p = vi = \left(L \frac{di}{dt} \right) i$$

- The energy stored is:

$$w = \int_{-\infty}^t p(\tau) d\tau = L \int_{-\infty}^t \frac{di}{d\tau} i d\tau$$

$$= L \int_{-\infty}^t i di = \frac{1}{2} Li^2(t) - \frac{1}{2} Li^2(-\infty)$$

$$w = \frac{1}{2} Li^2$$



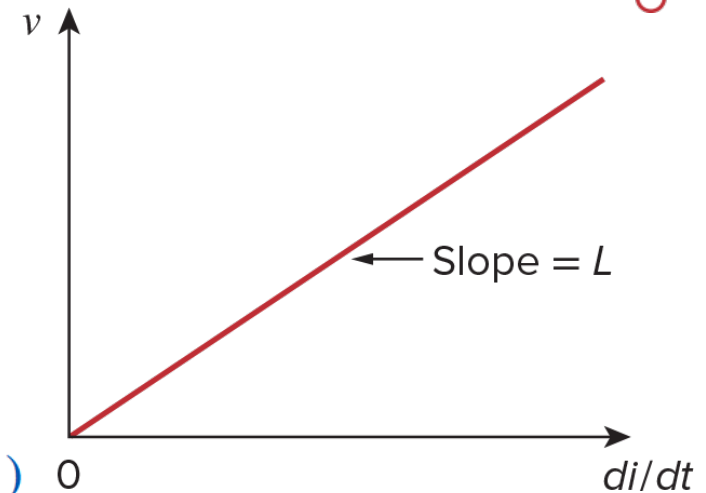


Properties of Inductors

- If the **current** through an **inductor** is **constant**, the **voltage** across it is **zero**
- Thus an **inductor** acts like a **short for DC**


$$v = L \frac{di}{dt} \qquad i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

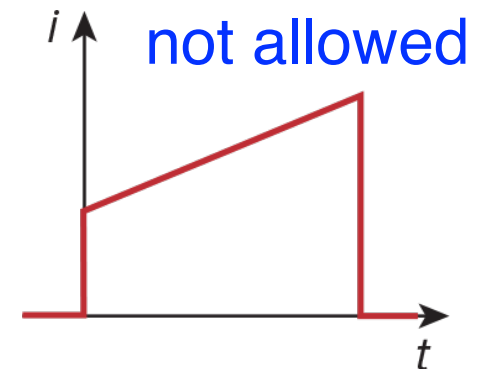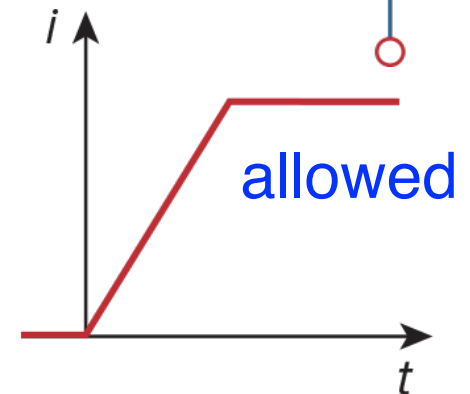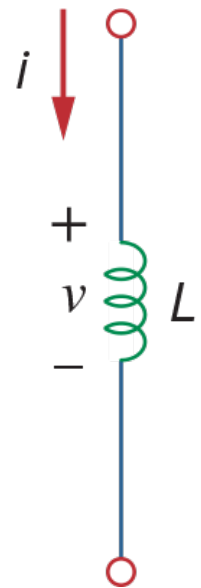- The **current** through an inductor **cannot change instantaneously**
- If this did happen, the **voltage** across the inductor would be **infinity**!
- This is an important consideration if an inductor is to be turned off abruptly; it will produce a high voltage



Properties of Inductors

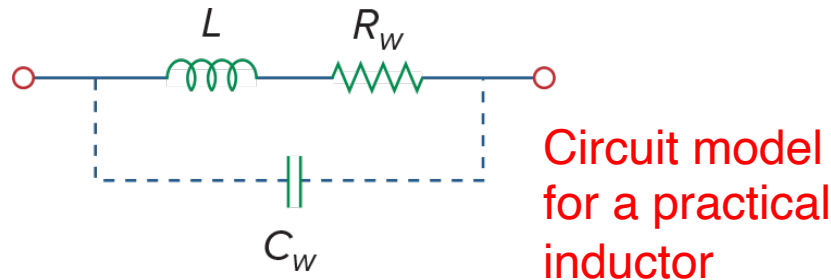- Like the ideal capacitor, the **ideal inductor does not dissipate energy** stored in it.
- **Energy stored** will be returned to the circuit later
- In reality, **inductors** do have **internal resistance** due to the wiring used to make them.
- A **real inductor** thus has a **winding resistance** in **series** with it.



- There is also a small **winding capacitance** due to the closeness of the windings
- These two characteristics are typically small, though at **high frequencies**, the **capacitance** may matter.

Example 6.8

Find the voltage across the inductor and the energy stored in it.

The current through a 0.1-H inductor is $i(t) = 10te^{-5t}$ A.


$$v = L \frac{di}{dt}$$

$$v = 0.1 \frac{d}{dt} (10te^{-5t})$$

$$= e^{-5t} + t(-5)e^{-5t} = e^{-5t}(1 - 5t) \text{ V}$$

$$w = \frac{1}{2} Li^2$$
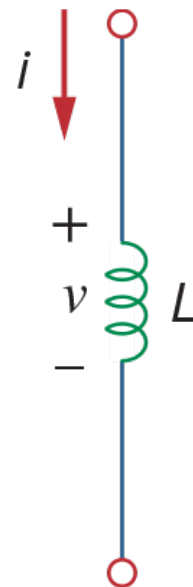
$$= \frac{1}{2} (0.1) 100t^2 e^{-10t} = 5t^2 e^{-10t} \text{ J}$$



$$v = L \frac{di}{dt}$$

$$I = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

$$p = vi = \left(L \frac{di}{dt} \right) i$$

$$w = \frac{1}{2} Li^2$$

Example 6.9


Find the current through a 5-H inductor

if the voltage across it is $v(t) = \begin{cases} 30t^2 \text{ (V)} & t > 0 \\ 0 & t < 0 \end{cases}$

Find the energy stored at $t = 5$ s. Assume $i(v) > 0$.

$$\begin{aligned} i(t) &= \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0) \\ &= \frac{1}{5} \int_0^t 30\tau^2 d\tau + i(0) \\ &= \frac{30}{5} \left(\frac{t^3}{3} \right) + 0 \\ &= 2t^3 \text{ (A)} \end{aligned}$$

$$\begin{aligned} p &= v \times i \\ &= 30t^2 \times 2t^3 \\ &= 60t^5 \\ w &= \int_0^t p dt \\ &= \int_0^5 60t^5 dt \\ &= 60 \left(\frac{t^6}{6} \right) \Big|_0^{t=5} \\ &= 156,250 \text{ (J)} \\ &= 156.25 \text{ (kJ)} \end{aligned}$$

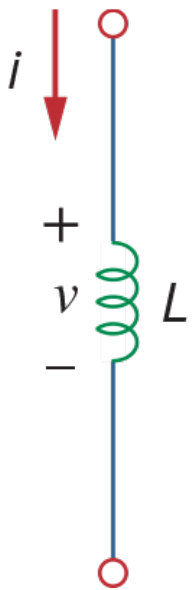
$$\begin{aligned} v &= L \frac{di}{dt} \\ I &= \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0) \\ p &= vi = \left(L \frac{di}{dt} \right) i \\ w &= \frac{1}{2} Li^2 \end{aligned}$$

Example 6.10

Consider the circuit under dc conditions, find:

(a) \mathbf{i} , $\mathbf{v_C}$, and $\mathbf{i_L}$,

(b) the energy stored in the capacitor and inductor.

$$i = C \frac{dv}{dt} \quad \text{DC} \Rightarrow i \rightarrow 0 \Rightarrow \text{C open circuit}$$



$$v = L \frac{di}{dt} \quad \text{DC} \Rightarrow v \rightarrow 0 \Rightarrow \text{L short circuit}$$

$$i = i_L = \frac{12}{1 + 5} = 2 \text{ A}$$

$$v_C = 5i = 10 \text{ V}$$

$$w_C = \frac{1}{2} C v_C^2 = \frac{1}{2} (1)(10^2) = 50 \text{ J}$$
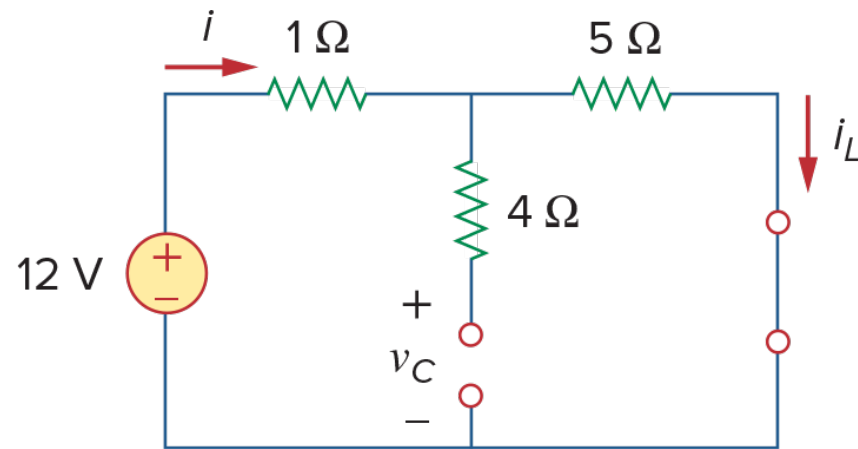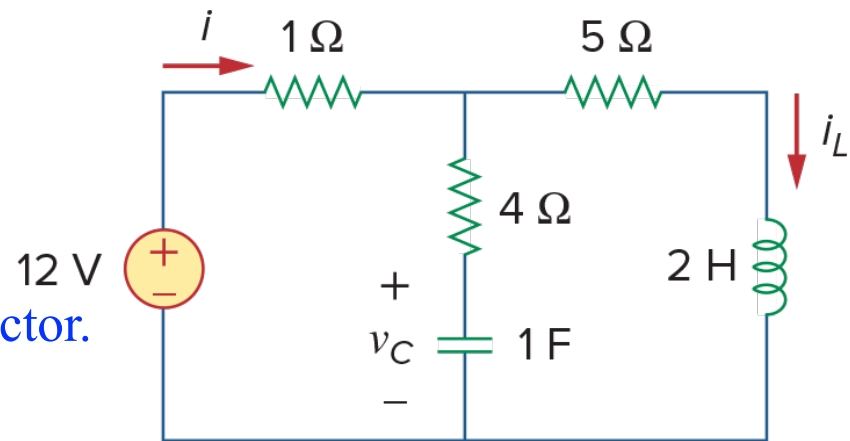
$$w_L = \frac{1}{2} L i_L^2 = \frac{1}{2} (2)(2^2) = 4 \text{ J}$$



6.5 Series and Parallel Inductors

Series Inductors


- Applying KVL to the loop:

$$v = v_1 + v_2 + v_3 + \cdots + v_N$$


$$v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} + \cdots + L_N \frac{di}{dt}$$

$$= \left(\sum_{k=1}^N L_k \right) \frac{di}{dt} = L_{eq} \frac{di}{dt}$$
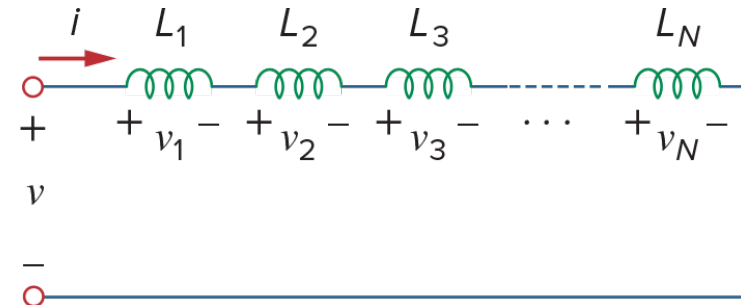
$$L_{eq} = L_1 + L_2 + L_3 + \cdots + L_N$$




$$v = L \frac{di}{dt}$$

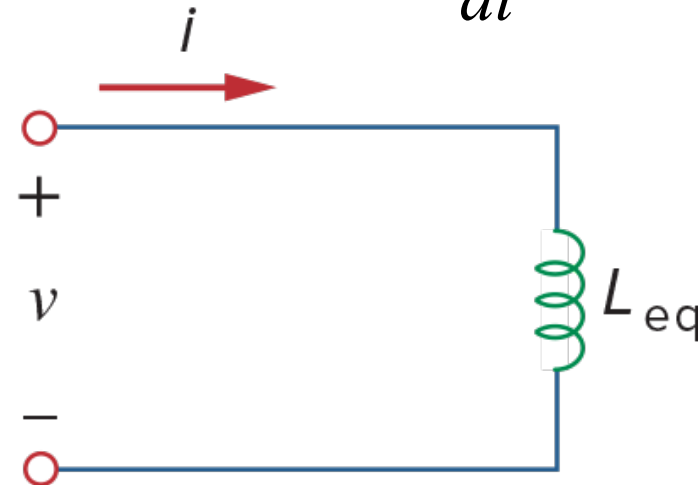


Here we can see that the **inductors** have the **same behavior as resistors**

Parallel Inductors

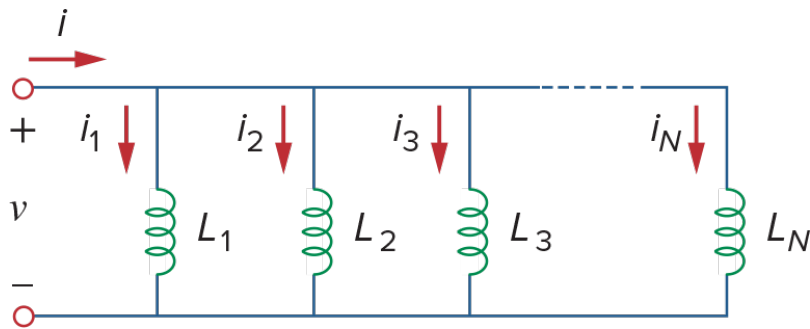

$$v = L \frac{di}{dt}$$

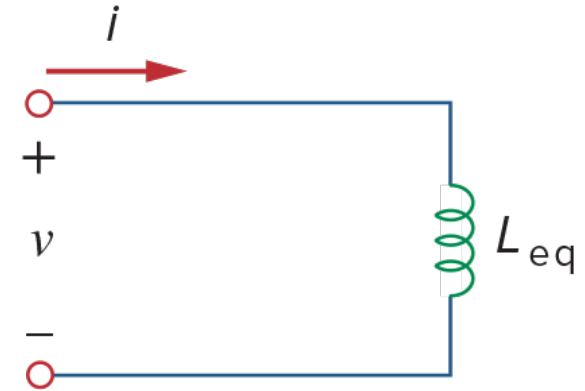

- Applying KCL to the circuit:

$$i = i_1 + i_2 + i_3 + \cdots + i_N$$

$$i = \left(\sum_{k=1}^N \frac{1}{L_k} \right) \int_{t_0}^t v dt + \sum_{k=1}^N i_k(t_0) = \frac{1}{L_{eq}} \int_{t_0}^t v dt + i(t_0)$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \cdots + \frac{1}{L_N}$$

$$i(t_0) = i_1(t_0) + i_2(t_0) + \cdots + i_N(t_0)$$


- Once again, the **parallel combination** resembles that of **resistors**
- On a related note, the **Δ -Y transformation** can also be applied to **inductors** and **capacitors** in a similar manner, as long as all elements are the same type.

Example 6.11


Find the equivalent inductance

$$\frac{7 \times 42}{7 + 42} = 6 \text{ H}$$

$$L_{eq} = 4 + 6 + 8 = 18 \text{ H}$$

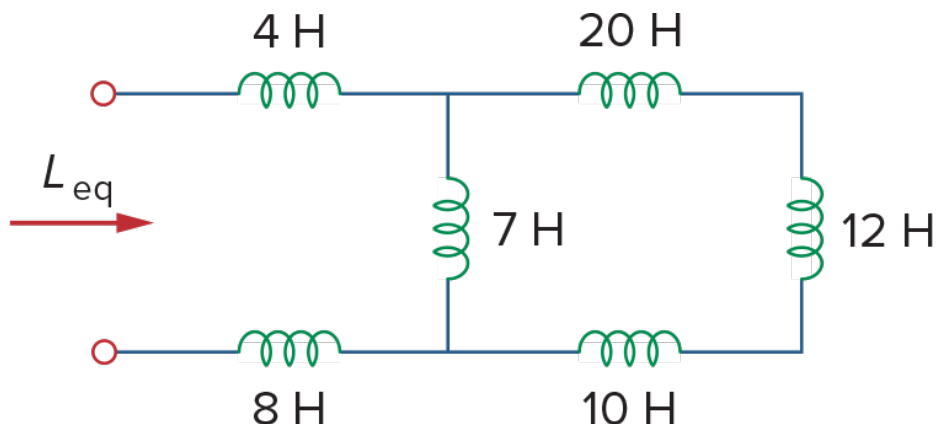

Practice Problem 6.11

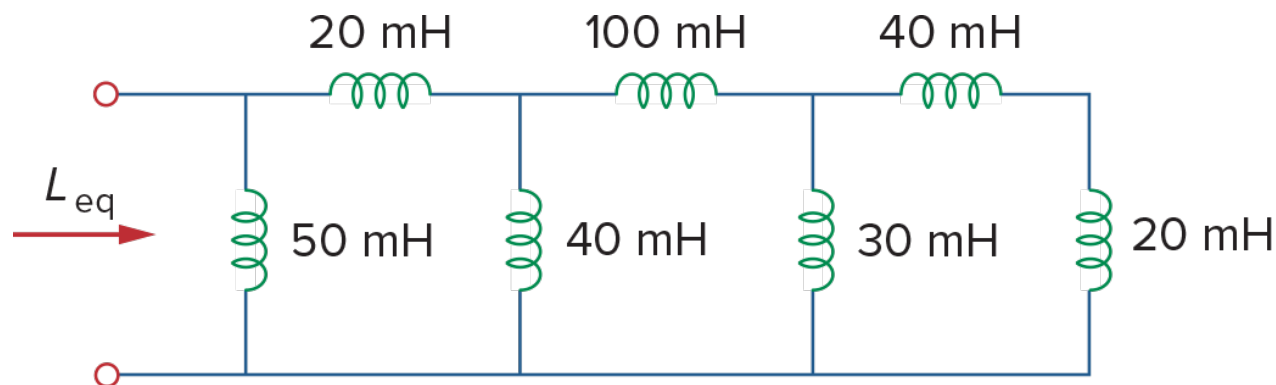

$$\begin{aligned} L_{eq} &= 50 \parallel \{20 + [40 \parallel (100 + 30 \parallel 60)]\} \\ &= 50 \parallel \{20 + [40 \parallel 120]\} \\ &= 50 \parallel \{20 + 30\} \\ &= 50 \parallel 50 \\ &= 25 \text{ (mH)} \end{aligned}$$

Example 6.12

For the, $i(t) = 4 \cdot (2 - e^{-10t})$ mA. If $i_2(0) = -1$ mA, find:

- (a) $i_1(0)$
- (b) $v(t)$, $v_1(t)$, and $v_2(t)$;
- (c) $i_1(t)$ and $i_2(t)$.

(a) From $i(t) = 4(2 - e^{-10t})$ mA,

$$i(0) = 4(2 - 1) = 4 \text{ mA}$$

$$i = i_1 + i_2$$

$$\Rightarrow i_1(0) = i(0) - i_2(0) = 4 - (-1) = 5 \text{ mA}$$


(b) The equivalent inductance

$$L_{eq} = 2 + 4 \parallel 12 = 2 + 3 = 5 \text{ H}$$

$$\begin{aligned} v(t) &= L_{eq} \frac{di(t)}{dt} \\ &= 5 \times \frac{d[4 \cdot (2 - e^{-10t})]}{dt} \\ &= 5 \times [4 \times 10 e^{-10t}] \\ &= 200 e^{-10t} \text{ (mV)} \end{aligned}$$

$$\begin{aligned} v_1(t) &= 2 \frac{di(t)}{dt} = 2 \times [4 \times 10 e^{-10t}] \\ &= 80 e^{-10t} \text{ (mV)} \end{aligned}$$
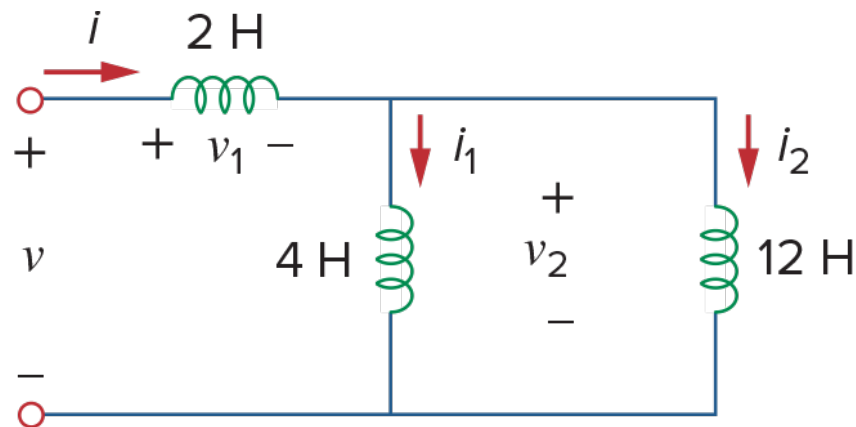
$$\begin{aligned} v_2(t) &= v(t) - v_1(t) \\ &= (200 - 80) e^{-10t} \\ &= 120 e^{-10t} \text{ (mV)} \end{aligned}$$



(c) The current i_1

$$\begin{aligned} i_1(t) &= \frac{1}{4} \int_0^t v_2(t) dt + i_1(0) \\ &= \frac{1}{4} \int_0^t 120 e^{-10t} dt + 5 \\ &= \frac{120}{4} \left(\frac{e^{-10t}}{-10} \right) \Big|_0^t + 5 \\ &= -3(e^{-10t} - e^0) + 5 \\ &= -3e^{-10t} + 8 \text{ (mA)} \end{aligned}$$

$$\begin{aligned} i_2(t) &= \frac{1}{12} \int_0^t v_2(t) dt + i_2(0) \\ &= \frac{1}{12} \int_0^t 120 e^{-10t} dt - 1 \\ &= \frac{120}{12} \left(\frac{e^{-10t}}{-10} \right) \Big|_0^t - 1 \\ &= -(e^{-10t} - e^0) - 1 \\ &= -e^{-10t} \text{ (mA)} \end{aligned}$$


Check if
 $i(t) = 4 \cdot (2 - e^{-10t})$?

Summary of Capacitors & Inductors

TABLE 6.1

Important characteristics of the basic elements.[†]


Relation	Resistor (R)	Capacitor (C)	Inductor (L)
v - i :	$v = iR$	$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$	$v = L \frac{di}{dt}$
i - v :	$i = v/R$	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$
p or w :	$p = i^2 R = \frac{v^2}{R}$	$w = \frac{1}{2} C v^2$	$w = \frac{1}{2} L i^2$
Series:	$R_{\text{eq}} = R_1 + R_2$	$C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$	$L_{\text{eq}} = L_1 + L_2$
Parallel:	$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$	$C_{\text{eq}} = C_1 + C_2$	$L_{\text{eq}} = \frac{L_1 L_2}{L_1 + L_2}$
At dc:	Same	Open circuit	Short circuit
Circuit variable that cannot change abruptly:	Not applicable	v	i

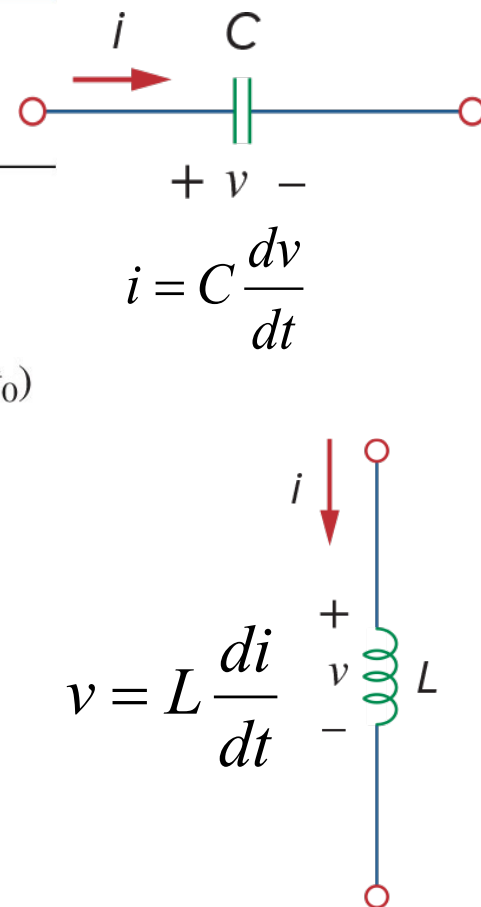

Applications

Inductors

$$v = L \frac{di}{dt}$$

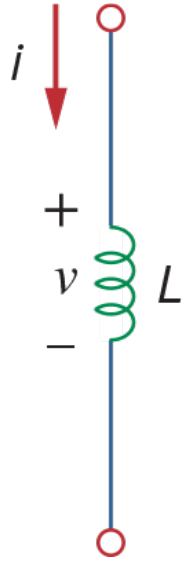

- Due to their bulky size, **inductors** are **less frequently used** as compared to **capacitors**, however they have some applications where they are best suited.
- They can be used to create a large amount of **current** or **voltage** for a short period of time.
- Their **resistance** to **sudden changes in current** can be used for spark suppression.
- Along with capacitors, they can be used for **frequency** discrimination.