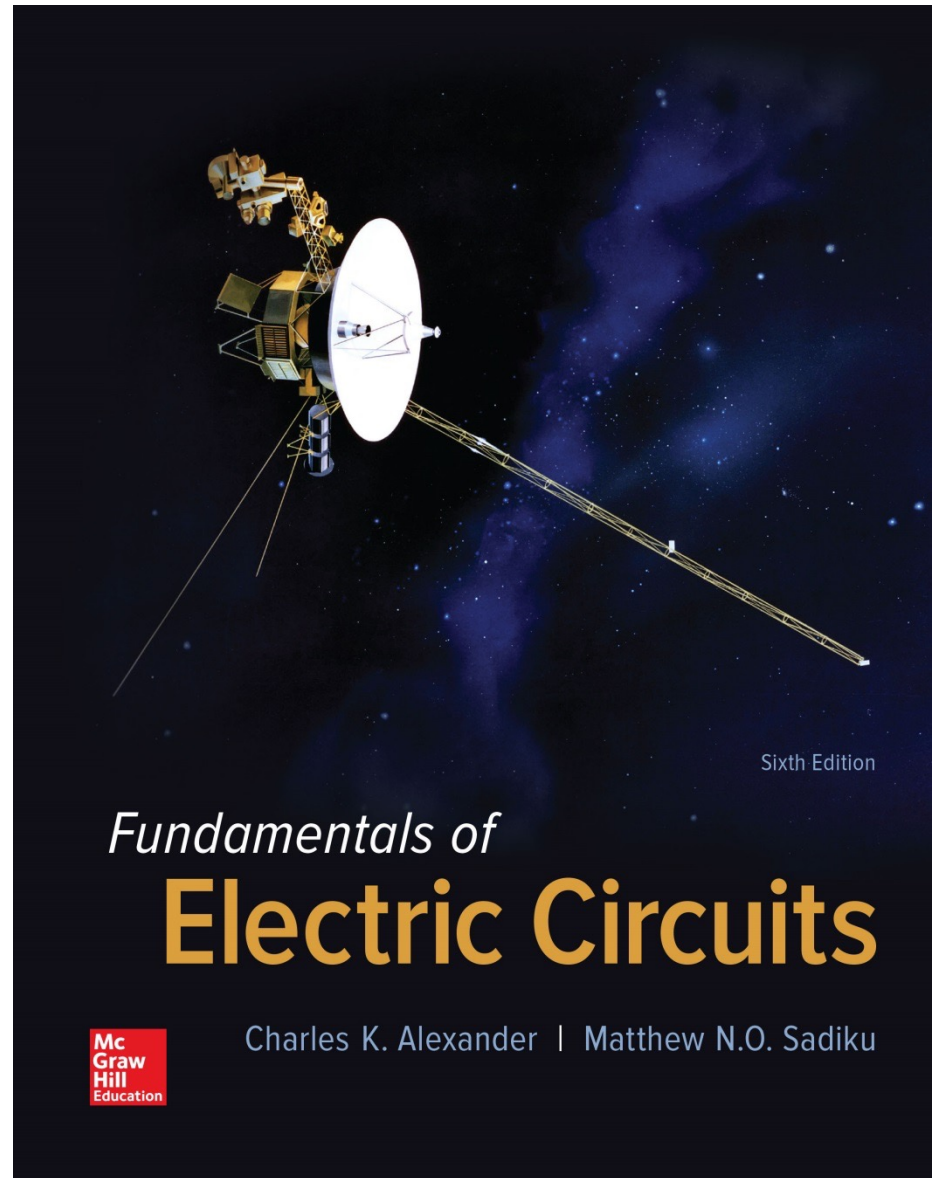


Fundamentals of Electric Circuits Chapter 14

Frequency Response



- This chapter will introduce the idea of the **transfer function**:
 - a means of describing the relationship between the **input** and **output** of a circuit.
- **Bode plots** and their utility
 - in describing the **frequency response** of a circuit will also be introduced.
- The concept of **resonance** as applied to LRC circuits will be covered as well
- Finally, **frequency filters** will be discussed.

The **frequency response** of a circuit is the variation in its behavior with change in signal frequency.

- **Frequency response is the variation in a circuit's behavior with change in signal frequency.**
- **This is significant for applications involving filters.**
- **Filters play critical roles in blocking or passing specific frequencies or ranges of frequencies.**
- **Without them, it would be impossible to have multiple channels of data in radio communications.**


14.2

Transfer Function

- One useful way to analyze the frequency response of a circuit is the concept of the transfer function $H(\omega)$.
- It is the frequency dependent ratio of a forced function $Y(\omega)$ to the forcing function

$$X(\omega) \cdot H(\omega) = Y(\omega)$$
$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

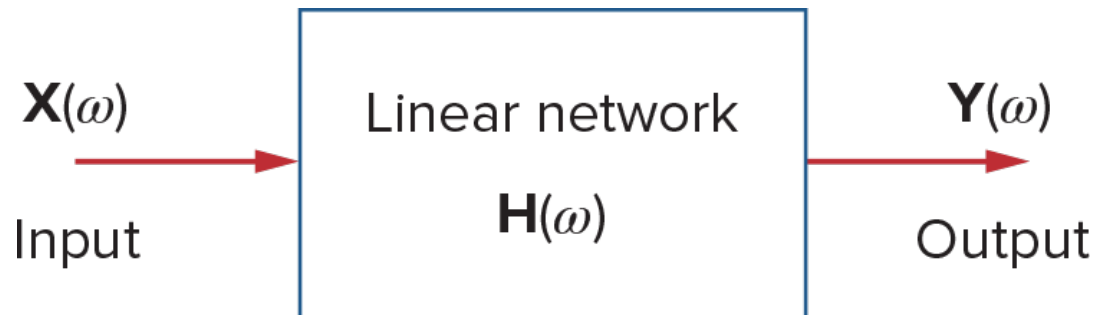$\mathbf{X}(\omega)$ and $\mathbf{Y}(\omega)$ denote the input and output phasors of a network



Transfer Function

- There are four possible input/output combinations:

$$\mathbf{H}(\omega) = \text{Voltage gain} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} \quad (14.2a)$$

$$\mathbf{H}(\omega) = \text{Current gain} = \frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)} \quad (14.2b)$$

$$\mathbf{H}(\omega) = \text{Transfer Impedance} = \frac{\mathbf{V}_o(\omega)}{\mathbf{I}_i(\omega)} \quad (14.2c)$$

$$\mathbf{H}(\omega) = \text{Transfer Admittance} = \frac{\mathbf{I}_o(\omega)}{\mathbf{V}_i(\omega)} \quad (14.2d)$$

Zeros and Poles

- To obtain $H(\omega)$, we first convert to **frequency domain** equivalent components in the circuit.
- $H(\omega)$ can be expressed as the ratio of numerator $N(\omega)$ and denominator $D(\omega)$ polynomials.

$$H(\omega) = \frac{N(\omega)}{D(\omega)}$$

- **Zeros**
 - where the transfer function goes to **zero**.
- **Poles**
 - where it goes to **infinity**.
- They can be related to the **roots** of $N(\omega)$ and $D(\omega)$

Example 14.1

For the RC circuit, obtain the transfer function V_o/V_s and its frequency response. Let $v_s = V_m \cos \omega t$.

Convert to the frequency domain

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

obtain the magnitude and phase of $\mathbf{H}(\omega)$

$$H = \frac{1}{\sqrt{1 + (\omega/\omega_0)^2}}$$

$$\phi = -\tan^{-1} \frac{\omega}{\omega_0}$$

$$\text{where } \omega_0 = 1/RC$$

Plot H and ϕ for $0 < \omega < \infty$

TABLE 14.1

For Example 14.1.

ω/ω_0	H	ϕ	ω/ω_0	H	ϕ
0	1	0	10	0.1	-84°
1	0.71	-45°	20	0.05	-87°
2	0.45	-63°	100	0.01	-89°
3	0.32	-72°	∞	0	-90°

Multiplication:


$$z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2 \quad (9.18c)$$

Division:




$$\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2 \quad (9.18d)$$

Reciprocal:
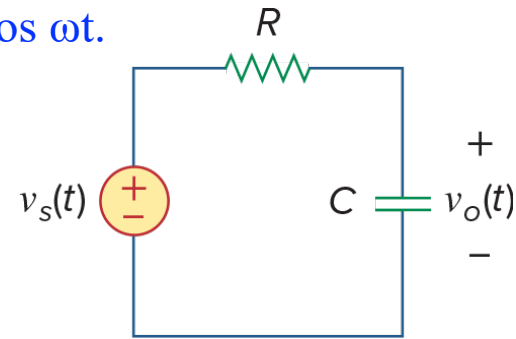
$$\frac{1}{z} = \frac{1}{r} \angle -\phi \quad (9.18e)$$



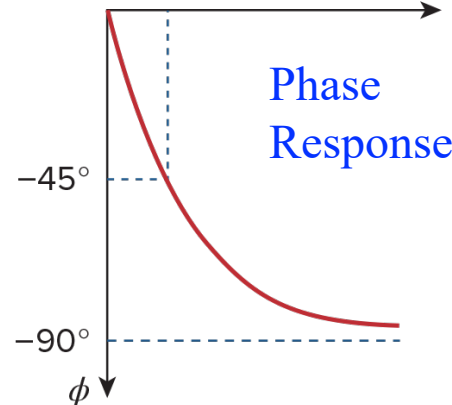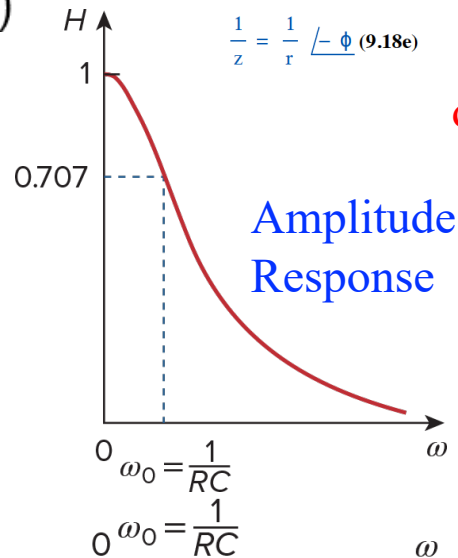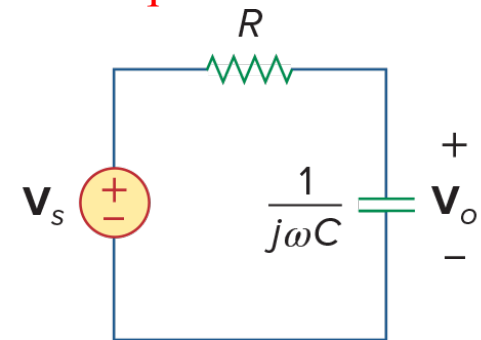Convert to the frequency domain equivalent circuit






Low-pass Filters

Practice Problem 14.1

For the RC circuit, obtain the transfer function V_O/V_S and its frequency response. Let $v_s = V_m \cos \omega t$.

$$\begin{aligned} H(\omega) &= \frac{V_O}{V_S} = \frac{j\omega L}{R + j\omega L} \\ &= \frac{1}{1 + \frac{R}{j\omega L}} \\ &= \frac{1}{1 - j\frac{R/L}{\omega}} \end{aligned}$$

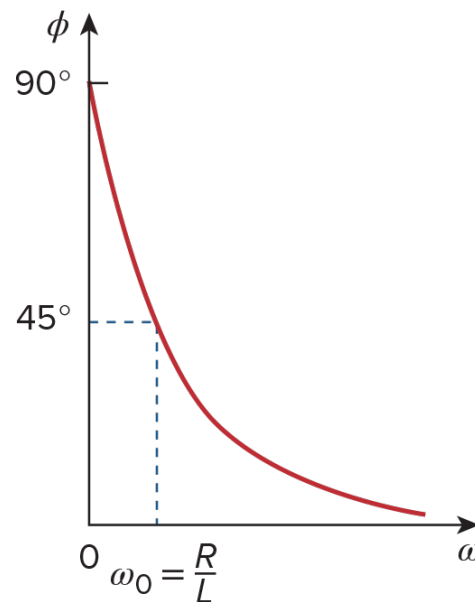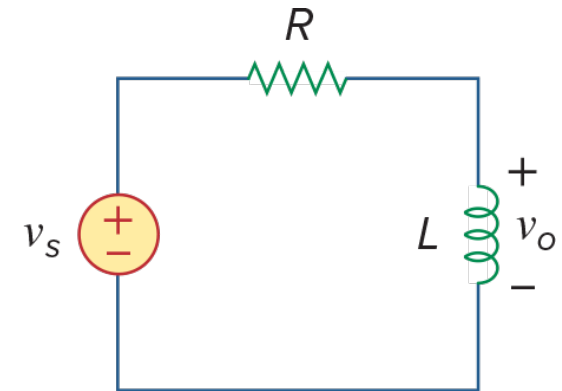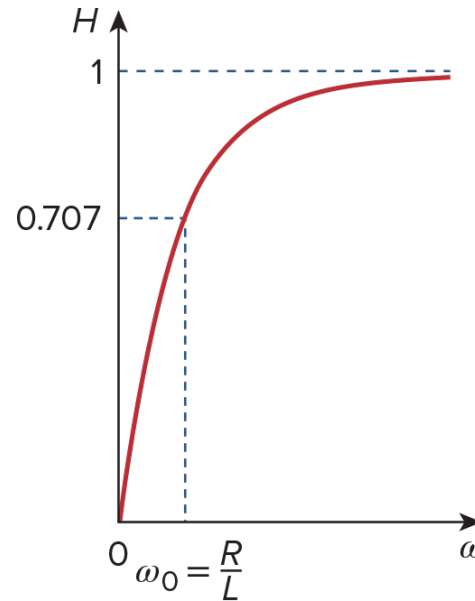


Example 14.2

For the circuit, calculate the gain $I_o(\omega)/I_i(\omega)$ and its poles and zeros.

By current division

$$I_o(\omega) = \frac{4 + j2\omega}{4 + j2\omega + 1/j0.5\omega} I_i(\omega)$$
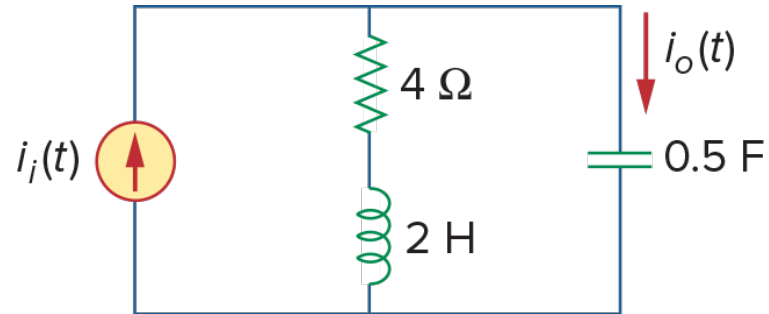
$$\frac{I_o(\omega)}{I_i(\omega)} = \frac{j0.5\omega(4 + j2\omega)}{1 + j2\omega + (j\omega)^2} = \frac{s(s + 2)}{s^2 + 2s + 1} \leftarrow s = j\omega$$



The zeros

$$s(s + 2) = 0 \Rightarrow z_1 = 0, z_2 = -2$$

The poles

$$s^2 + 2s + 1 = (s + 1)^2 = 0 \Rightarrow p = -1$$

repeated pole
(or double pole)

14.3

† The Decibel Scale

- Bode plots
- These plots are based on **logarithmic** scales.
- The transfer function
 - as an expression of gain.
- **Gain** expressed in **log form**
 - typically expressed in bels
 - or more commonly **decibels** (1/10 of a bel)

$$1. \log P_1 P_2 = \log P_1 + \log P_2$$

$$2. \log P_1 / P_2 = \log P_1 - \log P_2$$

$$3. \log P^n = n \log P$$

$$4. \log 1 = 0$$

power gain G

$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1}$$

reason why logarithms are greatly used


$$G_{dB} = 10 \log_{10} 2 \approx 3 \text{ dB}$$

$$G_{dB} = 10 \log_{10} 0.5 \approx -3 \text{ dB}$$

The logarithm of the reciprocal of a quantity is simply negative the logarithm of that quantity.

The gain G can be expressed in terms of voltage or current ratio

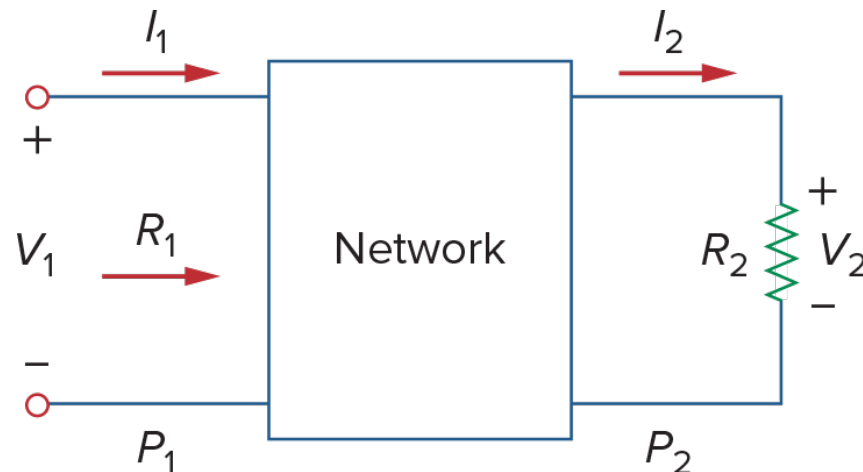If P_1 is the input power,
 P_2 is the output (load) power,
 R_1 is the input resistance,
 R_2 is the load resistance.



$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \frac{V_2^2 / R_2}{V_1^2 / R_1}$$
$$= 10 \log_{10} \left(\frac{V_2}{V_1} \right)^2 + 10 \log_{10} \frac{R_1}{R_2}$$

$$G_{dB} = 20 \log_{10} \frac{V_2}{V_1} - 10 \log_{10} \frac{R_2}{R_1}$$

For the case when $R_2 = R_1$

when comparing **voltage** levels

$$G_{dB} = 20 \log_{10} \frac{V_2}{V_1}$$

when comparing **current** levels

$$G_{dB} = 20 \log_{10} \frac{I_2}{I_1}$$

14.4

Bode Plots

Bode plots are semilog plots of the magnitude (in decibels) and phase (in degrees) of a transfer function versus frequency.

- One problem with the transfer function is that it needs to cover a **large range in frequency**.
- Plotting the frequency response on a **semilog** plot makes the task easier
 - where the x axis is plotted in log form

- **⇒ Bode plots**

- Bode plots either show
 - **magnitude** (in **decibels**)
 - **phase** (in **degrees**)as a function of **frequency**.

$$\mathbf{H} = H \angle \phi = H e^{j\phi}$$

$$\ln \mathbf{H} = \ln H + \ln e^{j\phi} = \ln H + j\phi$$

$$H_{\text{dB}} = 20 \log_{10} H$$

Standard Form



- The transfer function:

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1) \left[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2 \right] \cdots}{(1 + j\omega/p_1) \left[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2 \right] \cdots}$$

- This standard form may include the following seven factors in various combinations:
 - A gain **K**
 - A pole $(j\omega)^{-1}$
or a zero $(j\omega)$
 - A simple pole $1/(1+j\omega/p_1)$
or a simple zero $(1+j\omega/z_1)$
 - A quadratic pole $1/[1+j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$
or zero $[1+j2\zeta_1\omega/\omega_n + (j\omega/\omega_k)^2]$

Bode Plots

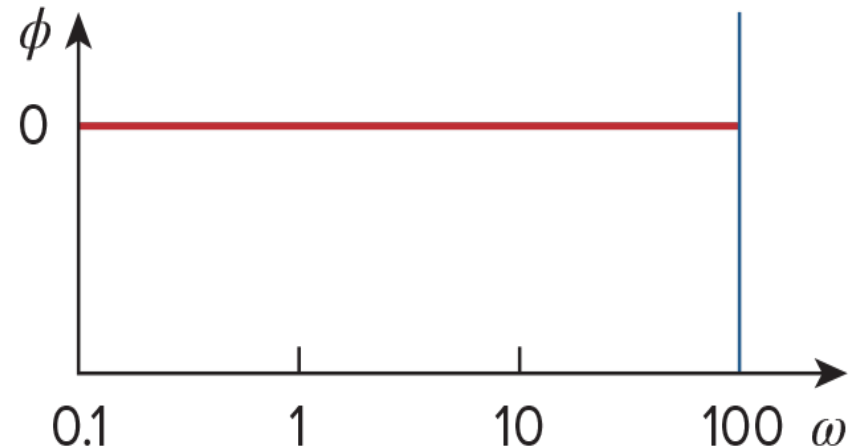
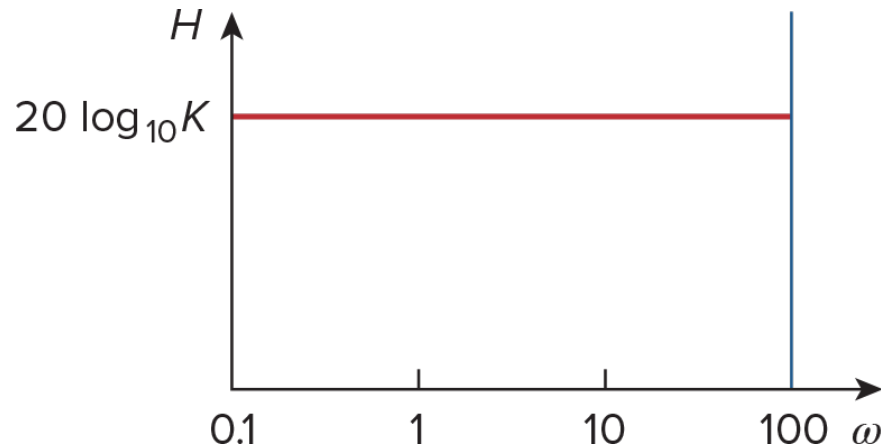
- In a bode plot, each of these factors is plotted separately and then added graphically.
- Gain, K : the magnitude is $20\log_{10}K$ and the phase is 0° . Both are constant with frequency.



Bode Plots

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1) \left[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2 \right] \cdots}{(1 + j\omega/p_1) \left[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2 \right] \cdots}$$

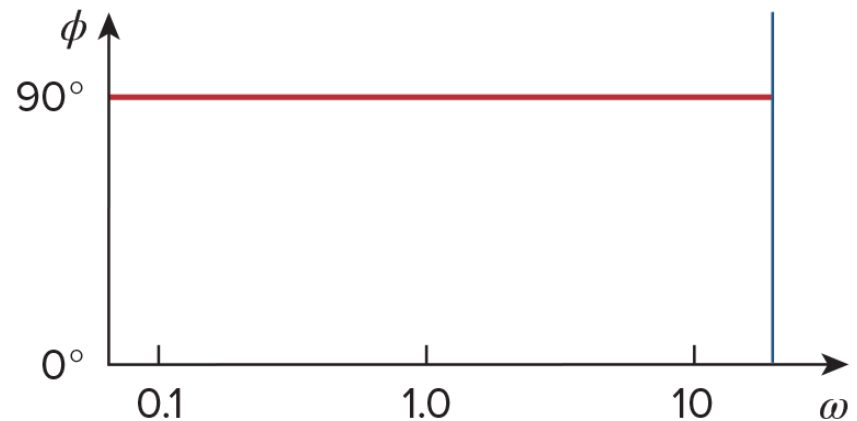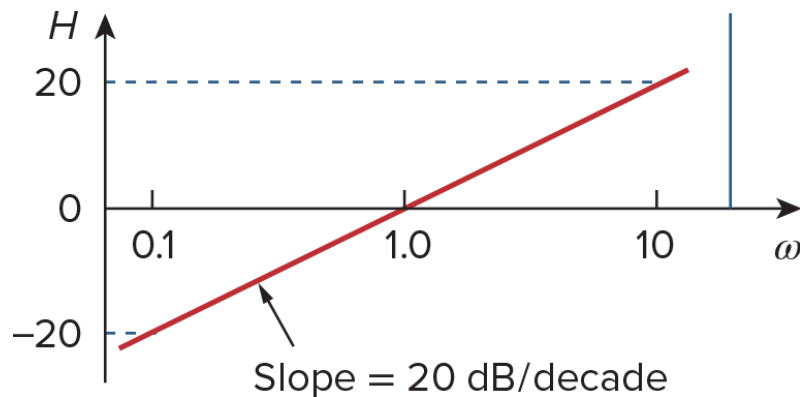- Pole/zero at the origin:
 - For the **zero** $(j\omega)$, the slope in magnitude is **20 dB/decade** and the **phase is 90°** .
 - For the **pole** $(j\omega)^{-1}$ the slope in magnitude is **-20 dB/decade** and the **phase is -90°**



Bode Plots

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1) \left[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2 \right] \dots}{(1 + j\omega/p_1) \left[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2 \right] \dots}$$

- Simple zero


- the magnitude is $20\log_{10}|1+j\omega/z_1|$

- the phase is $\tan^{-1} \omega/z_1$

where:

$$H_{dB} = 20\log_{10} \left| 1 + \frac{j\omega}{z_1} \right| \Rightarrow 20\log_{10} \frac{\omega}{z_1} \quad \text{as } \omega \rightarrow \infty$$

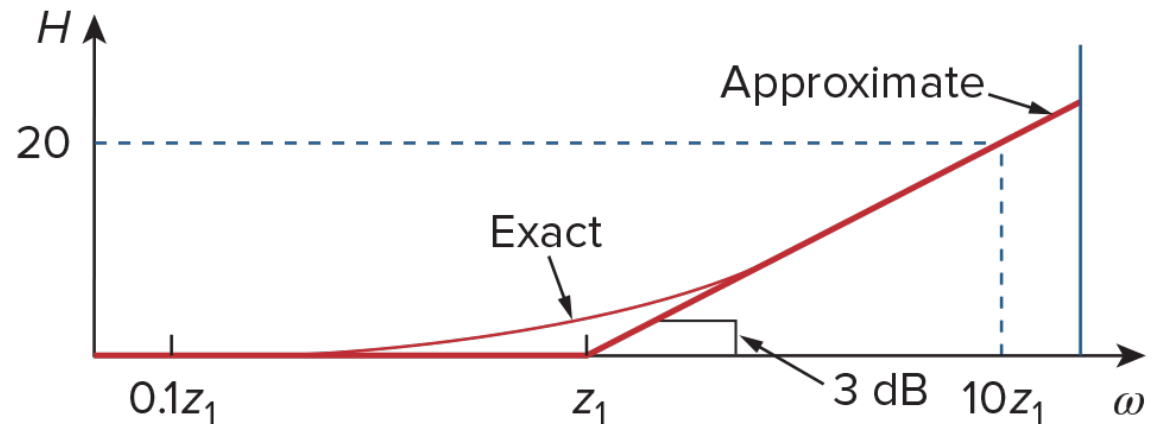- The pole is similar, except the corner frequency is at $\omega=p_1$, the magnitude has a negative slope
- approximated as a flat line and sloped line that intersect at $\omega=z_1$ (corner or break frequency)




Bode Plots

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1) \left[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2 \right] \cdots}{(1 + j\omega/p_1) \left[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2 \right] \cdots}$$

- The **phase** can be plotted as a series straight lines
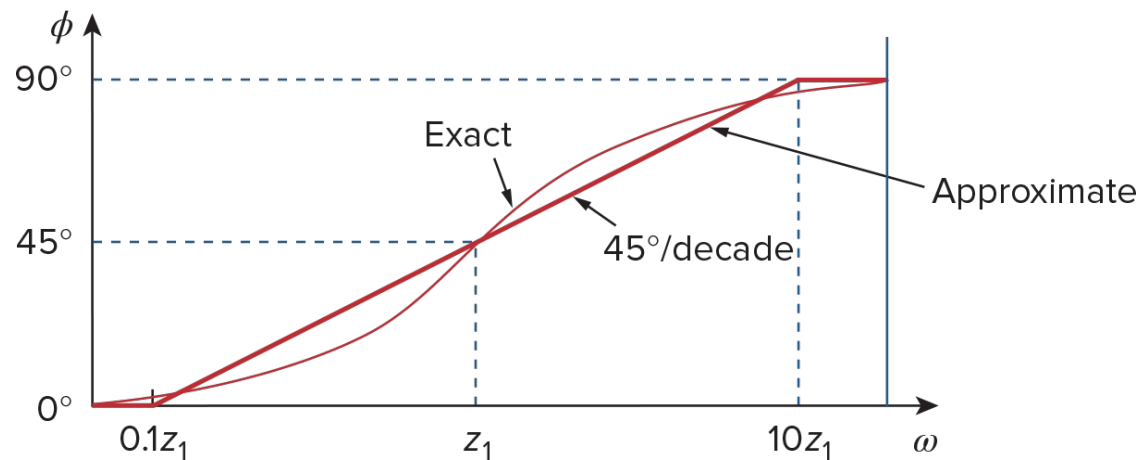
$$\phi = \tan^{-1}\left(\frac{\omega}{z_1}\right) = \begin{cases} 0^\circ, & \omega = 0 \\ 45^\circ, & \omega = z_1 \\ 90^\circ, & \omega \rightarrow \infty \end{cases}$$




Bode Plots

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega / z_1) \left[1 + j2\zeta_1 \omega / \omega_k + (j\omega / \omega_k)^2 \right] \cdots}{(1 + j\omega / p_1) \left[1 + j2\zeta_2 \omega / \omega_n + (j\omega / \omega_n)^2 \right] \cdots}$$

- The **phase** can be plotted as a series straight lines
- From **$\omega=0$** to **$\omega \leq z_1/10$** , we let $\phi=0$
- At $\omega=z_1$ we let $\phi=45^\circ$
- For $\omega \geq 10z_1$, we let $\phi=90^\circ$
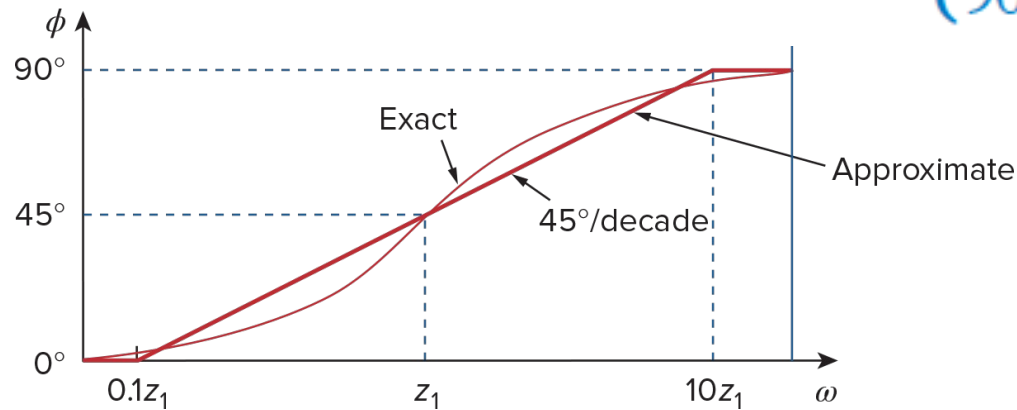
$$\phi = \tan^{-1}\left(\frac{\omega}{z_1}\right) = \begin{cases} 0, & \omega = 0 \\ 45^\circ, & \omega = z_1 \\ 90^\circ, & \omega \rightarrow \infty \end{cases}$$



Bode Plots Quadratic pole/zero


- Quadratic pole:

- The magnitude of the quadratic pole $1/[1+j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$
 - $-20\log_{10} [1+j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$

$$H_{dB} \begin{matrix} \Rightarrow 0 \\ \text{as } \omega \rightarrow 0 \end{matrix} \Rightarrow -40\log_{10} \frac{\omega}{\omega_n} \begin{matrix} \\ \text{as } \omega \rightarrow \infty \end{matrix}$$

- The magnitude plot will be two lines:

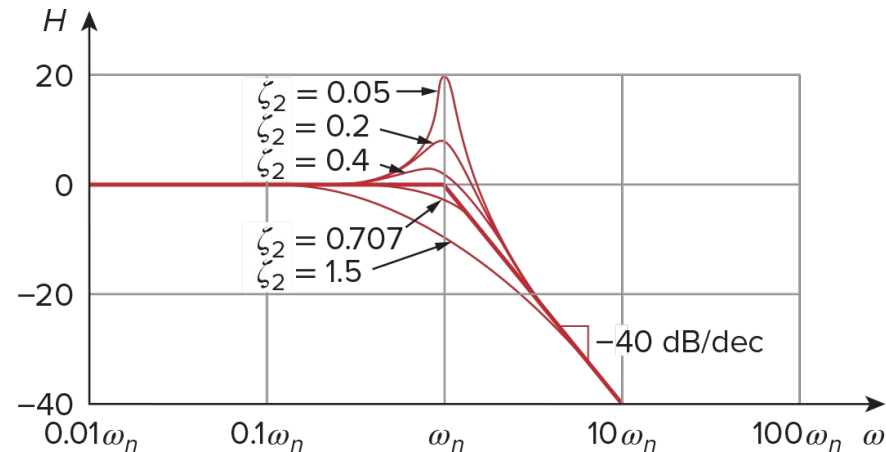- slope zero for $\omega < \omega_n$
- slope -40dB/decade, with ω_n as the corner frequency




- Quadratic zero, the plots are inverted.

Bode Plots Quadratic pole/zero

- The phase can be expressed as:

$$\phi = -\tan^{-1} \frac{2\zeta_2 \omega / \omega_n}{1 - \omega^2 / \omega_n^2} = \begin{cases} 0 & \omega = 0 \\ -90^\circ & \omega = \omega_n \\ -180^\circ & \omega \rightarrow \infty \end{cases}$$

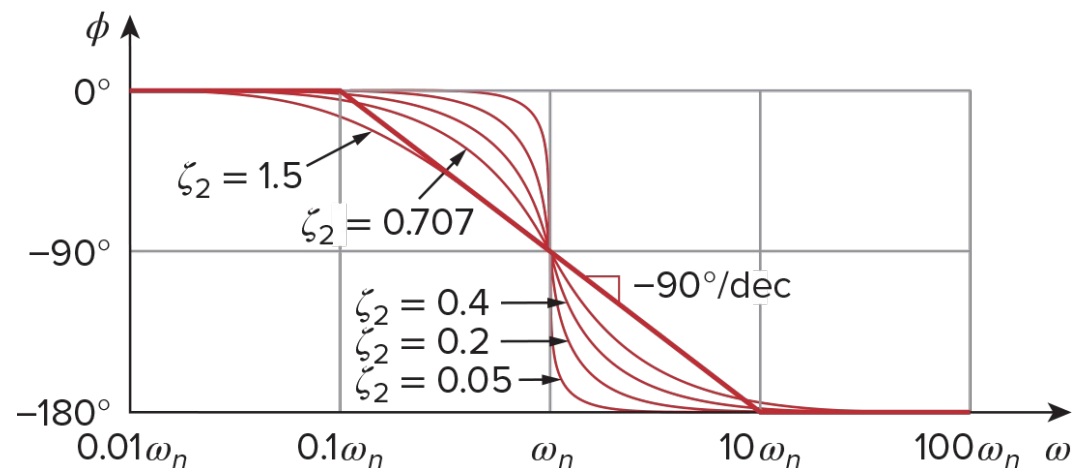- This will be a straight line with **slope of $-90^\circ/\text{decade}$** starting at $\omega_n/10$ and ending at $10\omega_n$.



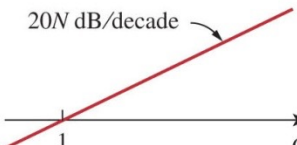

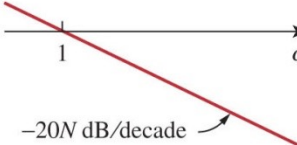

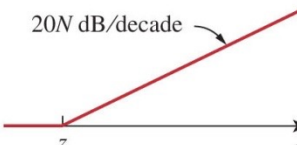
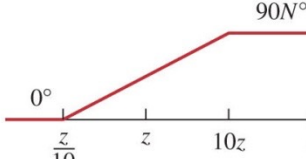


Bode Plots

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display



TABLE 14.3

Summary of Bode straight-line magnitude and phase plots.



Factor	Magnitude	Phase
K	$20 \log_{10} K$ 	
$(j\omega)^N$	$20N \text{ dB/decade}$ 	$90N^\circ$ 
$\frac{1}{(j\omega)^N}$	 $-20N \text{ dB/decade}$	 $-90N^\circ$
$\left(1 + \frac{j\omega}{z}\right)^N$	$20N \text{ dB/decade}$ 	

Bode Plots



$$\frac{1}{(1 + j\omega/p)^N}$$

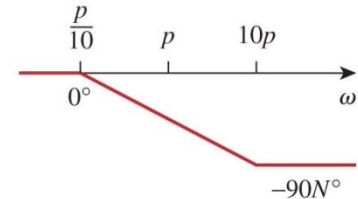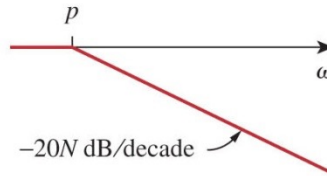
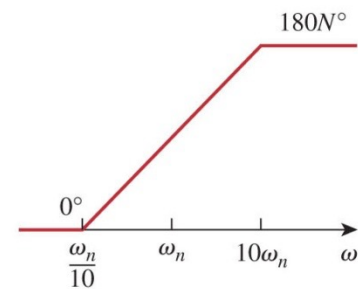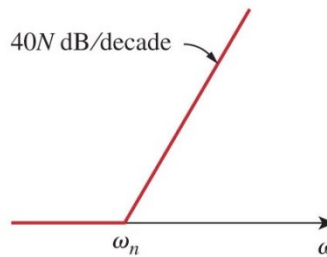
$$\left[1 + \frac{2j\omega\zeta}{\omega_n} + \left(\frac{j\omega}{\omega_n} \right)^2 \right]^N$$



$$\frac{1}{[1 + 2j\omega\zeta/\omega_k + (j\omega/\omega_k)^2]^N}$$

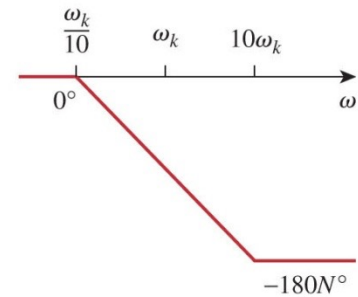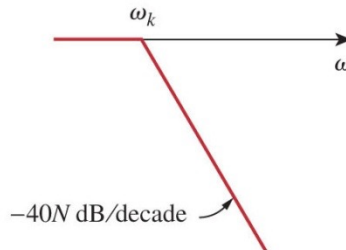

Example 14.3

Construct the Bode plots for the transfer function

$$\mathbf{H}(\omega) = \frac{200j\omega}{(j\omega + 2)(j\omega + 10)}$$


Converting $H(\omega)$ in the standard form

$$\begin{aligned}\mathbf{H}(\omega) &= \frac{10j\omega}{(1 + j\omega/2)(1 + j\omega/10)} \\ &= \frac{10|j\omega|}{|1 + j\omega/2||1 + j\omega/10|} \angle 90^\circ - \tan^{-1} \omega/2 - \tan^{-1} \omega/10\end{aligned}$$

$$H_{\text{dB}} = 20 \log_{10} 10 + 20 \log_{10} |j\omega| - 20 \log_{10} \left| 1 + \frac{j\omega}{2} \right| - 20 \log_{10} \left| 1 + \frac{j\omega}{10} \right|$$

$$\phi = 90^\circ - \tan^{-1} \frac{\omega}{2} - \tan^{-1} \frac{\omega}{10}$$

two corner frequencies at $\omega=2, 10$ rad/s

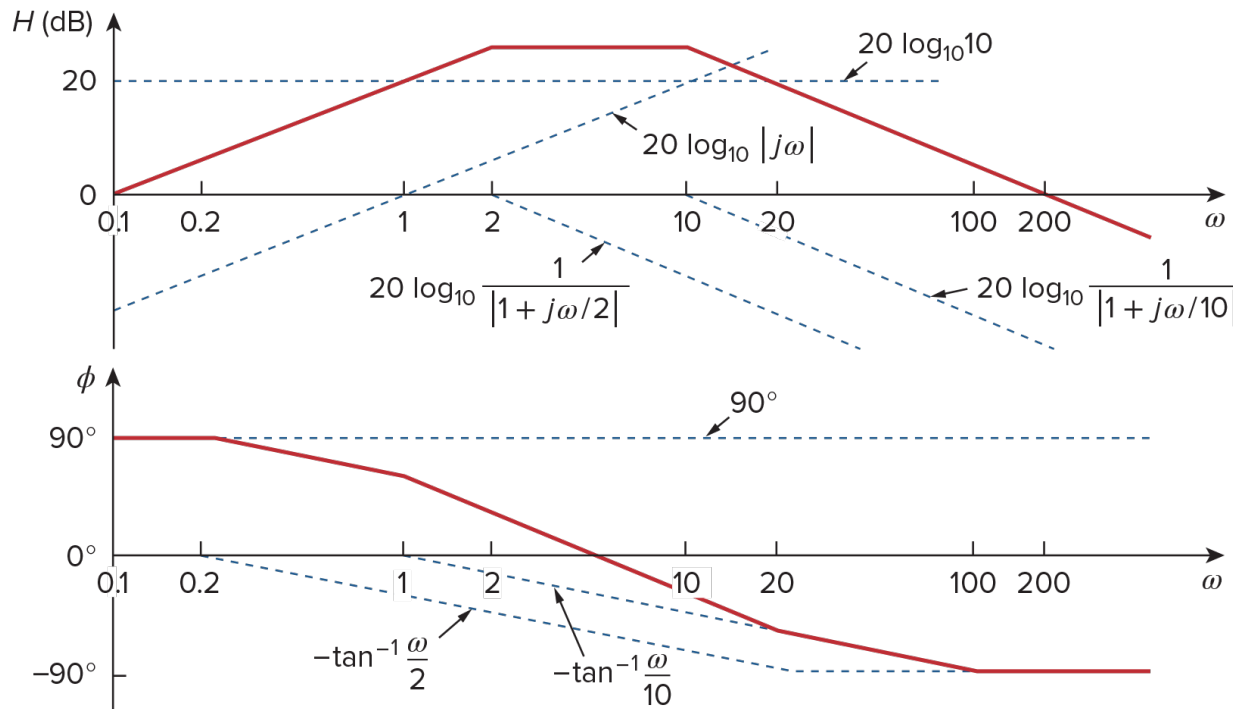

Example 14.4

Construct the Bode plots for the transfer function

$$\mathbf{H}(\omega) = \frac{j\omega + 10}{j\omega(j\omega + 5)^2}$$



Converting $\mathbf{H}(\omega)$ in the standard form

$$\mathbf{H}(\omega) = \frac{0.4(1 + j\omega/10)}{j\omega(1 + j\omega/5)^2}$$

$$H_{\text{dB}} = 20 \log_{10} 0.4 + 20 \log_{10} \left| 1 + \frac{j\omega}{10} \right| - 20 \log_{10} |j\omega| - 40 \log_{10} \left| 1 + \frac{j\omega}{5} \right|$$

$$\phi = 0^\circ + \tan^{-1} \frac{\omega}{10} - 90^\circ - 2 \tan^{-1} \frac{\omega}{5}$$

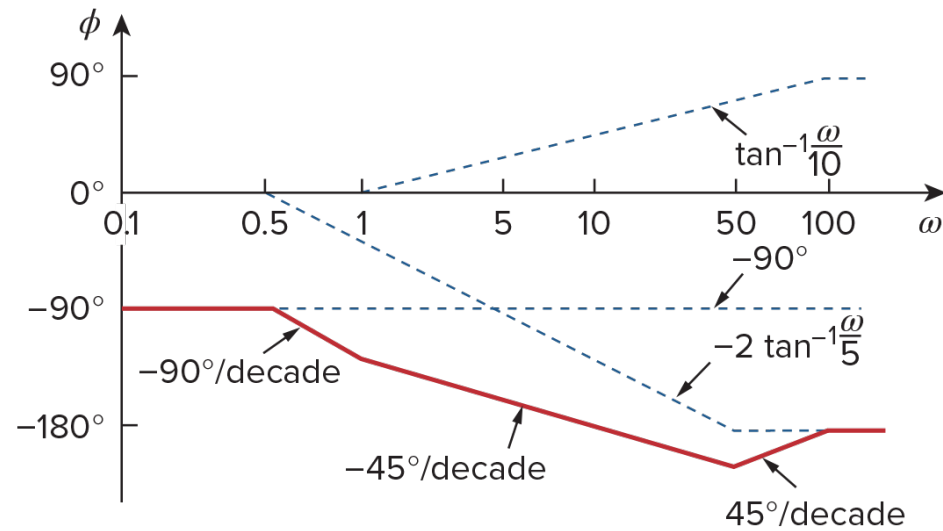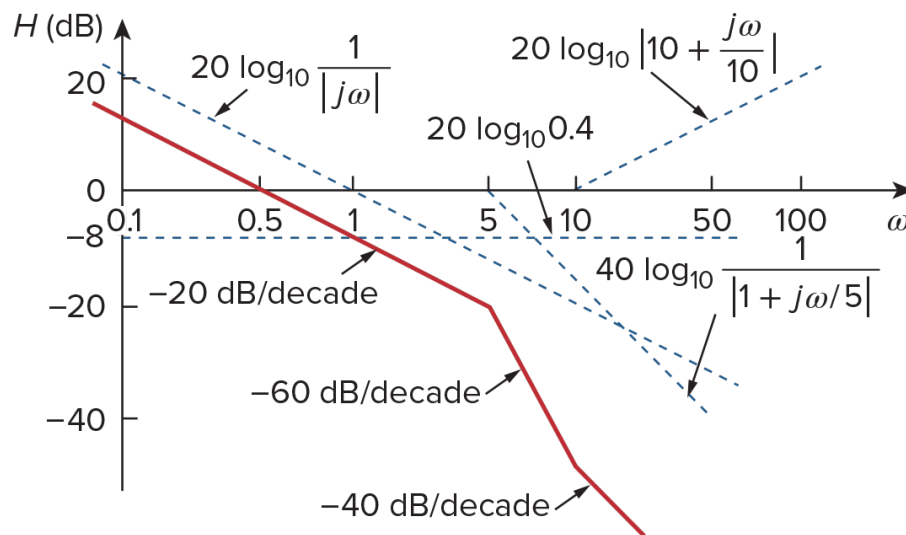two corner frequencies at $\omega=5, 10$ rad/s



- A **filter** is a circuit that is designed to
 - pass signals with **desired frequencies**
 - reject or **attenuate** others.
- **Passive filter** consists only of passive elements:
 - **R**, **L**, and **C**.
- They are very important circuits in that many technological advances would not have been possible without the development of filters.

Passive Filters





- **Low-pass Filter**
 - passes only low frequencies and blocks high frequencies.
- **High-pass Filter**
 - does the opposite of lowpass
- **Band-pass Filter**
 - only allows a range of frequencies to pass through.
- **Band-stop Filter**
 - does the opposite of bandpass

TABLE 14.5

Summary of the characteristics of ideal filters.

Type of Filter	$H(0)$	$H(\infty)$	$H(\omega_c)$ or $H(\omega_0)$
Lowpass	1	0	$1/\sqrt{2}$
Highpass	0	1	$1/\sqrt{2}$
Bandpass	0	0	1
Bandstop	1	1	0

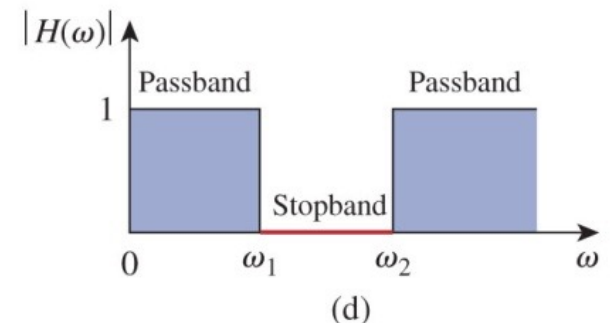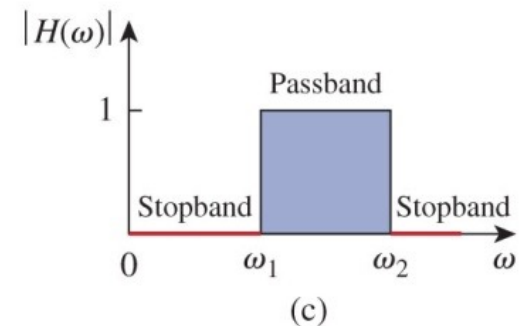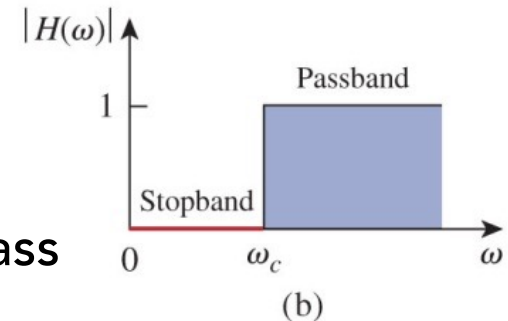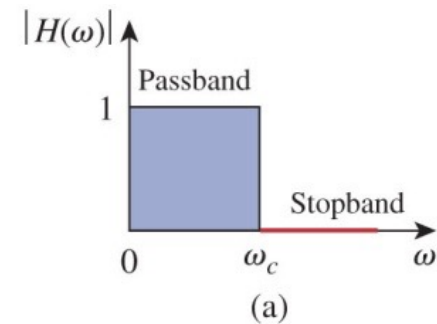ω_c is the cutoff frequency for lowpass and highpass filters; ω_0 is the center frequency for bandpass and bandstop filters.





14.7.1 Low-Pass Filter

$$H(\omega) = \frac{V_o}{V_i} = \frac{1/j\omega C}{R + 1/j\omega C} \Rightarrow H(\omega) = \frac{1}{1 + j\omega RC}$$

$$H(\omega_c) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}} \Rightarrow \omega_c = \frac{1}{RC}$$

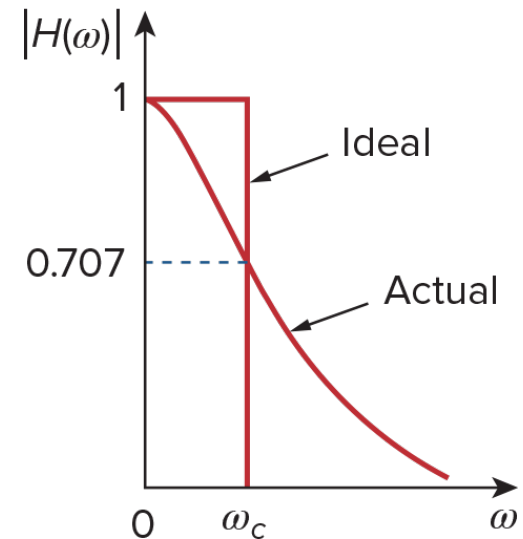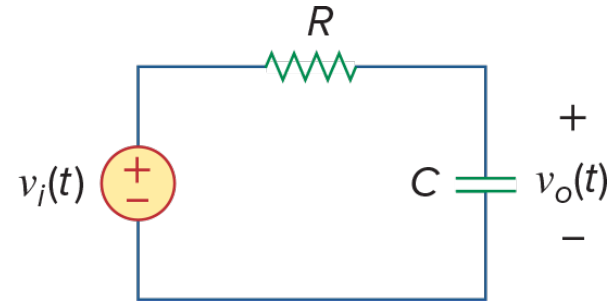- **Low-pass** filter
 - when the output of a RC circuit is taken off the capacitor.
- **ω_c**
 - The half power frequency
 - cutoff frequency
 - or 3dB frequency.
- The filter is designed to pass from DC up to **ω_c**





14.7.2 High-Pass Filter

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + 1/j\omega C} \Rightarrow H(\omega) = \frac{j\omega RC}{1 + j\omega RC}$$


$$\Rightarrow \omega_c = \frac{1}{RC}$$

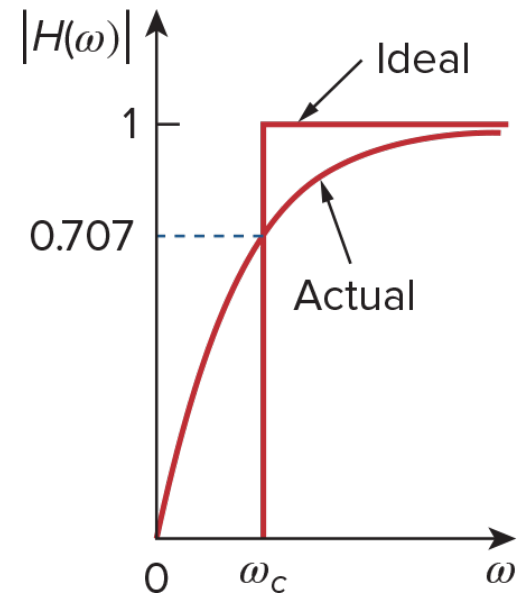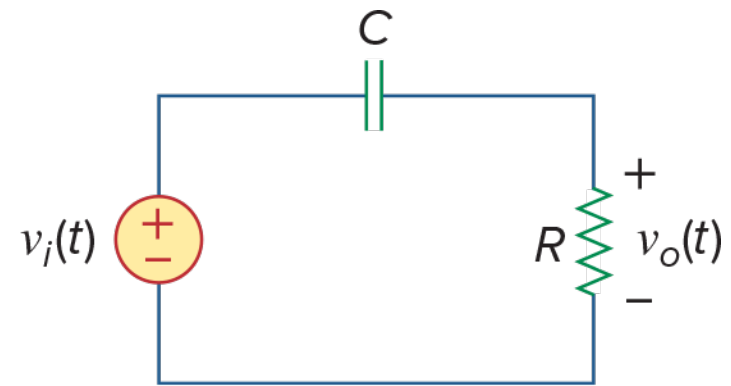- **High-pass** filter
 - when the output taken off the resistor.
- **ω_c**
 - The half power frequency
 - cutoff frequency
 - or 3dB frequency.
- The cutoff frequency will be the same as the lowpass filter.
- The difference being that the frequencies passed go from **ω_c** to **infinity**.



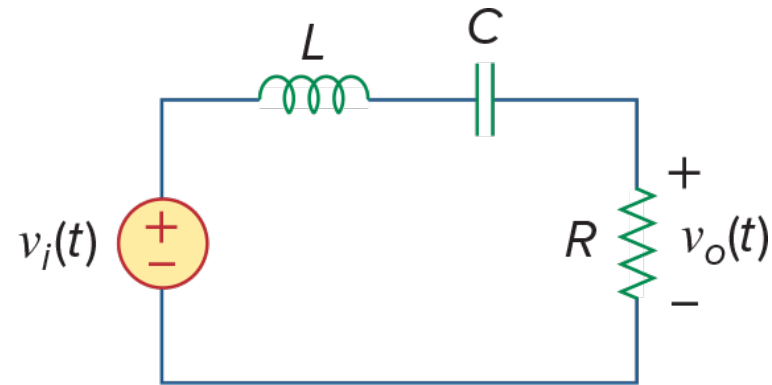
14.7.3 Band-Pass Filter

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + j(\omega L - 1/\omega C)} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$



- **Band-pass filter**
 - The **RLC series resonant** circuit
 - when the output is taken off the resistor.

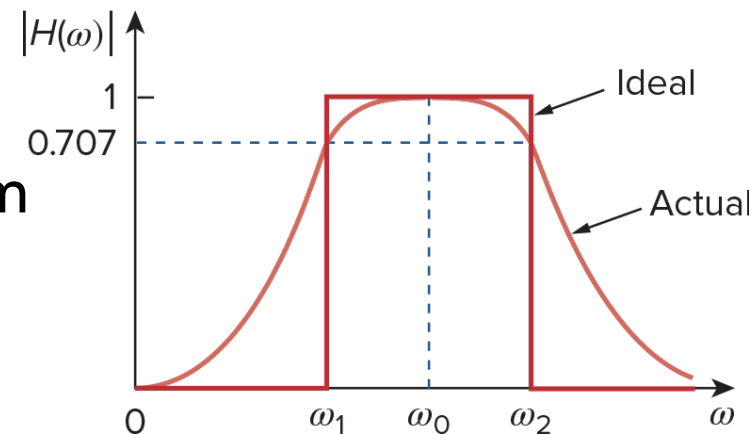- **ω_0**
 - The **center frequency**
- The filter will **pass frequencies** from **ω_1** to **ω_2** .
 - passes a band of frequencies
 - **$\omega_1 < \omega < \omega_2$** centered on **$\omega_0$**





- It can also be made by feeding the **output** from a **low-pass** to a **high-pass filter**.

14.7.4 Band-Stop Filter

$$H(\omega) = \frac{V_o}{V_i} = \frac{j(\omega L - 1/\omega C)}{R + j(\omega L - 1/\omega C)} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

- **Band-Stop (Band-Reject) filter**
 - The **RLC series resonant** circuit
 - the output is taken off the taken off the **LC** series combination.
- The range of blocked frequencies
 - the same as the range of passed frequencies for the band-pass filter.
- ω_0 – center frequency
- The filter will **reject frequencies** from ω_1 to ω_2 .
 - rejects a band of frequencies
 - $\omega_1 < \omega < \omega_2$ centered on ω_0

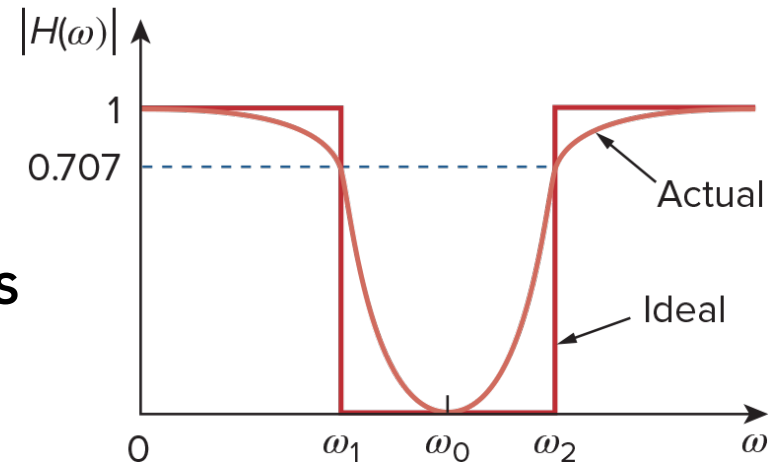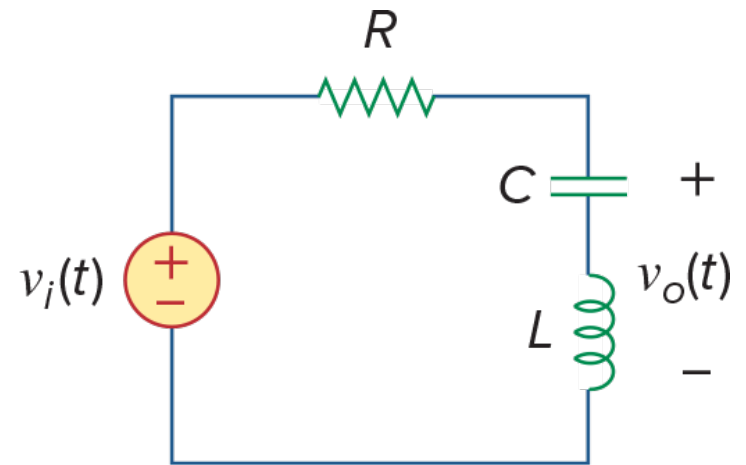

Example 14.10

Determine what type of filter. Calculate the corner or cutoff frequency. Take $R = 2 \text{ k}\Omega$, $L = 2 \text{ H}$, and $C = 2 \text{ }\mu\text{F}$.

The transfer function

$$\mathbf{H}(s) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{R \parallel 1/sC}{sL + R \parallel 1/sC}, \quad s = j\omega \quad R \parallel \frac{1}{sC} = \frac{R/sC}{R + 1/sC} = \frac{R}{1 + sRC}$$

$$\Rightarrow \mathbf{H}(s) = \frac{R/(1 + sRC)}{sL + R/(1 + sRC)} = \frac{R}{s^2RLC + sL + R}, \quad s = j\omega$$

$$\mathbf{H}(\omega) = \frac{R}{-\omega^2RLC + j\omega L + R}$$


$\mathbf{H}(0) = 1$ & $\mathbf{H}(\infty) = 0 \Rightarrow$ second-order low-pass filter

$$H = \frac{R}{\sqrt{(R - \omega^2RLC)^2 + \omega^2L^2}}$$

The corner frequency is the same as the half-power frequency, that is, where H is reduced by a factor of $1/\sqrt{2}$.

dc value of $\mathbf{H}(\omega)$ is 1
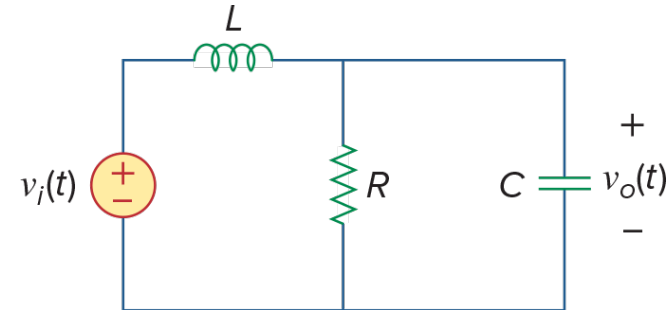
$$\Rightarrow H^2 = \frac{1}{2} = \frac{R^2}{(R - \omega_c^2RLC)^2 + \omega_c^2L^2}$$



$$\Rightarrow 2 = (1 - \omega_c^2LC)^2 + \left(\frac{\omega_c L}{R}\right)^2$$

$$2 = (1 - \omega_c^2 4 \times 10^{-6})^2 + (\omega_c 10^{-3})^2$$

$$2 = (1 - 4\omega_c^2)^2 + \omega_c^2$$

$$16\omega_c^4 - 7\omega_c^2 - 1 = 0$$

$$\omega_c^2 = 0.5509 \text{ and } -0.1134$$

$$\omega_c = 0.742 \text{ krad/s} = 742 \text{ rad/s}$$